

## STEADY-STATE SINUSOIDAL ANALYSIS


So far, we have considered circuits in which the sources are D.C. We now investigate circuits where the sources deliver sinusoidal (AC) currents and voltages.

- methods of analysis are identical.
- arithmetic changes from real to complex.
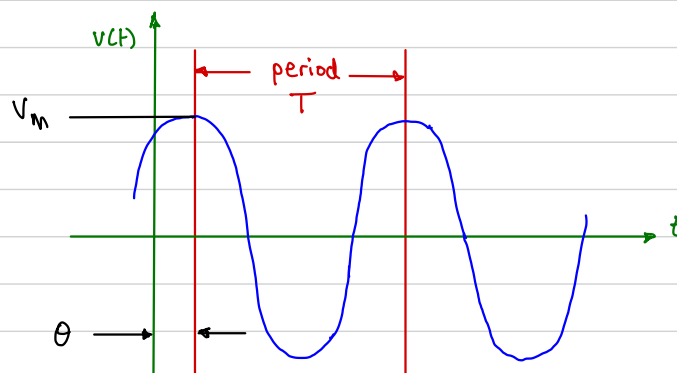
## Sinusoidal voltages and currents

Let  $v(t) = V_m \cos(\omega t + \theta)$

peak value  $\nearrow$   $V_m$   $\nwarrow$  phase angle (radians)  
radian frequency (radians/sec)  $\nwarrow$   $\omega$



The sinusoid is periodic with period  $T$ . We have one complete period when the angle increases by  $2\pi$  radians.

$$\left. \begin{array}{l} \omega t \\ t = T \end{array} \right| = 2\pi, \quad \text{so } \omega T = 2\pi$$

$$\text{and } T = \frac{2\pi}{\omega}$$

Frequency is defined as the number of complete periods (cycles) per second.

$$f = \frac{1}{T}, \quad f = \text{frequency in Hertz (Hz)}$$

We also have

$$\omega = \frac{2\pi}{T}, \quad \text{so } \omega = 2\pi f.$$

By convention, we use cosine and not sine. They are related by a simple phase difference:

$$\begin{aligned}\sin(\omega t) &= \cos(\omega t - \pi/2) \\ &= \cos(\omega t - 90^\circ)\end{aligned}$$

We say that  $\sin(\omega t)$  has the phase angle of  $-90^\circ$  (or  $-\pi/2$  rads).

### Root-mean-square values

We often express voltages and currents in terms of their peak values ( $V_m, I_m$ ), but also in terms of their root-mean-square (rms) values.

Consider power in a resistor over one period of the waveform.  
Instantaneous power is simply

$$p(t) = v(t)i(t) = \frac{v(t)}{R}, \quad v(t) = \frac{v^2(t)}{R}$$

The energy over one period is  $E_T = \int_0^T p(t) dt$ , where  $p(t) = v^2(t)/R$ .

An important measure is average power over one period.

$$P_{\text{avg}} = \frac{E_T}{T} = \frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt$$

which can be expressed as

$$P_{\text{avg}} = \frac{\left[ \sqrt{\frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt} \right]^2}{R} = \frac{V_{\text{rms}}^2}{R}$$

Thus, we define rms voltage as

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt}$$

root                      mean                      square

Rms values are sometimes called effective values. In the real world,

- AC voltages are specified as rms, not peak (e.g., household voltages are in the range 110-120 V<sub>rms</sub>).
- Power is average power, not instantaneous power (e.g., a 100 W light bulb uses 100 W of average power).

For sinusoidal voltages and currents,

$$V_{rms} = \sqrt{\int_0^T V_m^2 \cos^2(\omega t + \theta) dt}$$

This can be used to show that

$V_{rms} = \frac{V_m}{\sqrt{2}}$	SINUSOIDAL RMS VOLTAGE
----------------------------------	---------------------------

If the voltage in your home is  $V_{rms} = 120$  V<sub>rms</sub>, then

$$v(t) = 120\sqrt{2} \cos(\omega t + \theta) \text{ V, where } \omega = 2\pi f$$

$$= 2\pi \times 60$$

$$v(t) = 169.7 \cos(120\pi t + \theta) \text{ V.}$$

Example: Let  $v(t) = 10 \sin(1000\pi t + 30^\circ)$

Express this as a cosine, give angular frequency, frequency in Hz, and average power in a  $10\Omega$  resistor.

$$\begin{aligned} \text{We have } v(t) &= 10 \sin(1000\pi t + 30^\circ) \\ &= 10 \cos(1000\pi t + 30^\circ - 90^\circ) \end{aligned}$$

Angular frequency

$$\omega = 1000\pi \text{ radians/sec}$$

$$f = \omega / 2\pi = 500 \text{ Hz}$$

$$\text{And } V_{rms} = \frac{V_m}{\sqrt{2}} = 7.071 \text{ V.}$$

$$\text{and average power } P_{avg} = \frac{V_{rms}^2}{R} = \frac{(7.071)^2}{10} = 5 \text{ W}$$


Let's also sketch the instantaneous power  $p(t)$

$$p(t) = \frac{V^2(t)}{R} = \frac{100}{10} \cos^2(1000\pi t - 60^\circ)$$

Using the identity  $\cos^2(x) = \frac{1}{2} [1 + \cos(2x)]$

$$p(t) = 5 + 5 \cos(2000\pi t - 120^\circ)$$

↖ makes the average 5!

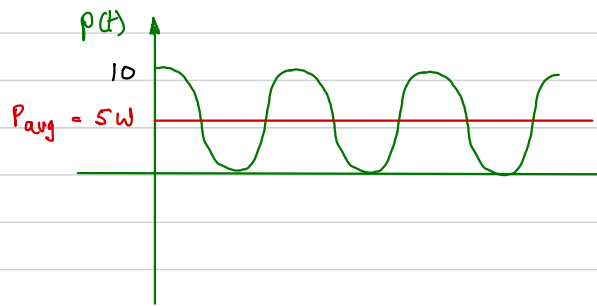

Phasors

For sinusoidal voltages and currents, we need a convenient way to add them to satisfy KVL, KCL.


Consider a simple loop:

and assume that:

$$V_1(t) = 10 \cos(\omega t)$$

$$V_2(t) = 5 \cos(\omega t - 30^\circ)$$

$$V_3(t) = 5 \cos(\omega t + 90^\circ)$$

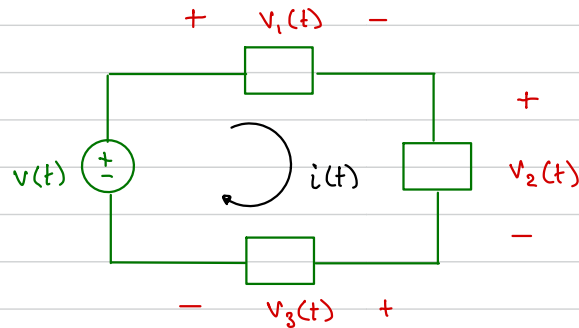

We wish to find  $v(t)$  in the form  $v(t) = V_m \cos(\omega t + \theta)$

KVL must be satisfied by this circuit over all time.

$$-v(t) + V_1(t) + V_2(t) + V_3(t) = 0$$

$$\text{So } v(t) = 10 \cos(\omega t) + 5 \cos(\omega t - 30^\circ) + 5 \cos(\omega t + 90^\circ)$$

How do we manipulate this to get the desired form  $V_m \cos(\omega t + \theta)$ ?

What will  $V_m$  and  $\theta$  be?

For this, we instead express voltages and currents in terms of phasors.

$$\text{Let } V_1(t) = V_1 \cos(\omega t + \theta_1)$$

$\omega$  is usually fixed in value throughout the circuit and is ignored in phasor notation.

We have a pair of parameters that describe this voltage:

$V_1$  — magnitude (i.e., peak value, or amplitude)

$\theta_1$  — phase angle

Basic idea — Represent as a vector on a plane; then add as vectors.

## Examples of phasor notation

Voltage

$$v_a(t) = V_a \cos(\omega t + \theta_a)$$

$$\begin{aligned} V_b(t) &= V_b \sin(\omega t + \theta_b) \\ &= V_b \cos(\omega t + \theta_b - 90^\circ) \end{aligned}$$

phasor notation

$$\bar{V}_a = \underbrace{V_a}_{\text{magnitude}} \angle \underbrace{\theta_a}_{\text{phase angle}}$$

$$\bar{V}_b = V_b \angle \theta_b - 90^\circ$$

Similarly, for currents:

$$i_c(t) = I_c \cos(\omega t + \theta_c) \longleftrightarrow \bar{I}_c = I_c \angle \theta_c$$

To manipulate phasors, we will need to use complex numbers.

## Complex numbers - review

We express and manipulate phasors as complex numbers. Complex numbers involve "imaginary" numbers:


Mathematicians :  $i = \sqrt{-1}$

Engineers :  $i$  is current, so  $j = \sqrt{-1}$   
or  $j^2 = -1$

E.g., complex number:  $x = 2 + j4$

real part

imaginary part

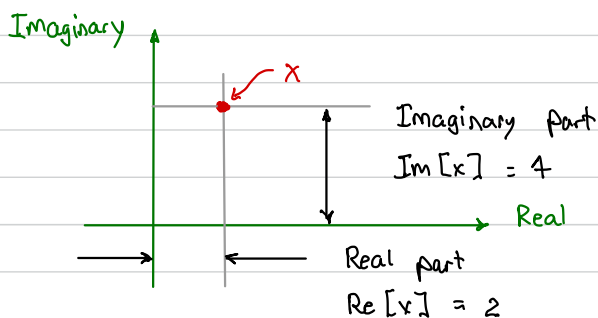

$x$  is a point in the complex plane

denotes complex conjugate

The complex conjugate of  $x$  is :


$$x^* = 2 - j4$$

flip the sign of  $\text{Im}[x]$

Rectangular and polar forms of complex numbers:

$$x = a + jb$$

$$x = M / \theta$$

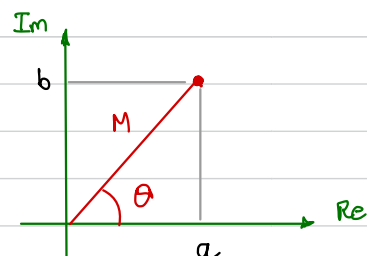

Conversion between forms:

Polar M

$$M = \sqrt{a^2 + b^2}$$

$$\theta = \tan^{-1}(b/a)$$

$$= \arctan(b/a)$$

Rectangular a + jb

$$a = M \cos \theta$$

$$b = M \sin \theta$$

Complex arithmetic

$$\text{Let } x = 2 + j4 \quad \text{and} \quad y = 4 + j5$$

- Addition and subtraction must be done in rectangular form:

$$x + y = (2 + j4) + (4 + j5) = 6 + j9$$

$$x - y = (2 + j4) - (4 + j5) = -2 - j$$

- Multiplication and division can be done in either form

Rectangular:

$$\begin{aligned} x \cdot y &= (2 + j4)(4 + j5) \\ &= 8 + j10 + j16 + \textcircled{j^2} 20 \quad j^2 = -1 \\ &= -12 + j26 \end{aligned}$$

$$x/y = \frac{2 + j4}{4 + j5} = \left( \frac{2 + j4}{4 + j5} \right) \left( \frac{4 - j5}{4 - j5} \right)$$

$$= \frac{8 - j10 + j16 - j^2 20}{16 - j20 + j20 - j^2 25} = \frac{28 + j6}{41}$$

$$= \frac{28}{41} + j \frac{6}{41}$$

· Polar: First convert x and y to polar

$$x = \sqrt{2^2 + 4^2} \angle \tan^{-1}(4/2) = \sqrt{20} \angle 63.44^\circ$$

$$y = \sqrt{4^2 + 5^2} \angle \tan^{-1}(5/4) = \sqrt{41} \angle 51.34^\circ$$

$$\text{Then: } x \cdot y = (\sqrt{20})(\sqrt{41}) \angle 63.44^\circ + 51.34^\circ$$

MULTIPLY MAGNITUDES,  
ADD ANGLES

$$x/y = (\sqrt{20})/(\sqrt{41}) \angle 63.44^\circ - 51.34^\circ$$

DIVIDE MAGNITUDES,  
SUBTRACT ANGLES



Phasors and Euler's identity

Key to the functioning of phasors is Euler's identity

$$e^{j\theta} = \cos \theta + j \sin \theta$$

Multiply both sides by  $M$

$$\underbrace{M e^{j\theta}}_{\substack{\text{complex exponential,} \\ \text{another way of expressing} \\ M/\theta}} = \underbrace{M \cos \theta + j M \sin \theta}_{\text{rectangular form}}$$

e.g.,  $x = 10e^{j30^\circ} = 10\angle 30^\circ$

Using Euler's identity,

$$x = 10e^{j30^\circ} = 10 \cos(30^\circ) + j 10 \sin(30^\circ)$$

$$\begin{aligned} \text{and where } \operatorname{Re}[x] &= \operatorname{Re}[10e^{j30^\circ}] = 10 \cos(30^\circ) = 8.66 \\ \operatorname{Im}[x] &= \operatorname{Im}[10e^{j30^\circ}] = 10 \sin(30^\circ) = 5 \end{aligned}$$

$$\text{So } 10e^{j30^\circ} = 8.66 + j5$$

Writing KVL/KCL equations using phasors

The key step: Express cosines as complex exponentials using Euler's identity.

$$\cos(x) = \operatorname{Re}[e^{jx}]$$

Finally, back to our original KVL example

$$v(t) = 10 \cos(\omega t) + 5 \cos(\omega t - 30^\circ) + 5 \cos(\omega t + 90^\circ)$$

Express each term as a complex exponential.

$$\begin{aligned}v_1(t) &= 10 \cos(\omega t) = \operatorname{Re}[10e^{j\omega t}] \\v_2(t) &= 5 \cos(\omega t - 30^\circ) = \operatorname{Re}[5e^{j(\omega t - 30^\circ)}] \\v_3(t) &= 5 \cos(\omega t + 90^\circ) = \operatorname{Re}[5e^{j(\omega t + 90^\circ)}]\end{aligned}$$

$$\text{so } v(t) = \operatorname{Re}[10e^{j\omega t}] + \operatorname{Re}[5e^{j(\omega t - 30^\circ)}] + \operatorname{Re}[5e^{j(\omega t + 90^\circ)}]$$

The sum of the real parts is equal to the real part of the sum.

$$\begin{aligned}v(t) &= \operatorname{Re}[10e^{j\omega t} + 5e^{j\omega t}e^{-j30^\circ} + 5e^{j\omega t}e^{j90^\circ}] \\&= \operatorname{Re}[\underbrace{(10 + 5e^{-j30^\circ} + 5e^{j90^\circ})}_{\text{addition of three complex constants (i.e., phasors)!}} e^{j\omega t}] \quad (1)\end{aligned}$$

factor out

Complex addition:

$$\begin{aligned}10 &= 10 + j0 \\5e^{-j30^\circ} &= 5\cos(-30^\circ) + j5\sin(-30^\circ) = 4.33 - j2.5 \\5e^{j90^\circ} &= 5\cos(90^\circ) + j5\sin(90^\circ) = 0 + j5\end{aligned}$$

$$\text{so } (10 + j0) + (4.33 - j2.5) + (0 + j5) = 14.33 + j2.5$$

$$\begin{aligned}\text{In polar notation: } M &= \sqrt{14.33^2 + 2.5^2} = 14.54 \\ \theta &= \tan^{-1}(2.5/14.33) = 9.90^\circ\end{aligned}$$

Finally, equation (1) simplifies to

$$\begin{aligned}v(t) &= \operatorname{Re}[(14.54 \angle 9.90^\circ) e^{j\omega t}] = \operatorname{Re}[14.54 e^{j9.90^\circ} e^{j\omega t}] \\&= \operatorname{Re}[14.54 e^{j(\omega t + 9.90^\circ)}]\end{aligned}$$

The final step using Euler's identity:  $\operatorname{Re}[e^{jx}] = \cos(x)$

$$v(t) = 14.54 \cos(\omega t + 9.90^\circ)$$

"TIME-DOMAIN"  
EXPRESSION

Summary of phasor-domain calculation method

1. Express cosine functions as phasors

$$\begin{aligned}\bar{V}_1 &= 10 \cos(\omega t) = 10 \angle 0^\circ = 10 + j0 \\ \bar{V}_2 &= 5 \cos(\omega t - 30^\circ) = 5 \angle -30^\circ = 4.33 - j2.5 \\ \bar{V}_3 &= 5 \cos(\omega t + 90^\circ) = 5 \angle 90^\circ = 0 + j5\end{aligned}$$


2. Use these phasors in the KVL equation

$$\begin{aligned}\bar{V} &= \bar{V}_1 + \bar{V}_2 + \bar{V}_3 = 14.33 + j2.5 \\ &= 14.54 \angle 9.90^\circ\end{aligned}$$

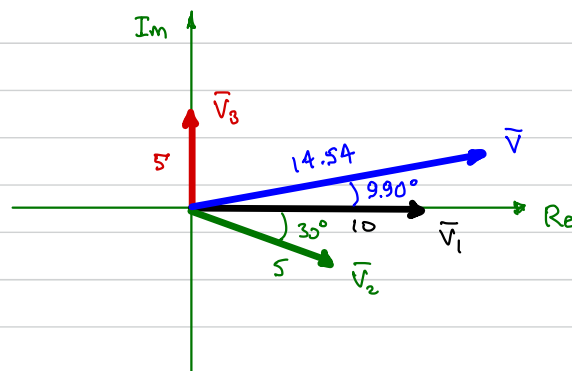3. If required, convert your combined phasor back into the time domain as a cosine function-

$$v(t) = 14.54 \cos(\omega t + 9.90^\circ)$$

A phasor diagram is often used to represent the sinusoidal components.



PHASOR  
DIAGRAM