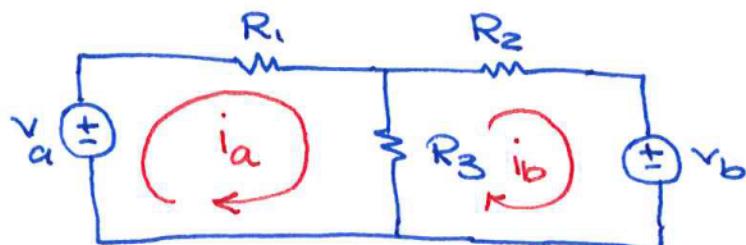



## The Mesh Current Method

- Another useful, systematic method for circuit analysis



$i_a$  &  $i_b$  : mesh currents  
 imagined currents  
 circulating in a closed  
 loop or mesh.

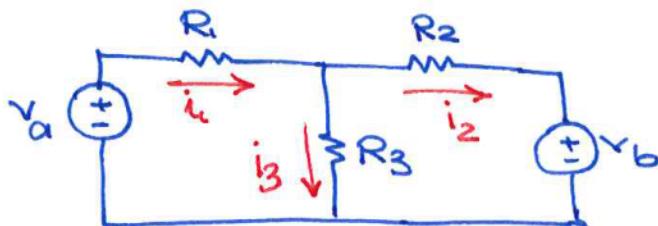
- Mesh currents are different from branch currents:
  - we use branch currents to write KCL
  - Branch currents can be measured with an ammeter
  - Branch current is used in Ohm's Law.



branch currents

$$i_1 = i_2 + i_3$$
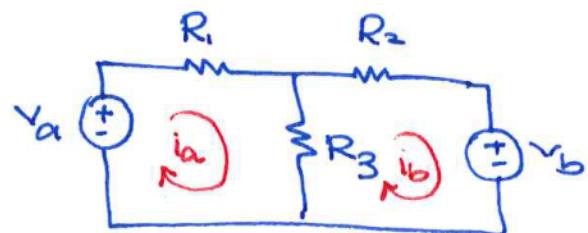
$$\begin{aligned} i_1 &= i_a \\ i_2 &= i_b \\ i_3 &= i_a - i_b \end{aligned}$$




mesh currents

3 main steps:

- 1) Identify meshes & any known mesh currents
- 2) Write a mesh equation (KVL) for each mesh; Develop a system of equations. Only unknowns should be mesh currents.
- 3) Solve for mesh currents
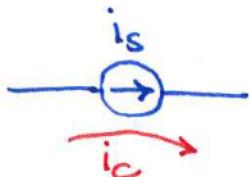
## Step 1 : Identify Meshes

- Imagine a circuit as a window pane; Assign a mesh current to each pane.
- Assumed mesh directions arbitrarily.
- Usually, mesh current method is easier (more systematic) if all meshes have the same direction
- Note the current source in the upper mesh:



$i_c$  labelled with the same direction as  $i_s$  :  $i_c = i_s$

i.e.  $i_c$  is known immediately


## Step 2 : Form mesh equations

- Labelling the circuit:


Include a polarity on each resistor inside each mesh.


Assume voltage drop in direction of mesh current

- Consider  $R_1$ :

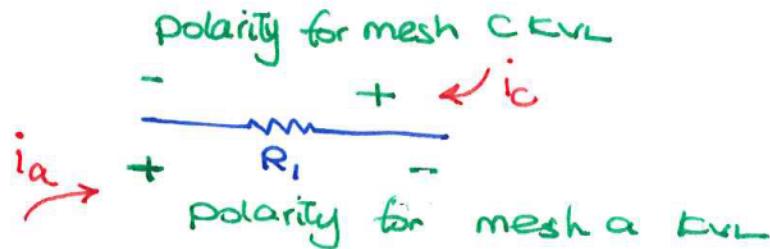

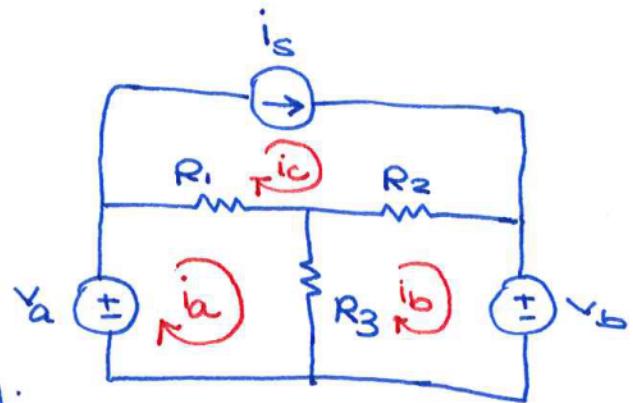- When writing KVL for mesh a: we need to determine branch currents in terms of mesh currents to find voltages across resistors:



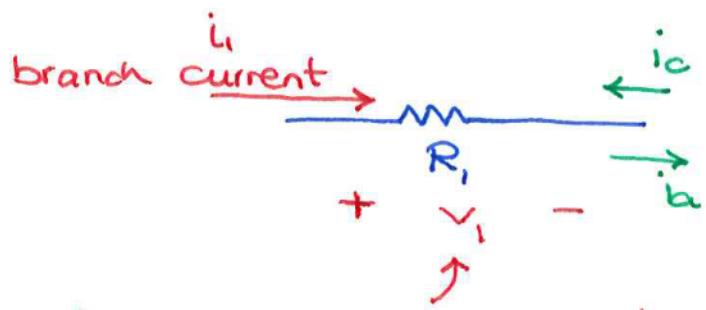

voltage across  $R_1$  due to branch current  $i_1$

choose  $i_1$  in the same direction as  $i_a$   $\therefore i_1 = i_a - i_c$

From Ohm's Law:  $V_1 = i_1 \cdot R_1 = (i_a - i_c) \cdot R_1$

Now, sum voltages around mesh a (clockwise direction;  
same as  $i_a$ )

$$-V_a + (i_a - i_c) R_1 + (i_a - i_b) R_3 = 0 \quad (i)$$


saw (-) terminal first

Similarly, for mesh b:

$$(i_b - i_a) R_3 + (i_b - i_c) R_2 + V_b = 0 \quad (ii)$$

Step 3: Solve 2 equations (i) & (ii) to find 2 unknowns  
 $i_a$  &  $i_b$

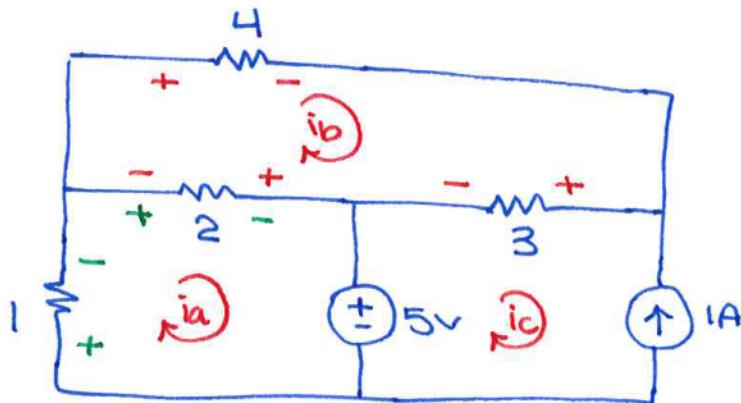Ex: Find power in 3Ω resistor using mesh current



We know that  $i_c = -1\text{A}$

Two unknowns  $i_a$  &  $i_b$

- Avoid mesh eq at c  
since we don't know the voltage across the 1A source

- Once all mesh currents are calculated, we can write KVL around mesh c to find voltage across 1A source

KVL around mesh a : 2 mesh currents in opposite direction

$$\underbrace{i_a \times 1}_{\text{only one mesh current through in resistor}} + 2(i_a - i_b) + 5 = 0$$

only one mesh current through in resistor

$$\therefore 3i_a - 2i_b = -5 \quad (\text{i})$$

KVL around mesh b : (use polarities labelled in red)

$$4i_b + 3(i_b - i_c) + 2(i_b - i_a) = 0$$


$$\therefore -2i_a + 9i_b = -3 \quad (\text{ii})$$

Solving (i) and (ii) gives  $i_a = -2.217 \text{ A}$ ,  $i_b = -0.826 \text{ A}$

To find power in  $3\Omega$  resistor :

- assumed direction for branch current
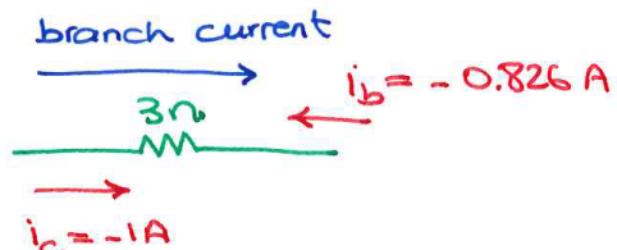
$$\begin{aligned} \text{branch current} &= i_c - i_b \\ &= -1 - (-0.826) \\ &= -0.174 \text{ A} \end{aligned}$$




$$P = i^2 R = (-0.174)^2 \times 3 = 0.09 \text{ W}$$

Ex (Dep. Source). Solve for mesh currents

Note:  $i_{bc}$  is a branch current

• KVL around mesh a:

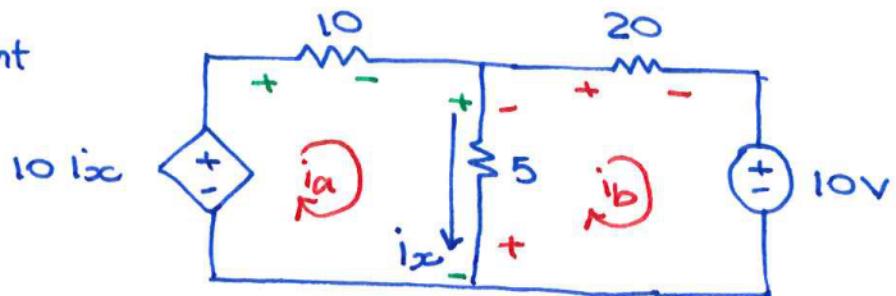

$$-10i_x + 10i_a + 5(i_a - i_b) = 0$$

ignore  $i_x$  when writing this

need to write  $i_x$  in terms of  $i_a$  &  $i_b$   $\therefore i_x = i_a - i_b$

$$\therefore -10(i_a - i_b) + 10i_a + 5(i_a - i_b) = 0$$

$$\therefore i_a = -i_b \quad (\text{i})$$


• KVL around mesh b:

$$5(i_b - i_a) + 20i_b + 10 = 0$$

$$\therefore -5i_a + 25i_b = -10 \quad (\text{ii})$$

• Solving (i) and (ii) gives:  $i_a = \frac{1}{3} \text{ A}$ ,  $i_b = \frac{-1}{3} \text{ A}$

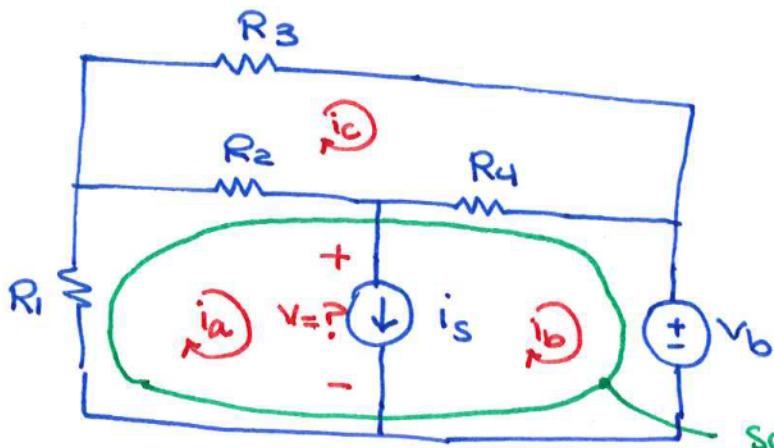Special Case: Circuits with current sources shared by 2 meshes.



- KVL for mesh C: no problem!
- When writing KVL for mesh a & b, we have an unknown voltage across the current source!

supermesh  $i_a \& i_b$

$$\text{Mesh a: } R_1 i_a + R_2 (i_a - i_c) + v = 0$$

$$\text{Mesh b: } R_4 (i_b - i_c) + v_b - v = 0 \quad \text{extra unknown!}$$

adding these 2 eliminates  $v$ :

$$R_1 i_a + R_2 (i_a - i_c) + R_4 (i_b - i_c) + v_b = 0 \quad (\text{i})$$

We can arrive at (i) directly with a supermesh.


i) KVL around Super mesh:

$$\underbrace{R_1 i_a + R_2 (i_a - i_c)}_{\text{mesh a side}} + \underbrace{R_4 (i_b - i_c) + v_b}_{\text{mesh b side}} = 0$$

ii) From inside the supermesh:

$$i_s = i_a - i_b$$

Dependence  
Equation

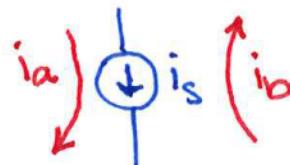


Ex : Find mesh currents

current source (vccs)

Shared by 2 meshes


.. need a supermesh

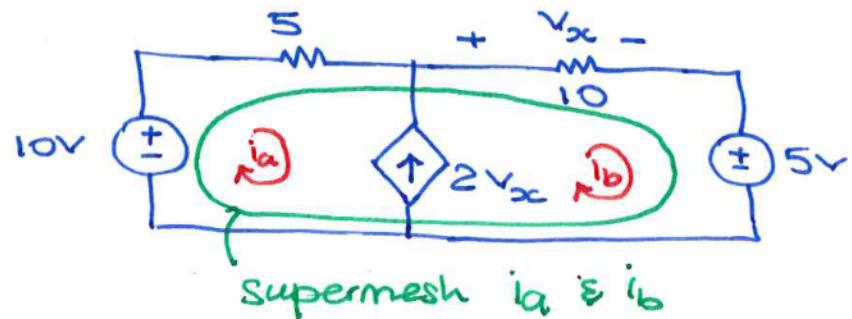

KVL around supermesh :  $-10 + 5i_a + 10i_b + 5 = 0$   
 $\therefore 5i_a + 10i_b = 5 \quad (i)$

Dependence Eq :  $i_b - i_a = 2v_x$

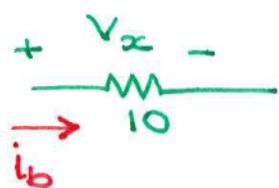Need to write  $v_x$  in terms of mesh current(s) :



From Ohm's Law :  $v_x = 10i_b$


$\therefore i_b - i_a = 2(10i_b) \quad \therefore i_a = -19i_b \quad (ii)$

Solve (i) and (ii) to get  $i_a = 1.12 \text{ A}$  ,  $i_b = -0.058 \text{ A}$

Ex: 2012 MT

a) Find Mesh Currents

b) Find power in 2A current source

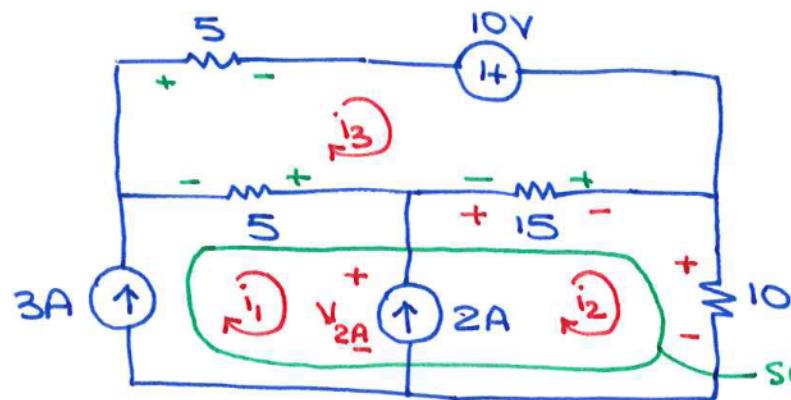

a)  $i_1 = 3 \text{ A}$

2A source shared by  
2 meshes  $\therefore$  supermesh!

supermesh  $i_1, i_2$

Avoid KVL for this supermesh since voltage across 3A source is unknown.

Dependence Eq from super mesh:  $i_2 - i_1 = 2 \quad \therefore i_2 = 5 \text{ A}$

KVL around mesh 3:  $5i_3 - 10 + 15(i_3 - i_2) + 5(i_3 - i_1) = 0$   
 $\therefore i_3 = 4 \text{ A}$

b) Need  $V_{2A}$  to find power. Assumed a polarity for  $V_{2A}$ .


Let's try KVL around mesh 2:

$$-V_{2A} + 15\left(\frac{i_2 - i_3}{5}\right) + 10\frac{i_2}{5} = 0 \quad \therefore V_{2A} = 65 \text{ V}$$


$$P_{2A} = -(V_{2A})(2A) = -65 \times 2 = -130 \text{ W}$$

↑  
supplies 130 W

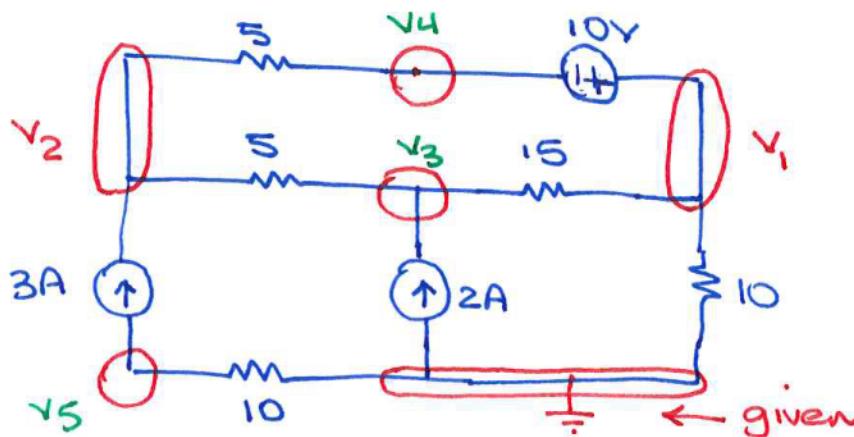Ex: Using the mesh currents in prev ex, find node voltages  $V_1$  &  $V_2$ .




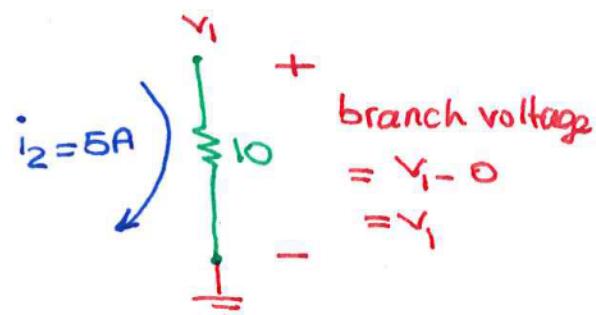Let's use the  $10\Omega$  resistor to find  $V_1$ :



$$\text{from Ohm's Law : } V_1 = 5 \times 10 = 50 \text{ V}$$

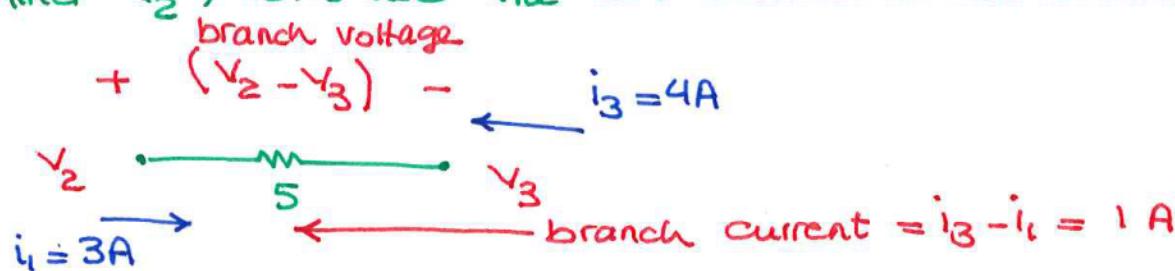
To find  $V_2$ , let's use the  $5\Omega$  resistor in the middle:



$$\text{Ohm's Law : } \frac{\text{branch Voltage}}{\text{across } R} = - \frac{\text{branch current}}{\text{thru } R} \times R$$

$$\therefore V_2 - V_3 = -1 \times 5 \\ = -5$$

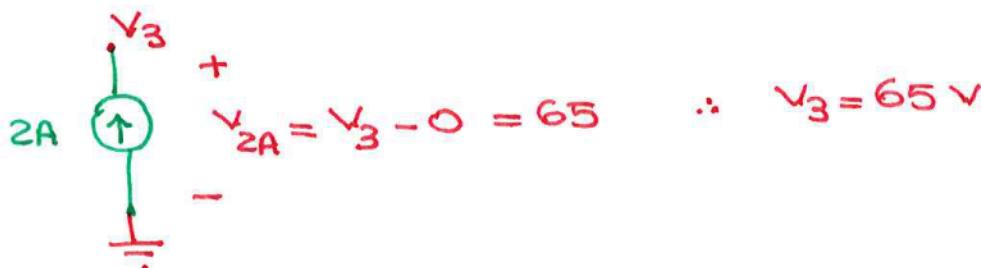but we know the voltage across 2A source:



$$\text{Finally, } V_2 - V_3 = -5 \quad \therefore V_2 = 60 \text{ V}$$

## Choosing between node voltage & mesh current methods


- Pick the method with fewer unknowns in a given circuit
- Node voltage: Look for nodes with voltage sources attached. May eliminate unknowns by good choice of ref node.
- Mesh current: Look for meshes where current is fixed in value due to current sources.

## Summary of circuit analysis methods


- So far :
  - 1) Circuit Simplification , KVL, KCL, Ohm's Law
  - 2) Node Voltage
  - 3) Mesh Current
- Coming next: 4) Thevenin Equivalent  
5) Superposition
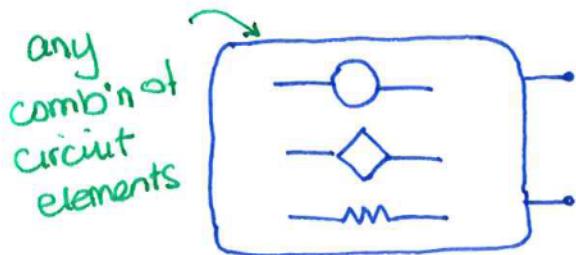
## Thevenin Equivalent Circuits

- Thevenin theorem states: An electric circuit containing voltage sources, current sources, and resistors with two terminals is electronically equivalent to a network with one voltage source and one resistor.
- This gives a way to model complex circuits:




can be modelled as

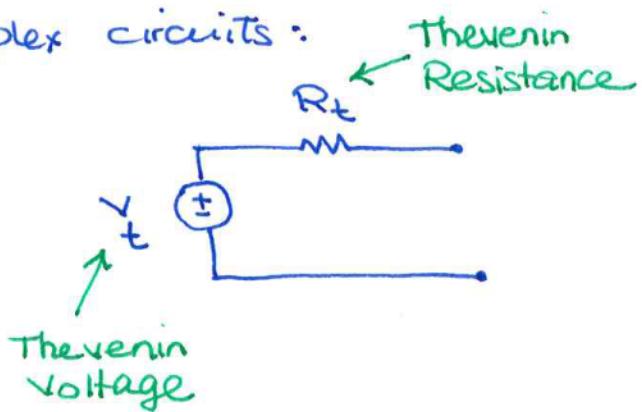

- The voltage-current characteristics are identical at the two terminals.  $v_t$  &  $R_t$  are found by considering operating extremes: open circuit, short circuit

open circuit

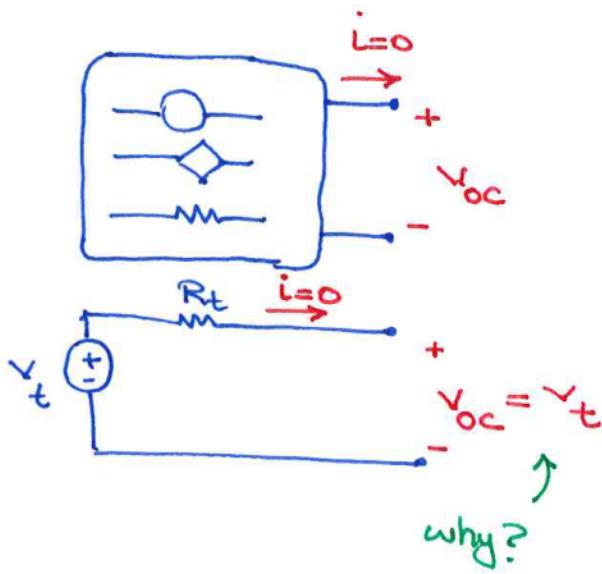


KVL around loop; voltage across  $R = 0$

therefore

$$v_t = v_{oc}$$


short circuit

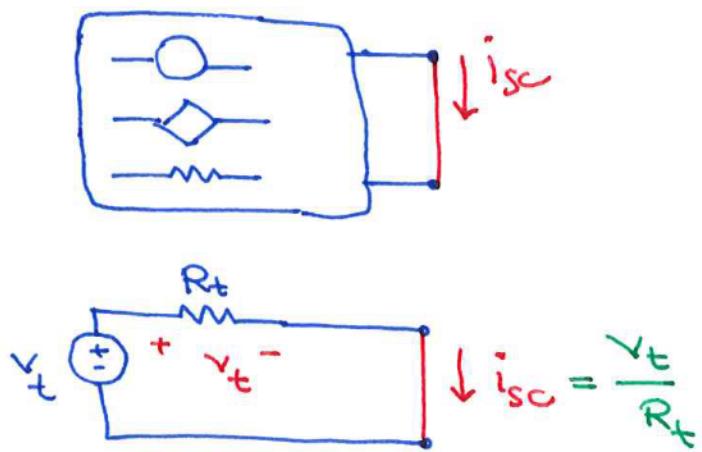

$$R_t = \frac{v_{oc}}{i_{sc}}$$

Later, a short cut for finding  $R_t$  for circuits without dep sources

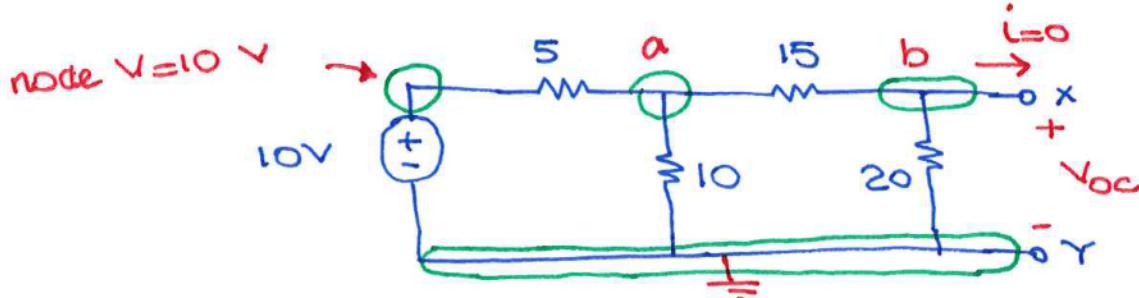Ex: Find thevenin Equivalent of the following circuit as seen from X & Y:



Determining a thevenin Equivalent is two separate analysis problems: Find  $v_{oc}$  & find  $i_{sc}$