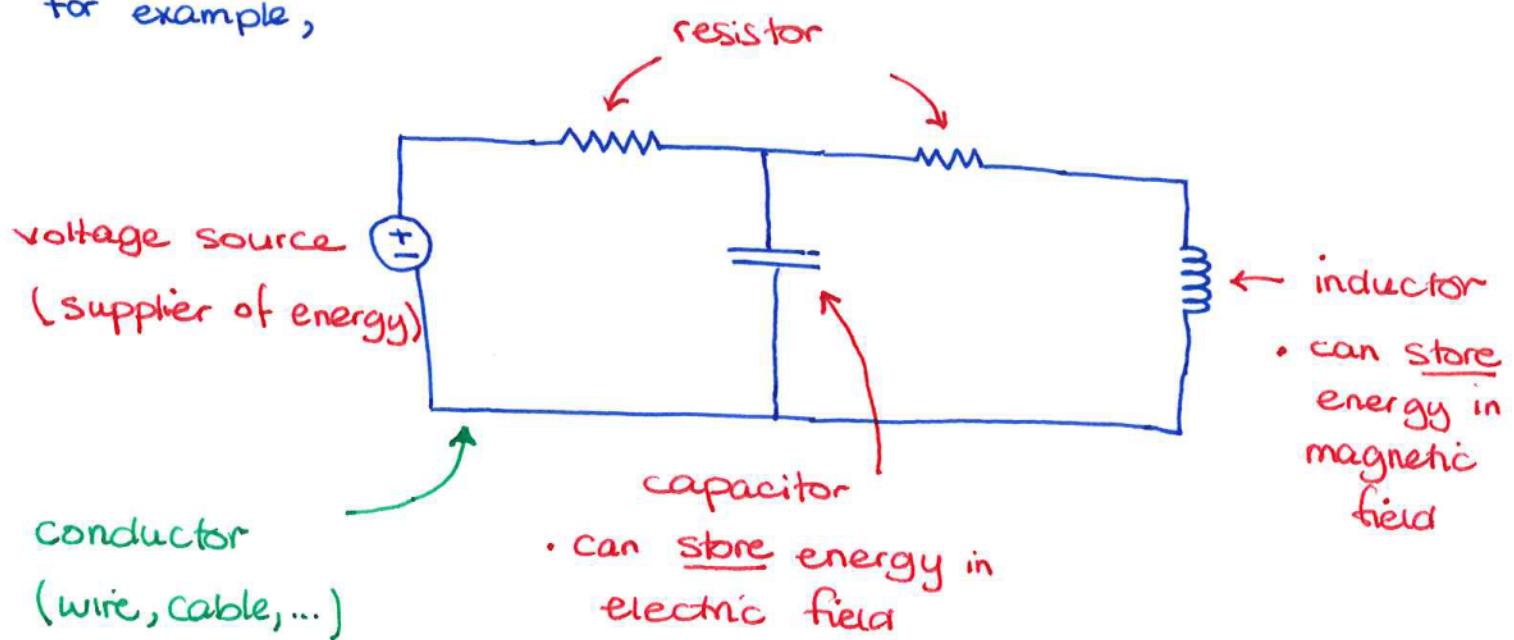


Electric circuit : Interconnection of circuit elements in a closed path by conductors

for example,



- The concept of electrical charge is the basis for describing all electrical phenomena.
 - charge exists in discrete quantities at integer multiples of 1.6×10^{-19} Coulomb (charge of an electron)
- When analyzing electric circuits, there are 2 fundamental electrical quantities : current & voltage

Electric Current : Rate of flow of electrical charge

$$i(t) = \frac{d q(t)}{dt}$$

$i(t)$: current in Amperes (A)

$q(t)$: charge in Coulombs (C)

t : time in seconds

e.g. 1 A = 1 C/S

- Note that $i(t)$ is a measure of equivalent positive charge flow. i.e.


$$i(t) = 2 \text{ A}$$

2 C/s of electrons
or 12.48×10^{18} electrons/sec

- Given $i(t)$, we can also find $q(t)$:

$$q(t) = \int_{t_0}^t i(t) dt + \underbrace{q(t_0)}_{\text{initial value at } t_0}$$

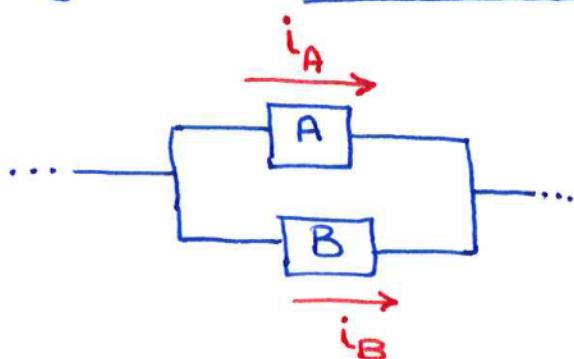- We normally assign reference direction for current:





A, B could be any circuit element:
source, resistor, etc.

- If current direction is not known, you can choose reference direction arbitrarily

Actual direction will be indicated by the sign of i_A, i_B once the circuit is analyzed (solved).



e.g. if we calculate $i_A = -5 \text{ A}$ in the circuit above, then the actual current in A is 5 A right to left.

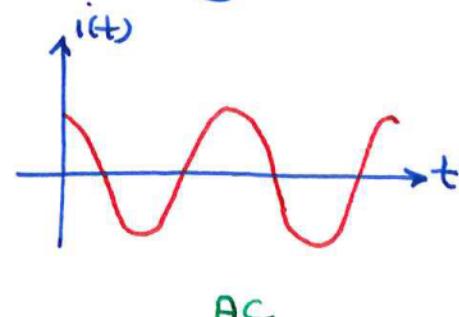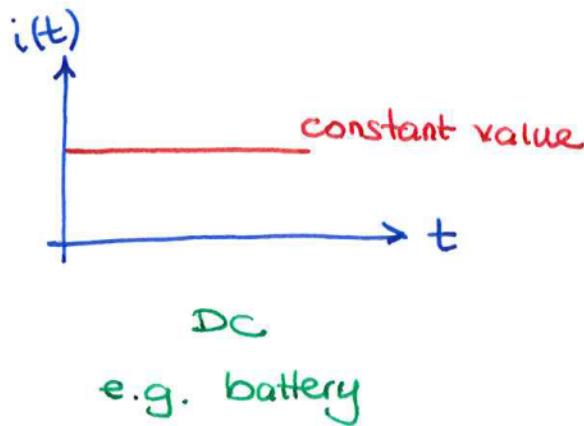We can have Direct Current (DC) & Alternating Current (AC) :



e.g. house outlets

Notation:

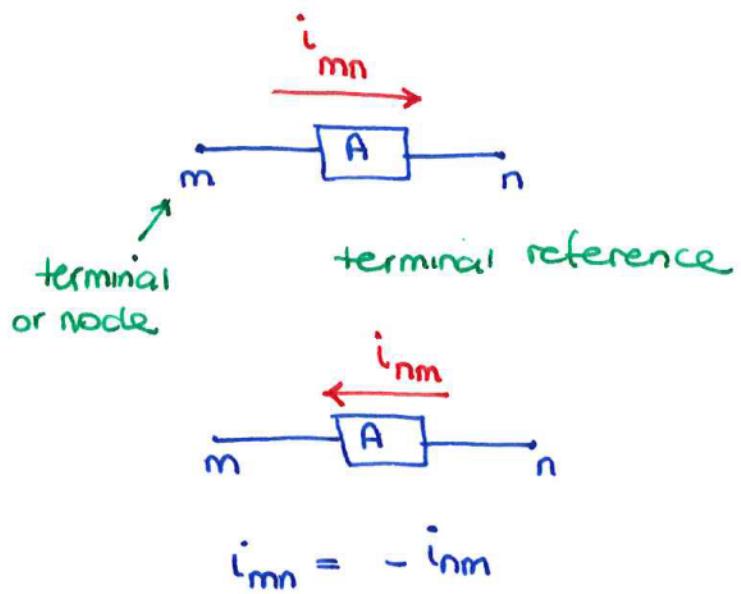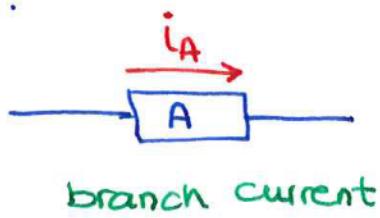

Voltage : Energy transferred to/ from a circuit element per unit of charge flowing through it. Also called potential difference.

$$v(t) = \frac{d w(t)}{d q(t)}$$


$v(t)$: Voltage in Volts (V)

$w(t)$: energy in Joules (J)

$q(t)$: charge in Coulombs (C)


e.g. $1 \text{ V} = 1 \text{ J/C}$

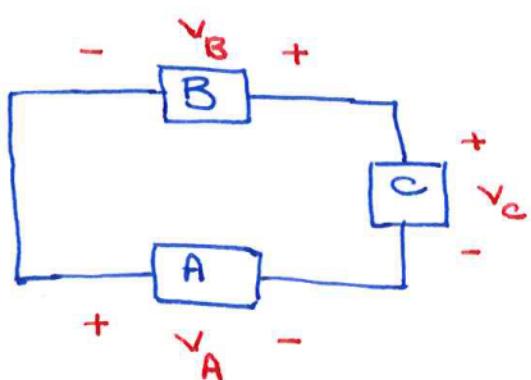- For analysis purposes, we can assign reference polarities (if they are not already given)




- can choose reference polarities arbitrarily
- If actual polarity is opposite, then value of v would be negative

- Common notation:

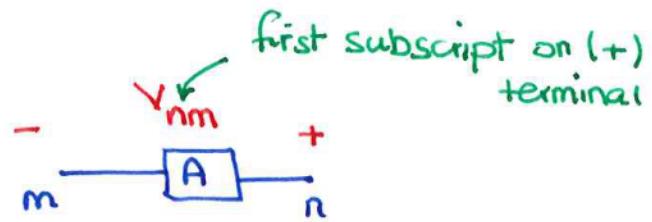


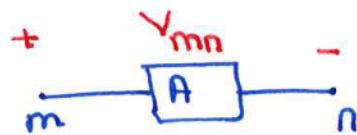- $v_A \in v_{nm}$ will produce the same answer




$$v_{mn} = -v_{nm}$$

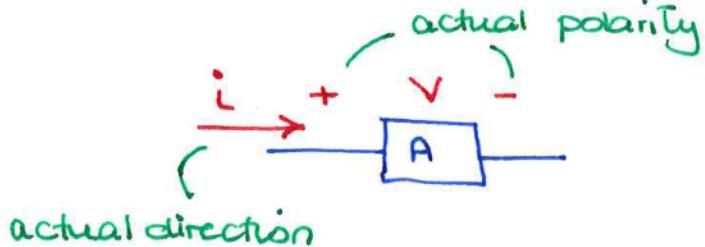- Actual direction of current & actual voltage polarity indicate if an element is absorbing or supplying power:




power absorbed by A

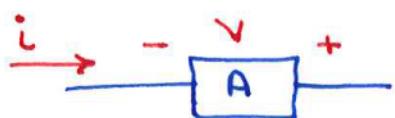

power supplied by A

Yani's cheap plastic circuit example

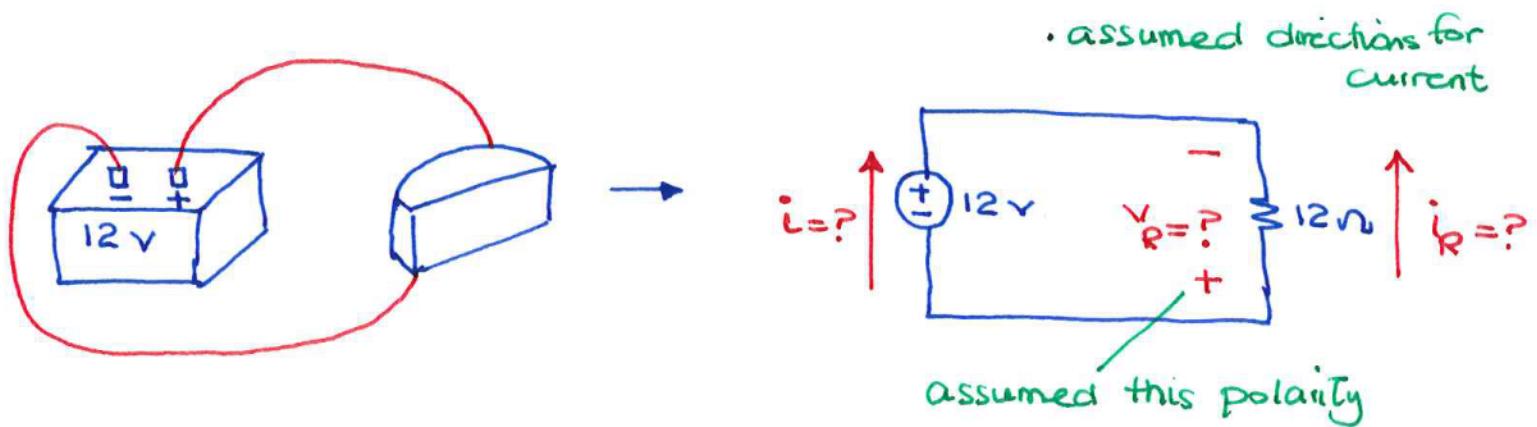Consider the circuit contacting the car battery and the headlights (Note: this is a simplified version of the actual circuit)



What do we know about this circuit (i.e. what is the voltage or current for any individual element)?

What we don't know:


- Voltage across the lights
- Current through the lights
- Current through the battery

We can assume arbitrary directions/polarities for all of the above unknowns.

Why do we care what the voltages/currents are? Reasons can include, but are not limited to, the following:

- Lights require a certain voltage to operate properly. We can solve this circuit to find out if that voltage is provided.
- All the elements in this circuit (battery, light, and conductors) have a certain current rating (maximum amount of current they can handle before they start to overheat/melt/catch fire!) We need to make sure that the current is not exceeding that value.
- Once we know voltage and current for an element, we can calculate the power and energy it consumes/supplies.

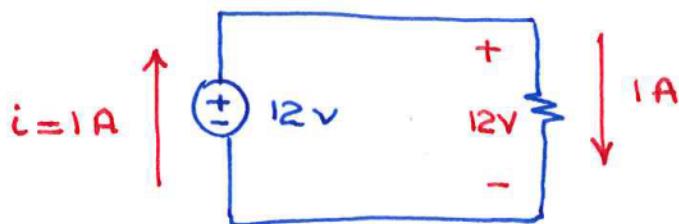After we solve this circuit (we haven't learned how to do that yet!), we will find the actual voltages and currents as follows:




actual current in direction
of voltage drop
 \therefore absorbs power



actual current in direction
of voltage rise
 \therefore supplies power

Ideal Circuit Elements

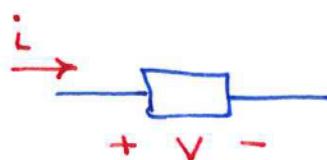- Here we talk about conductors, sources, resistors. Later, we will bring in inductors, capacitors, op amps.
- All circuit elements are characterized by their voltage-current relationships.




Ideal Conductors

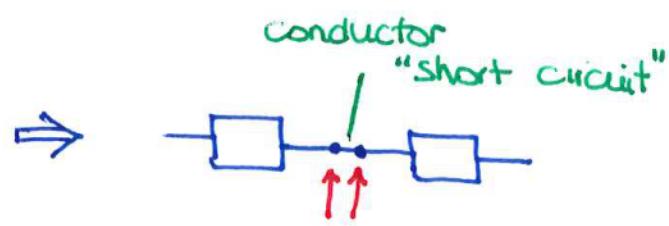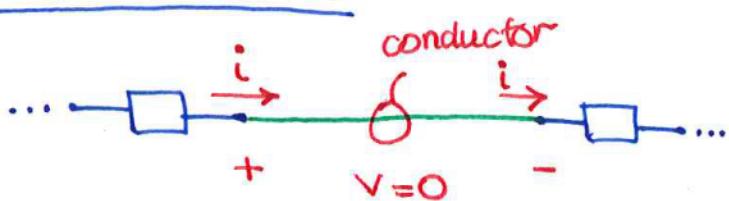

- The absence of a conductor between circuit elements is an open circuit:


open circuit (a gap)

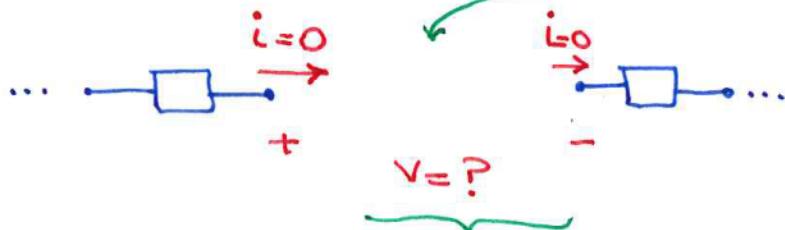


need to solve the circuit to find this

- Since all of our conductors are ideal, we can shorten or lengthen them as much as we like as long as the electrical connection between the circuit elements remain the same.

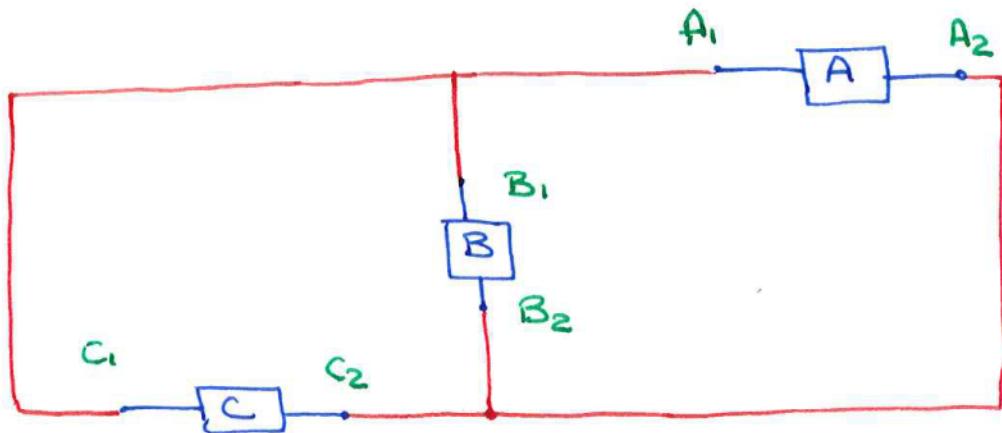For example, consider the following circuit where conductors connect terminals A_1 , B_1 , and C_1 together \Leftrightarrow
conductors connect terminals A_2 , B_2 , and C_2 together




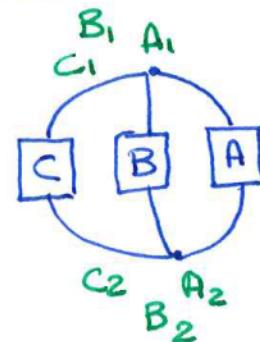this circuit is electrically equivalent to:




Sources:

1) Independent Voltage Source

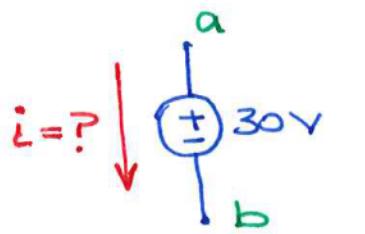

DC source

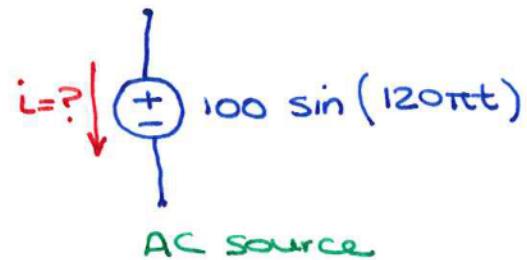terminal a is
higher in potential
than terminal b
by 30V.




Properties:


- Voltage (potential difference) is specified exactly.
- Not affected by any other circuit element.
- Current through the source depends on the circuit it is connected to. Need to solve the circuit to find this out.

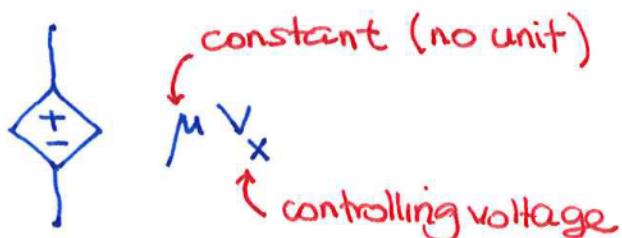2) Dependent Voltage Source

- Have the same properties as independent voltage sources except the value of voltage depends on either a voltage or current elsewhere in the circuit:




voltage-controlled voltage source
(VCVS)

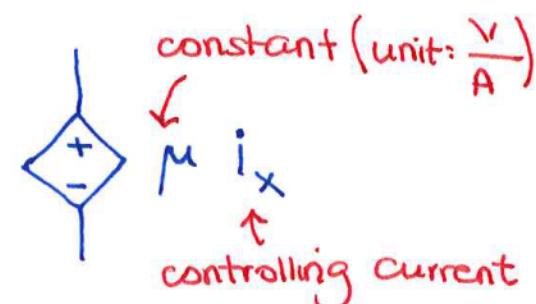


current-controlled voltage src.
(CCVS)

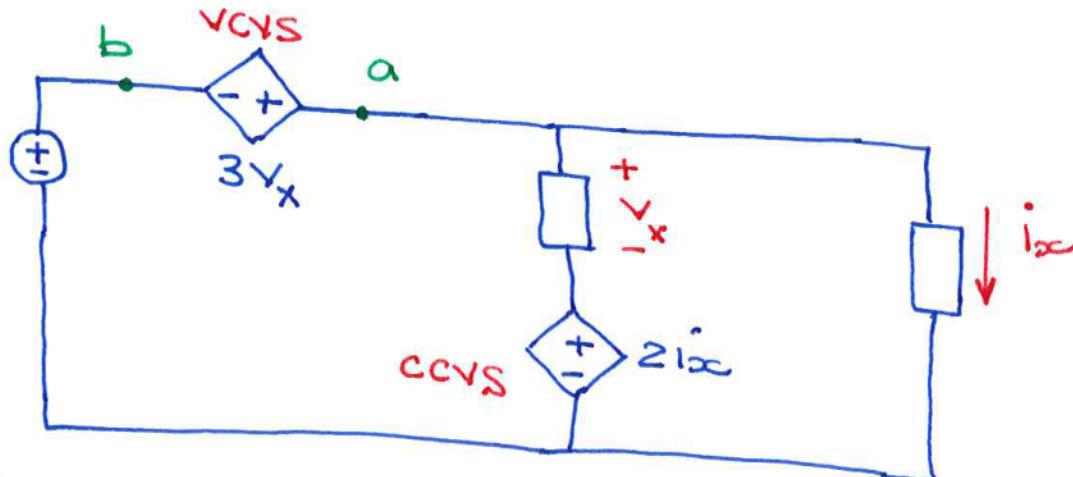
- These can be AC or DC.
- Ex: A circuit using dependent voltage sources:




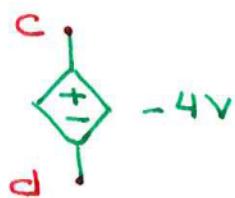
- If we calculate $V_x = 2 \text{ V}$, then VCVS is a 6V source. Point 'a' is higher in potential than point 'b' by 6V. Need to solve the circuit to find current through VCVS.
- If we calculate $i_x = -2 \text{ A}$, then CCVS is -4V:



which is the same as

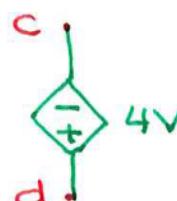



3) Independent Current Source

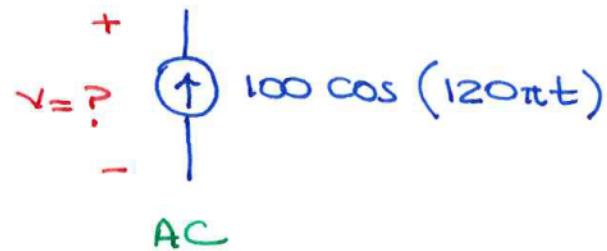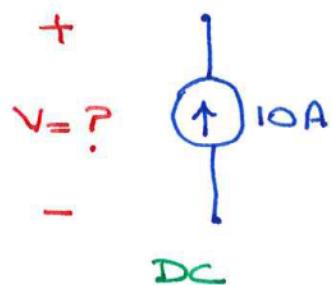

- Properties:
- Current specified explicitly. Not affected by other circuit elements.
 - Voltage across the source depends on the circuit it is connected to. Solve the circuit to find out.

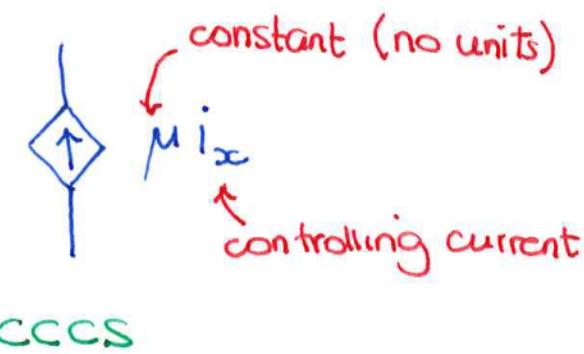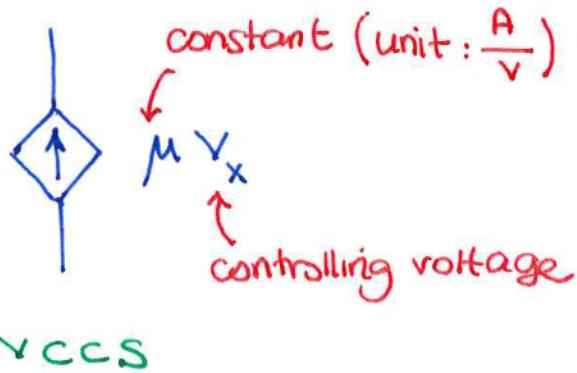4) Dependent Current Source

- . Same properties as independent CS, except current depends on voltage or current elsewhere.



- . For all dependent sources :

- i_x or V_x are always labelled on the circuit, i.e. You do not need to assume their direction or polarity.
- The given reference polarity or direction for V_x & i_x is not necessarily the actual polarity or direction of voltage or current for the controlling element.