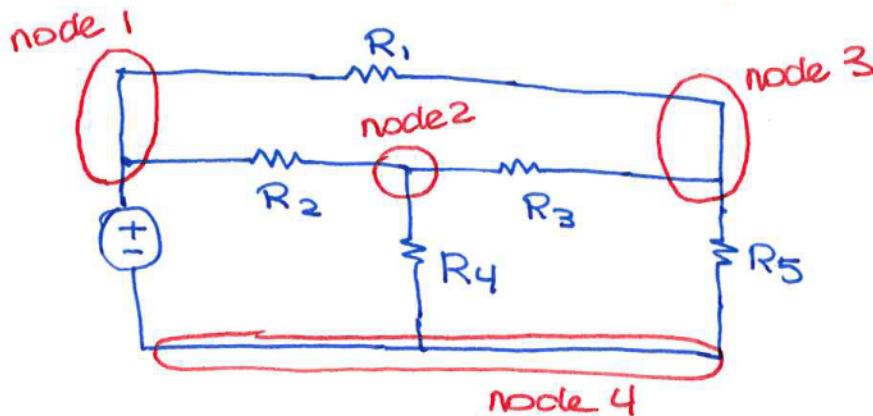


Node Voltage Analysis

- . There are limits to what we can do with series/parallel equivalents and voltage/current division:



Nothing in series
or parallel!

- . The node voltage method allows analysis of any circuit

Steps:

- 1) Identify nodes & known node voltages (if any)
- 2) Apply KCL at nodes; Develop a system of equations.

Unknowns: Node voltages.


- 3) Solve system of equations to determine node voltages.

- . Let's consider our example circuit:

Step 1: Identify nodes

Node Voltage: Potential difference between a node & the reference node.

e.g. v_1, v_2, v_3

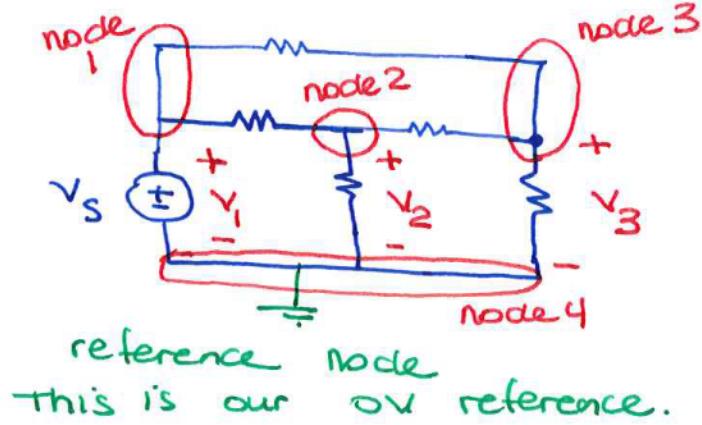

This is our 0V reference.


We can eliminate one unknown node voltage by selecting one end of a voltage source as the reference.

By selecting node 4 as the reference, v_1 automatically becomes $v_1 = v_s$


Step 2: Apply KCL at nodes

- New KCL convention: current leaving the node adds, current entering the node subtracts.
- For resistors, always assume the current is leaving the node of interest

writing equations for resistor currents in terms of node voltages:

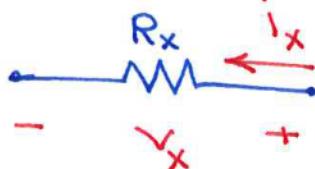- Node voltage vs. branch voltage:
 - So far, we have labelled branch voltages for circuit elements:
$$v_x = i_x \cdot R$$

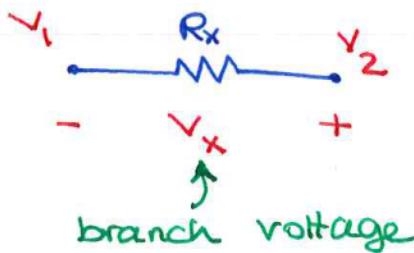- In node voltage method, node voltages are our only variable so we must express v_x and i_x in terms of node voltages:



v_1 & v_2 are node voltages of nodes 1 & 2 on either side of R_x

voltage v_2 is labelled as being at a higher potential than v_1 (v_2 is the + terminal of v_x , v_1 is the - terminal) therefore, the branch voltage v_x is the difference between higher (v_2) and lower (v_1) nodes:

$$v_x = v_2 - v_1$$


branch voltage = node labelled as (+) - node labelled as (-)

therefore, for resistor above :

$$i_x = \frac{v_2 - v_1}{R}$$

current in
terms of
node
voltages

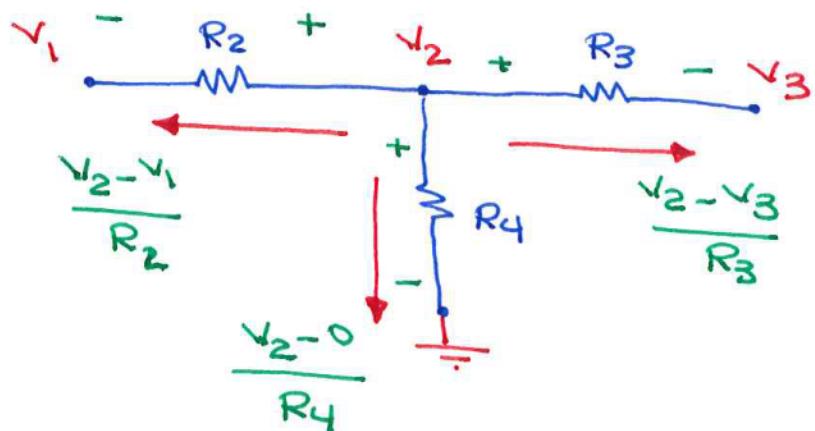Now, consider node 2 in the original circuit:



sum the currents at node 2 by KCL:

$$\frac{v_2 - v_1}{R_2} + \frac{v_2}{R_4} + \frac{v_2 - v_3}{R_3} = 0$$


- In summary, at each node n , calculate the outgoing current to node k through R_m is

$$\frac{v_n - v_k}{R_m}$$


- Now, forget about node 2 and repeat for node 3:

$$\frac{v_3 - v_1}{R_1} + \frac{v_3 - v_2}{R_3} + \frac{v_3}{R_5} = 0$$

Node eq for node 3

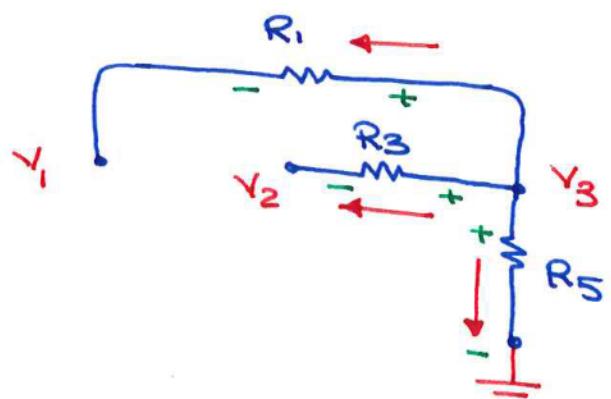

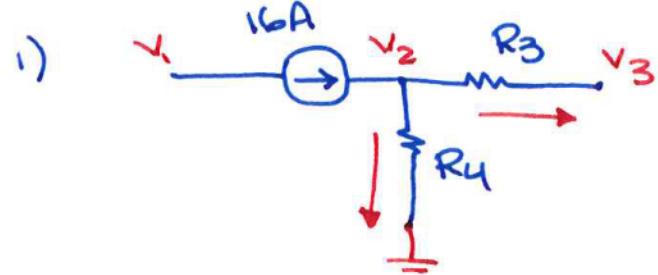Things other than resistors connected to nodes



Node eq at node 2:


node of interest comes first
subtract connecting node

$$\frac{v_2 - v_3}{R_3} + \frac{v_2 - 0}{R_4} - 16 = 0$$

connecting R

a constant
(-) since entering the node.

i.e. current sources are ok!

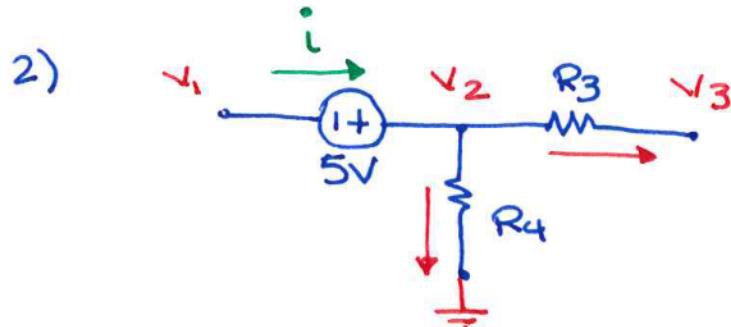

Node eq at 2:

$$\frac{v_2 - v_3}{R_3} + \frac{v_2}{R_4} - i = 0$$

another unknown if we must write an eq
at node 2. (Help is coming!)

.we can't express i in terms of node voltages.

Step 3: Solve Sys of equations

- we now have 2 equations for our example circuit and 2 unknown node voltages v_2 & v_3 .
- $v_1 = v_S$ is already known.

Ex: Find node voltages

Looks like 3 nodes + 1 ref node

We can get v_3 immediately:

$$v_3 = 10 \text{ V}$$

if we select node 4 as the ref node.

(if we select node 3 as the ref node, then $v_4 = -10 \text{ V}$)

KCL at node 1: $\frac{v_1 - v_3}{5} + \frac{v_1 - v_2}{2} - 1 = 0$ (i)

1A into the node \therefore subtract

KCL at node 2: $\frac{v_2 - v_1}{2} + \frac{v_2 - 0}{5} + \frac{v_2 - v_3}{10} = 0$ (ii)

. Don't write KCL at nodes 3 or 4 when solving for node voltages.
because we don't know the current through 10V source.

. can simplify (i) and (ii):

(i) $\times 10$: $2v_1 - 20 + 5v_1 - 5v_2 - 10 = 0$
 $7v_1 - 5v_2 = 30$ (iii)


(ii) $\times 10$: $5v_2 - 5v_1 + 2v_2 + v_2 - 10 = 0$
 $-5v_1 + 8v_2 = 10$ (iv)

Solve (iii) and (iv) with the method of your choosing to

find v_1, v_2 .

e.g.: (iii) $\times 8$: $56v_1 - 40v_2 = 240$
(iv) $\times 5$: $-25v_1 + 40v_2 = 50$
 $\underline{31v_1 = 290}$ $\therefore v_1 = 9.35 \text{ V}$


sub into (iii) to get $v_2 = 7.1 \text{ V}$

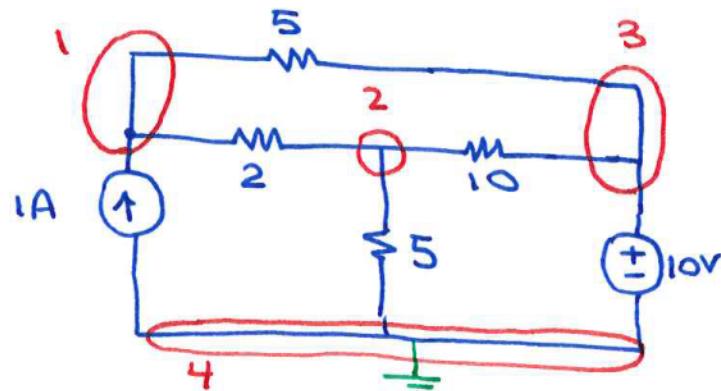

Ex 2 : with dependent current source

with this choice of ref node:

$$V_2 = 10 \text{ V}$$

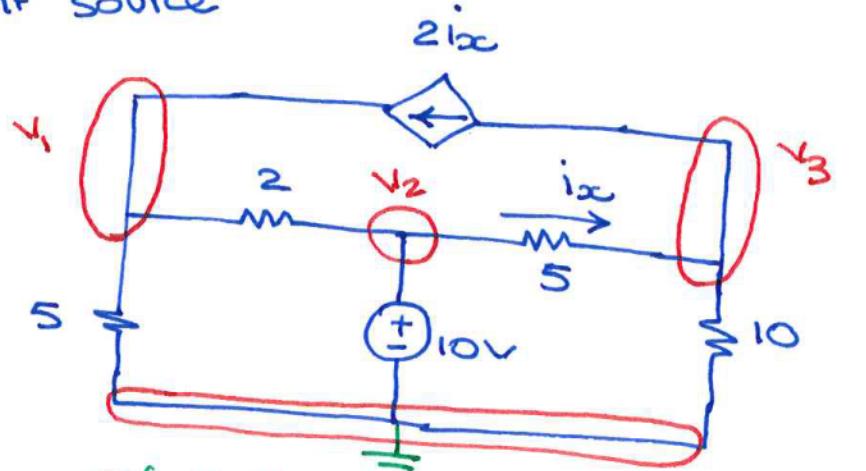

KCL at node 1 :

$$\frac{V_1 - 0}{5} + \frac{V_1 - V_2}{2} - 2i_x = 0 \quad (\text{i})$$

↑ current from dep source going into the node

KCL at node 3 :

$$\frac{V_3 - 0}{10} + \frac{V_3 - V_2}{5} + 2i_x = 0 \quad (\text{ii})$$

voltage at node of interest
voltage of adj. node
connecting R

ignored be when writing this term.

Want to keep eq's in terms of node voltages.

For dependent sources, we always want to write the controlling element in terms of unknowns (node voltages)

In this case, we need to write i_x in terms of node voltages :

$$V_2 \xrightarrow{\frac{1}{5}} V_3 \xrightarrow{i_x} + (V_2 - V_3) -$$

Ohm's Law :

$$i_x = \frac{V_2 - V_3}{5} = \frac{10 - V_3}{5}$$

Plug this into (i) and simplify : $7V_1 + 4V_3 = 90$


also, plug it into (ii) and simplify : $V_3 = 20 \text{ V}$

can now find $V_1 = \frac{10}{7} \text{ V}$



- How do we use node voltages to find voltage & current for individual elements?

Voltages across an element ("branch voltage")

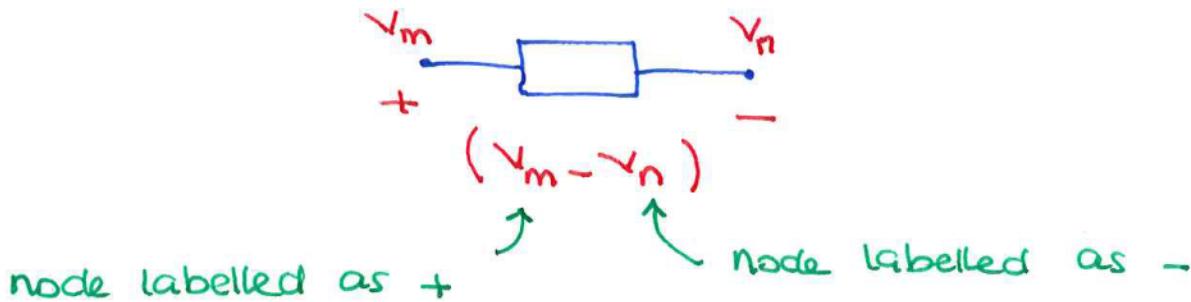- choose a polarity, subtract node voltages accordingly.





- For example, in previous circuit:

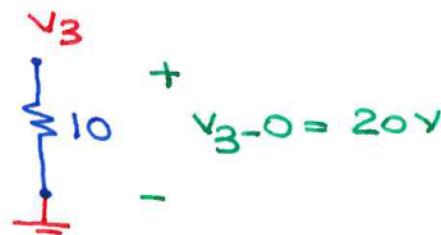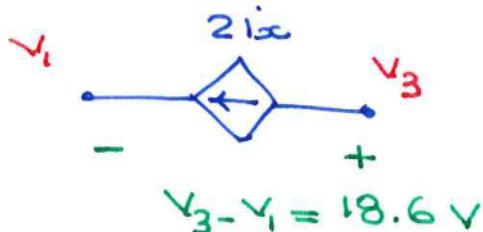

Current through resistors

- Choose a direction, apply Ohm's Law accordingly

For example,

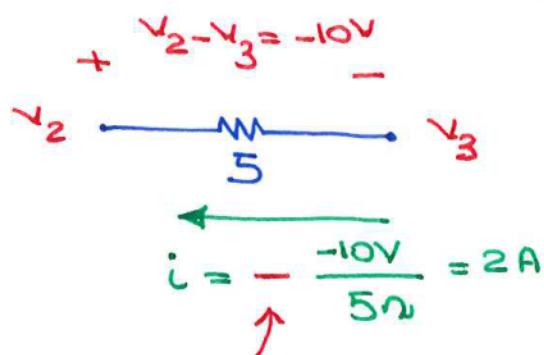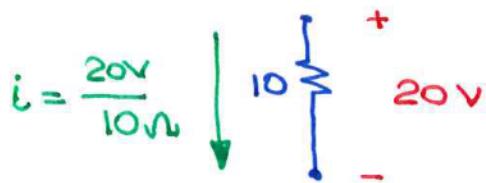


current sees - terminal first

Current through a voltage source

- Use KCL

In our example:

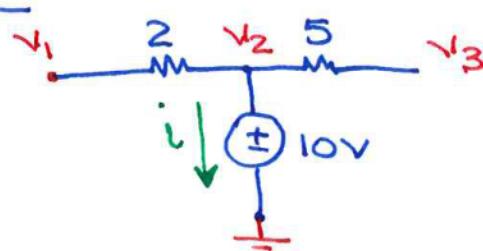
$$\frac{v_2 - v_1}{2} + \frac{v_2 - v_3}{5} + i = 0$$



the only unknown is i . We can solve this to find i through 10V source.

aside:


- From Assignment 2

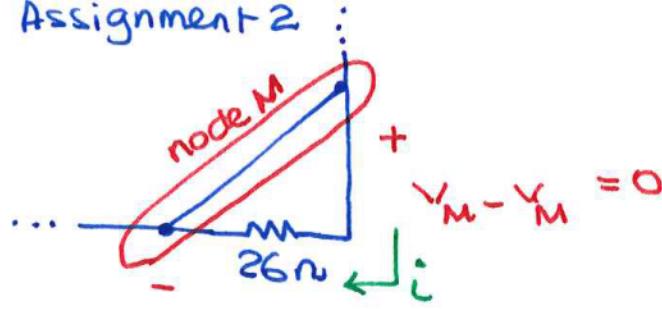

$$i = \frac{V_N - V_M}{0} = 0 \text{ A}$$

26n resistor is connected to the same node at both ends. It is "shorted out" so we can remove it from our analysis

Ex 3: Find node voltages

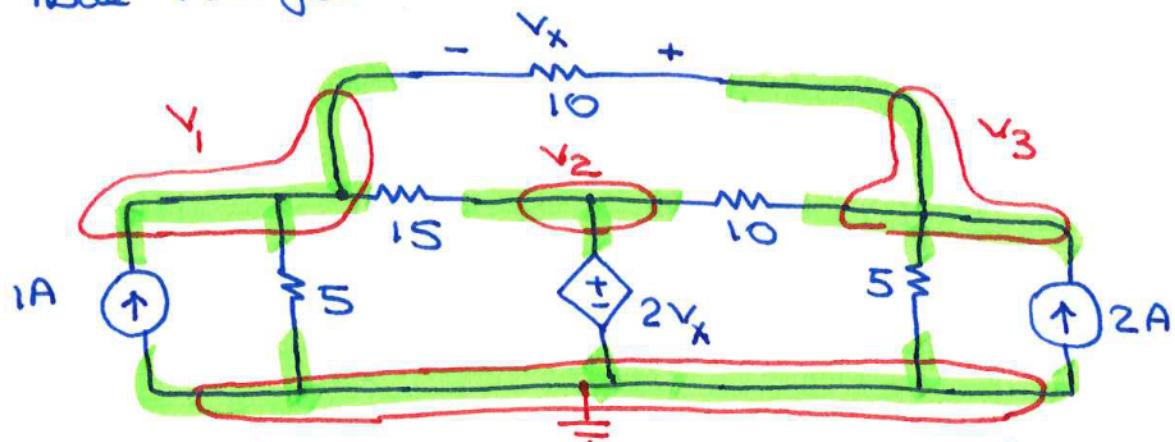

chose one terminal of the voltage source as ref.
Doesn't matter that it's dependent.

Because of ref node; $V_2 = 2V_x$

but we also know :



$$V_x = V_3 - V_1$$

$$\therefore V_2 = 2(V_3 - V_1) \quad (i)$$


$$\text{KCL at node 1: } -1 + \underbrace{\frac{V_1 - V_3}{10}}_{\text{ignored } V_x \text{ when writing this}} + \frac{V_1 - V_2}{15} + \frac{V_1 - 0}{5} = 0 \quad (ii)$$

ignored V_x when writing this

$$\text{KCL at node 3: } -2 + \frac{V_3 - V_1}{10} + \frac{V_3 - V_2}{10} + \frac{V_3 - 0}{5} = 0 \quad (iii)$$

Solve (i), (ii), (iii) to get $V_1 = 5.4\text{ V}$, $V_2 = 3.8\text{ V}$, $V_3 = 7.3\text{ V}$

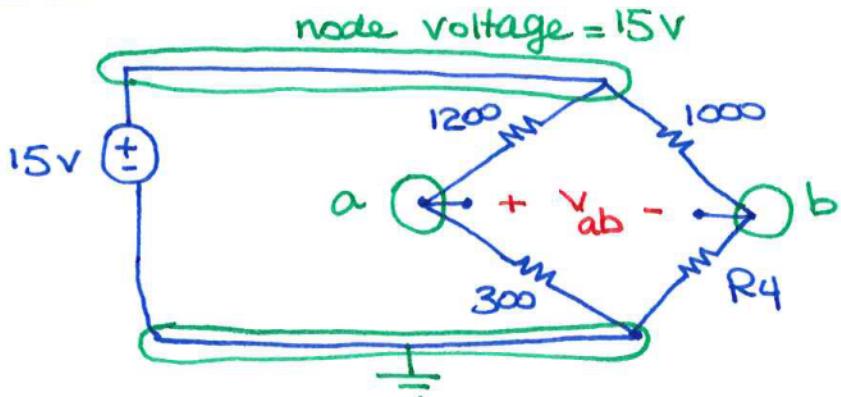Ex: Wheatstone Bridge. Find R_4 such that $V_{ab} = 0$.



Node eq (KCL) at a:

$$\frac{V_a - 15}{1200} + \frac{V_a - 0}{300} = 0$$

$$\therefore V_a = 3 \text{ V}$$

$$\text{For } V_{ab} = 0, V_a = V_b \quad \therefore V_b = 3 \text{ V}$$


$$\text{Node eq at b: } \frac{V_b - 15}{1000} + \frac{V_b - 0}{R_4} = 0 \quad \therefore R_4 = 250 \Omega$$

Node Voltage Method - Special case

- There is only one special case to handle when we have

a voltage source connected between two regular (non-ref) nodes

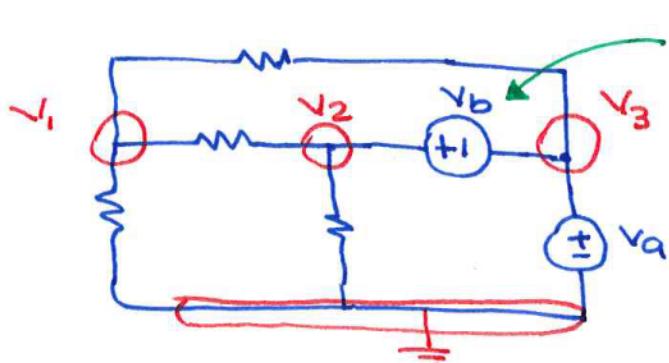- For the easy case where voltage sources are directly connected to other voltage sources:



voltage source between reg nodes

$$V_3 = V_a$$

but we also know that


$$V_2 - V_3 = V_b$$

$$\therefore V_2 = V_3 + V_b = V_a + V_b$$

i.e. V_2 & V_3 are known immediately. Leaves one unknown!

Write KCL at node 1 to find V_1

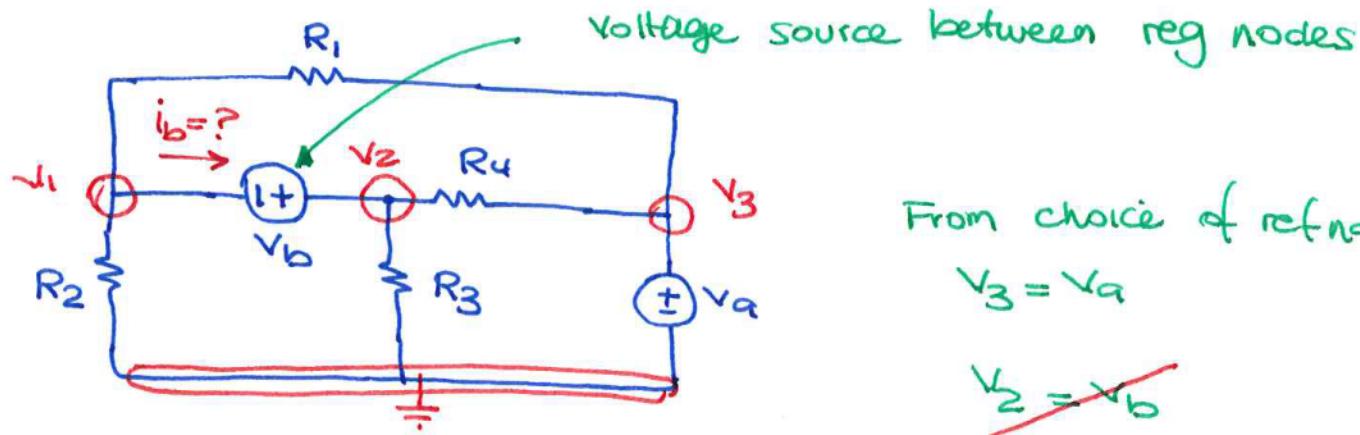In the trickier case, voltage sources are not directly connected to each other:



From choice of ref node:

$$v_3 = v_a$$

$$\cancel{v_2 = v_b}$$

Recall that in writing node equations, we sum currents leaving the nodes.

At node 1: $\frac{v_1 - v_3}{R_1} + \frac{v_1 - 0}{R_2} + \cancel{i_b} = 0$ (i) ↙ another unknown along with v_1, v_2


At node 2: $\frac{v_2 - v_3}{R_4} + \frac{v_2 - 0}{R_3} - \cancel{i_b} = 0$ (ii)

Now, let's eliminate i_b by adding (i) and (ii):

$$\frac{v_1 - v_3}{R_1} + \frac{v_1}{R_2} + \cancel{i_b} + \frac{v_2 - v_3}{R_4} + \frac{v_2}{R_3} - \cancel{i_b} = 0 \quad (\text{iii})$$

now have 1 eq & 2 unknowns v_1 & v_2

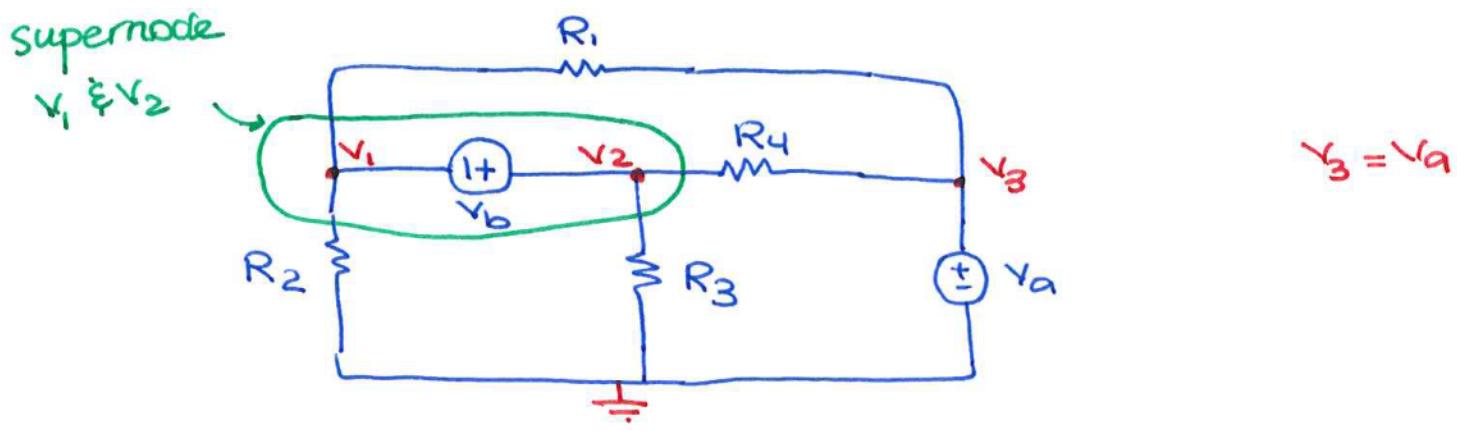This problem is handled by the concept of supernode:



i) KCL for all currents leaving supernode (green box):

$$\underbrace{\frac{v_1 - v_3}{R_1} + \frac{v_1 - 0}{R_2}}_{\text{left side (Node 1)}} + \underbrace{\frac{v_2 - v_3}{R_4} + \frac{v_2 - 0}{R_3}}_{\text{right side (Node 2)}} = 0$$

i.e. arrived at eq (iii) in one shot.

ii) A dependence equation for the two nodes within the supernode:


$$v_2 - v_1 = v_b$$

.this results in 2 equations (supernode KCL & dep eqn)
to solve for 2 unknowns v_1 & v_2 .

Ex: Find Node voltages

supernode v_1 & v_2 .

Voltage source between 2 regular nodes.

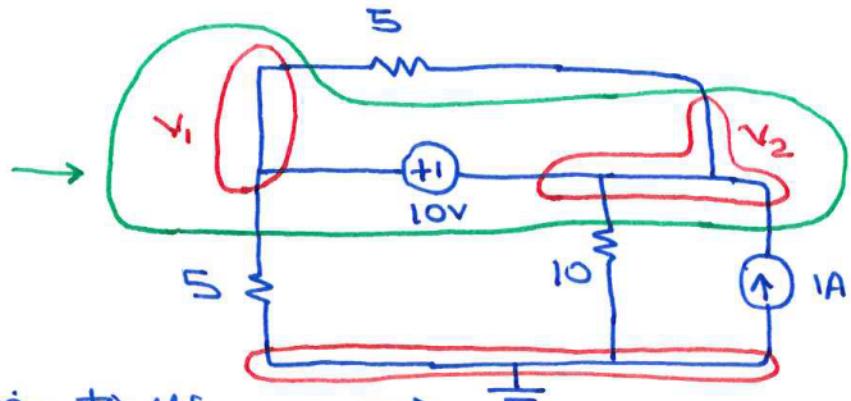

ref node given to us
(bad choice for ref node!)

Supernode KCL: $\frac{v_1 - v_2}{5} + \frac{v_1 - 0}{5} + \frac{v_2 - v_1}{5} + \frac{v_2 - 0}{10} - 1 = 0$

$\underbrace{\qquad\qquad\qquad}_{\text{node 1 side}}$ $\underbrace{\qquad\qquad\qquad}_{\text{node 2 side}}$


$\times 10:$ $2v_1 + v_2 = 10 \quad (i)$

Dependence Eq: $v_1 - v_2 = 10 \quad (ii)$

\uparrow \uparrow
the (+) terminal the (-) terminal

Solving (i) & (ii) gives: $v_1 = 6.6 \text{ V}$, $v_2 = -3.3 \text{ V}$

What if we used a different ref node?

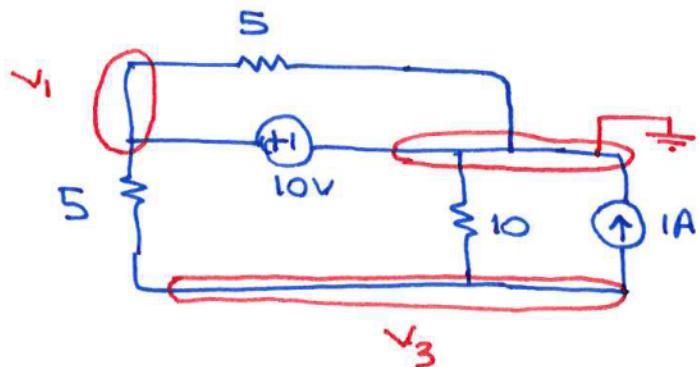


$v_1 = 10 \text{ V}$

One unknown node voltage, v_3 . Write KCL at node 3 to solve for v_3

$v_3 = 3.3 \text{ V}$

Node voltages change based on ref node location but voltages & currents for individual elements remain the same.

Ex: 2014 MT. Determine node voltages

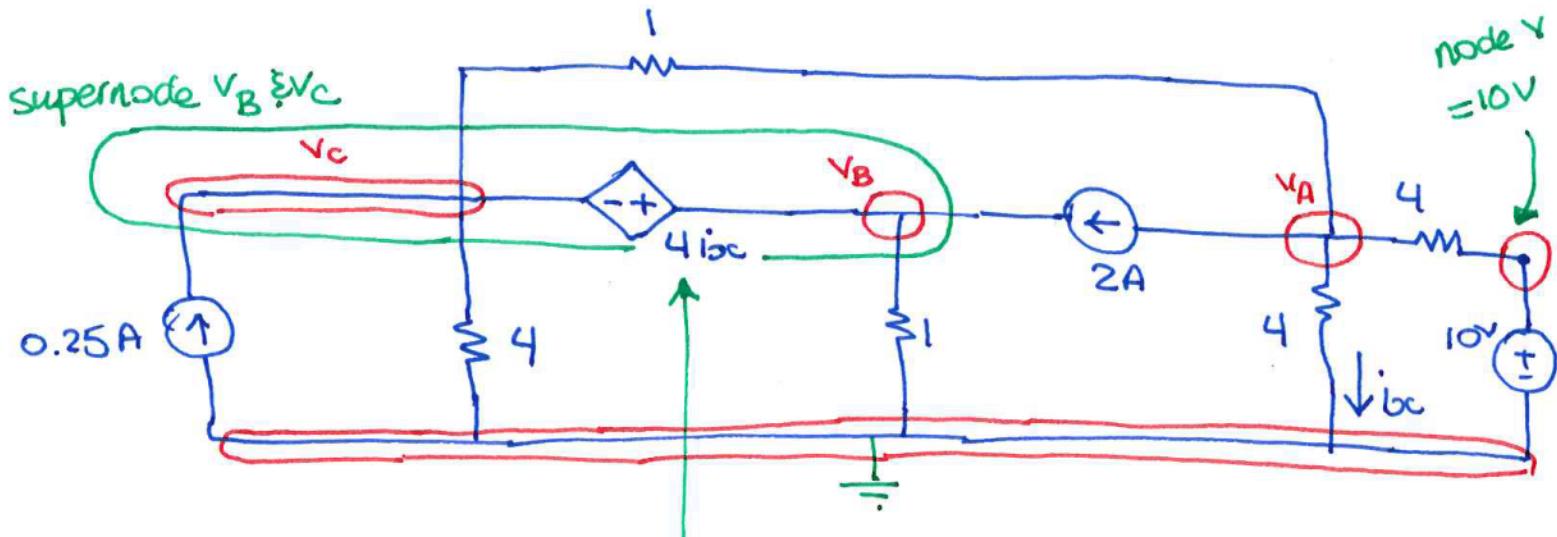

CCVS (voltage source). Don't know the current thru it.

$$\text{KCL at node A: } \frac{v_A - 10}{4} + \underbrace{\frac{v_A - 0}{4}}_{\text{this is } i_x} + \frac{v_A - v_C}{1} + 2 = 0$$

$$\text{simplify: } 6v_A - 4v_C = 2 \quad (\text{i})$$

$$\text{Supernode KCL: } \underbrace{-0.25 + \frac{v_C - 0}{4} + \frac{v_C - v_A}{1}}_{\text{node C side}} - 2 + \underbrace{\frac{v_B - 0}{1}}_{\text{node B side}} = 0$$

$$\text{simplify: } -4v_A + 4v_B + 5v_C = 9 \quad (\text{ii})$$

$$\text{Dep Eq'n from supernode: } v_B - v_C = 4ibc$$

$$\text{but we also know } ibc = \frac{v_A}{4}$$

$$\therefore v_B - v_C = v_A \quad \text{or} \quad -v_A + v_B - v_C = 0 \quad (\text{iii})$$

$$\text{Solve (i), (ii), (iii). e.g. (ii) + } -4 \times (\text{iii}) \text{ gives } 9v_C = 9 \\ \therefore v_C = 1$$

$$\text{then from (i), } v_A = 1 \text{ V}$$

$$\text{from (iii), } v_B = 2 \text{ V}$$