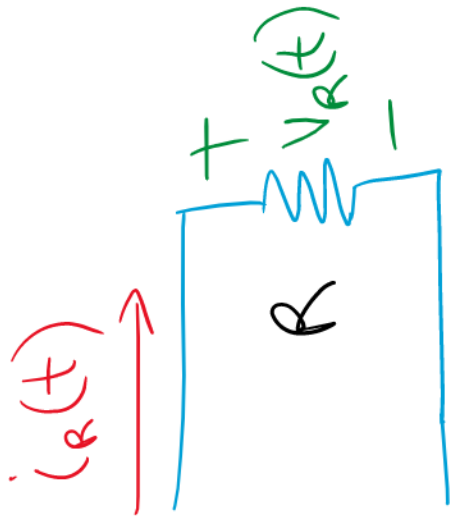


# Introduction to Complex Impedance

Impedance is similar to resistance, in that it relates the voltage and current relationship of circuit elements like resistors, capacitors, and inductors.

However, impedance is more general as it is affected by frequency and phase relationships of the circuit elements.

# Resistors




The impedance of resistors is easiest to understand, given in the following relationship

$$\overline{V_R} = R \overline{I_R}$$

where  $R$  is real-valued and is in units  $\Omega$ .


what does this mean?

# Resistors

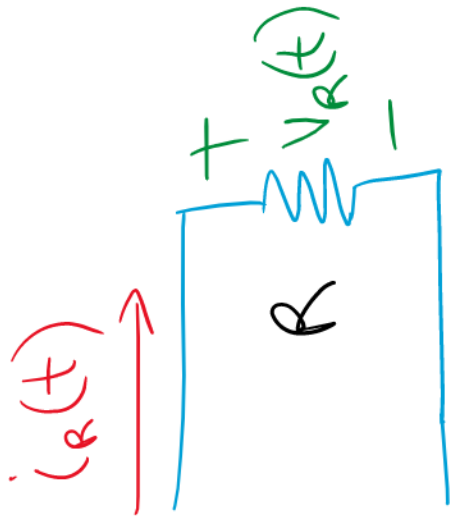

$$\bar{V}_R = R \bar{I}_R$$

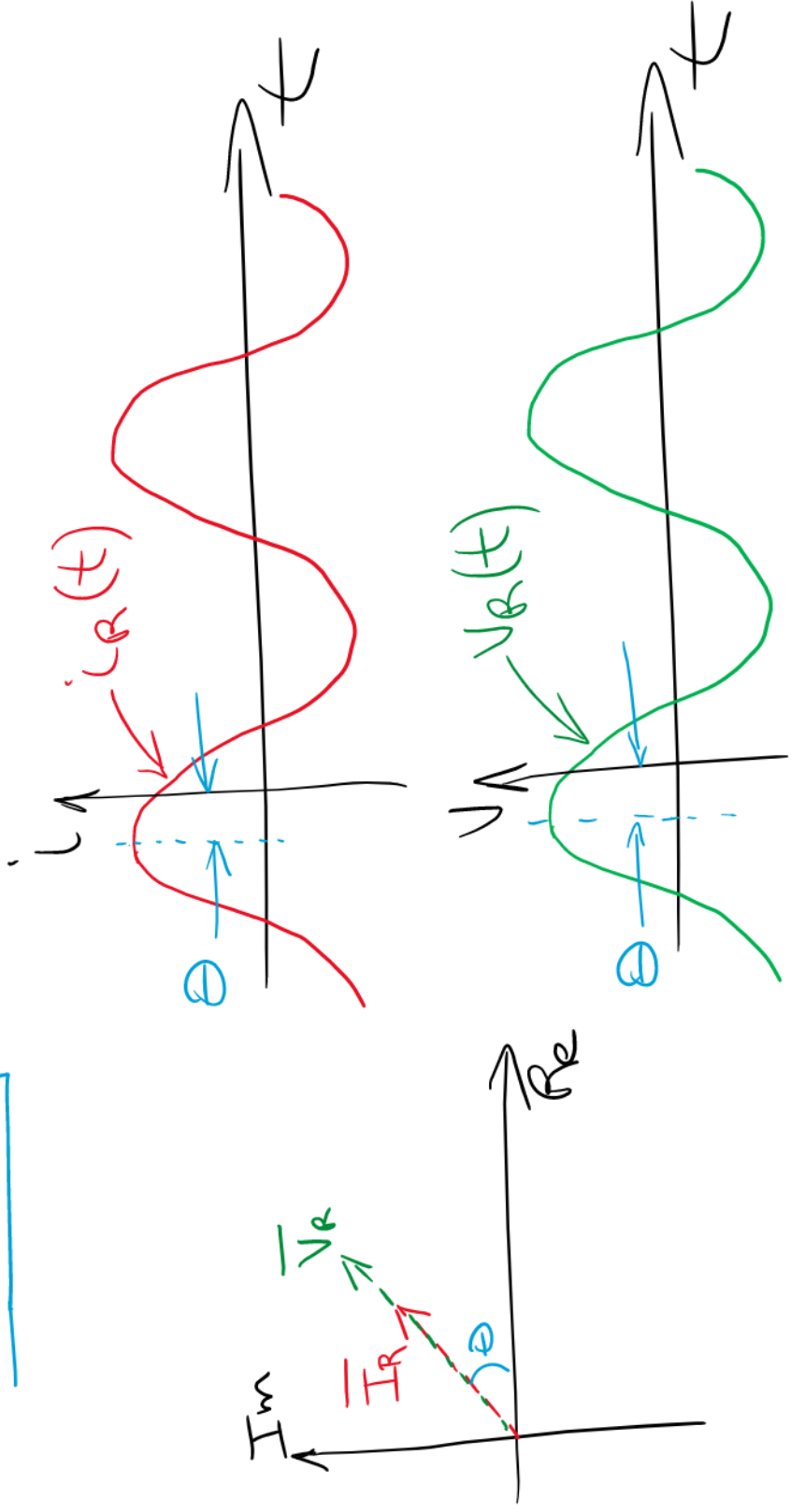Because  $R$  is real-valued, there is no phase-shift between the voltage and current waveforms.



$i_L(t)$



## Inductors

Inductors have a more complicated impedance than resistors, given by:

$$\bar{V}_L = Z_L \bar{I}_L$$


where

$$Z_L = j\omega L = \omega L \angle 90^\circ$$

and  $Z_L$  is in units  $\Omega$ .


what does this mean?

# Inductors

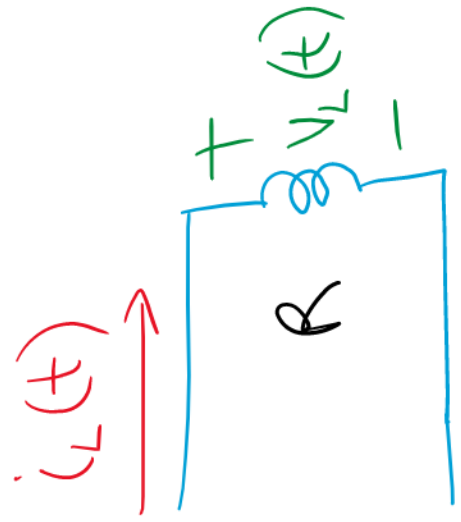


$$\underline{V}_L = Z_L \underline{I}_L = j\omega L \underline{I}_L = \omega L \underline{I}_L \angle 90^\circ$$

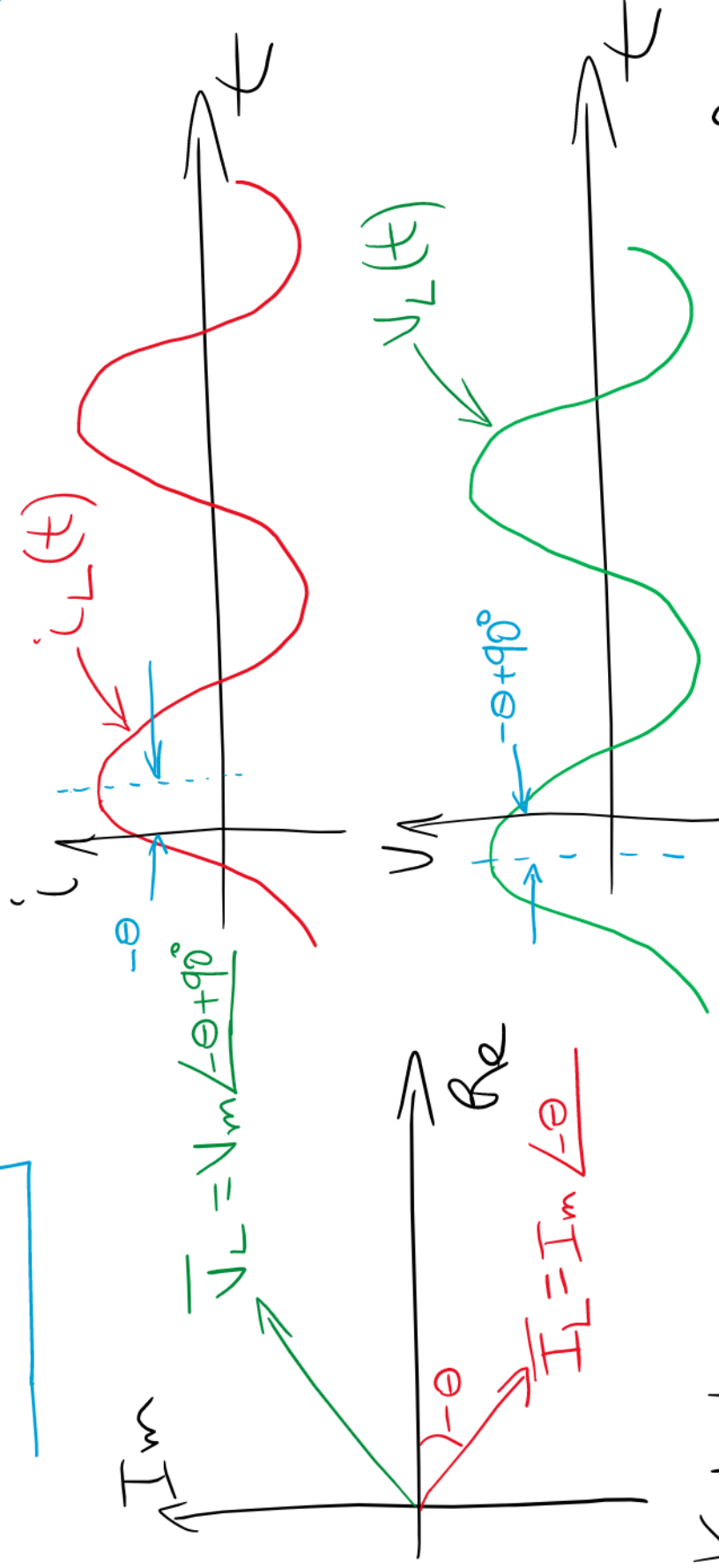Because  $Z_L$  has positive imaginary value, this represents a phase-shift of  $+90^\circ$ . For the inductor, the voltage waveform will be shifted  $90^\circ$  ahead of the current waveform.



\* Voltage leads current in an inductor by  $90^\circ$ .

# Inductors

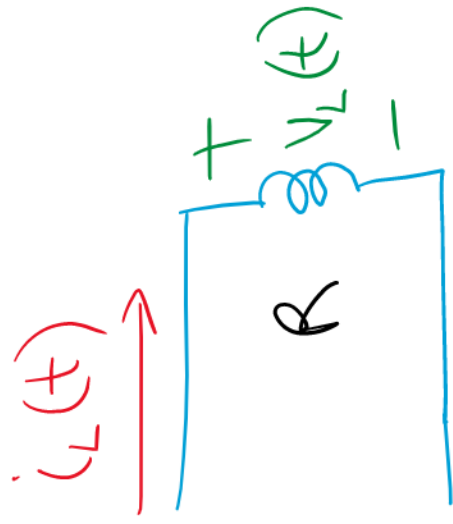


$$\bar{V}_L = Z_L \bar{I}_L = j\omega L \bar{I}_L = \omega L \bar{I}_L \angle 90^\circ$$


Other formulations:

$$\bar{I}_L = \frac{\bar{V}_L}{Z_L} = \frac{\bar{V}_L}{j\omega L} = \frac{\bar{V}_L}{\omega L} \angle -90^\circ$$

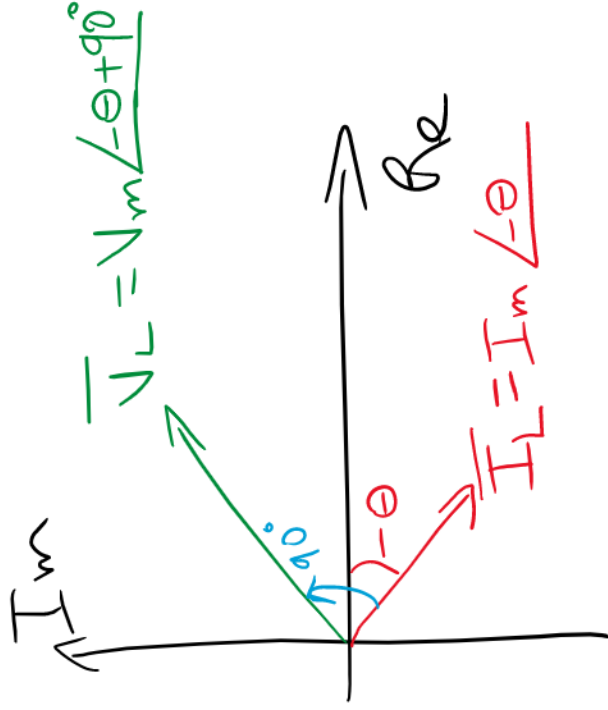
$$\text{or } Z_L = \frac{\bar{V}_L}{\bar{I}_L}$$




# Inductors

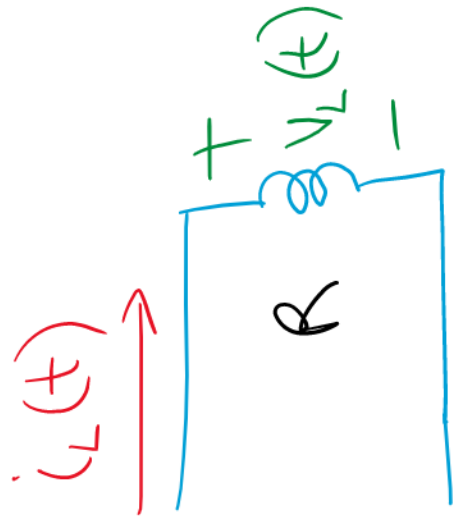

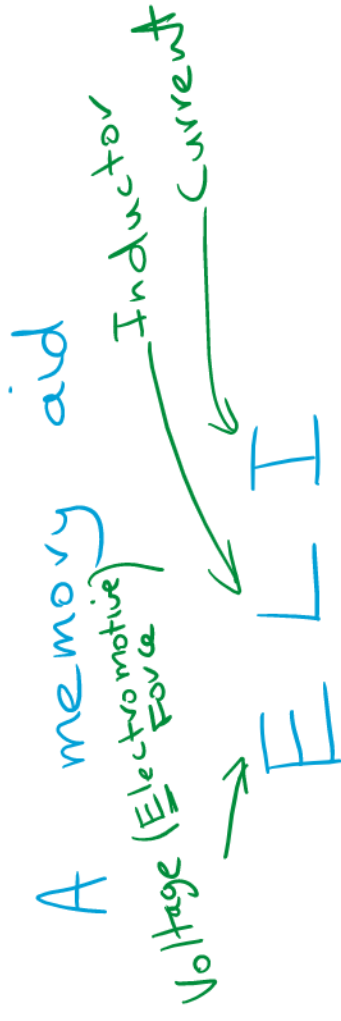
$$\bar{V}_L = Z_L \bar{I}_L = j\omega L \bar{I}_L = \omega L \bar{I}_L \angle 90^\circ$$



Voltage leads Current in an Inductor

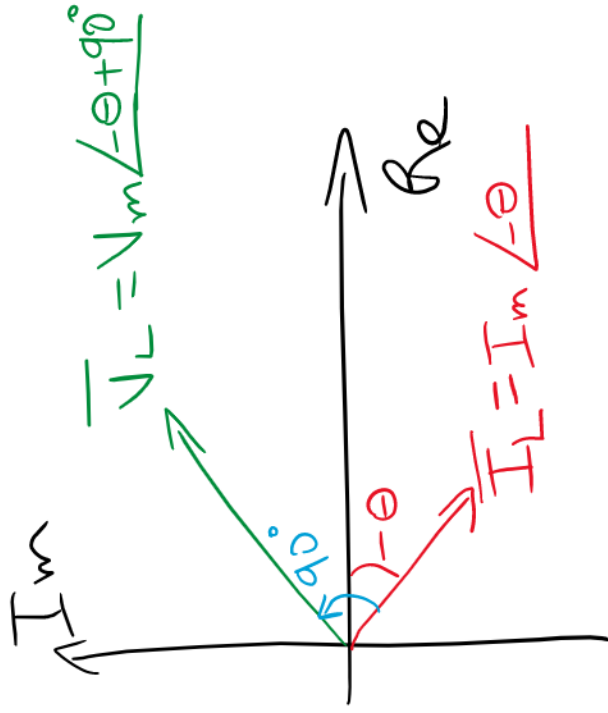

## Capacitors

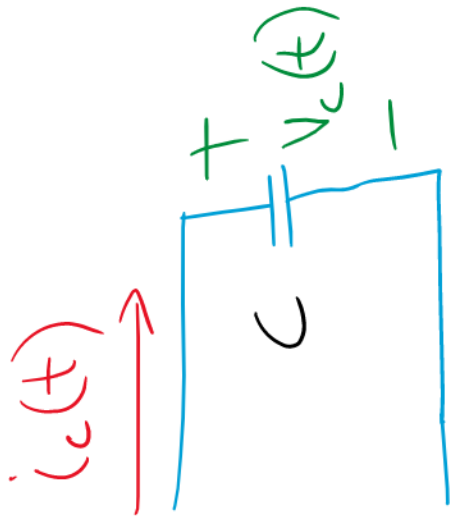

Capacitors have a more complicated impedance than resistors, given by:

where


$$Z_c = \frac{1}{j\omega C} = \frac{-j}{\omega C} = \frac{1}{\omega C} \angle -90^\circ$$

and  $Z_c$  is in units  $\Omega$ .

what does this mean?




# Capacitors

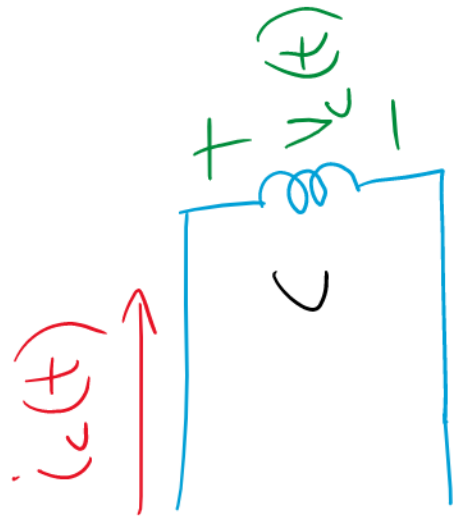



$$\bar{V}_c = Z_c \bar{I}_c = \frac{1}{j\omega C} \bar{I}_c = \frac{1}{\omega C} \bar{I}_c \angle -90^\circ$$

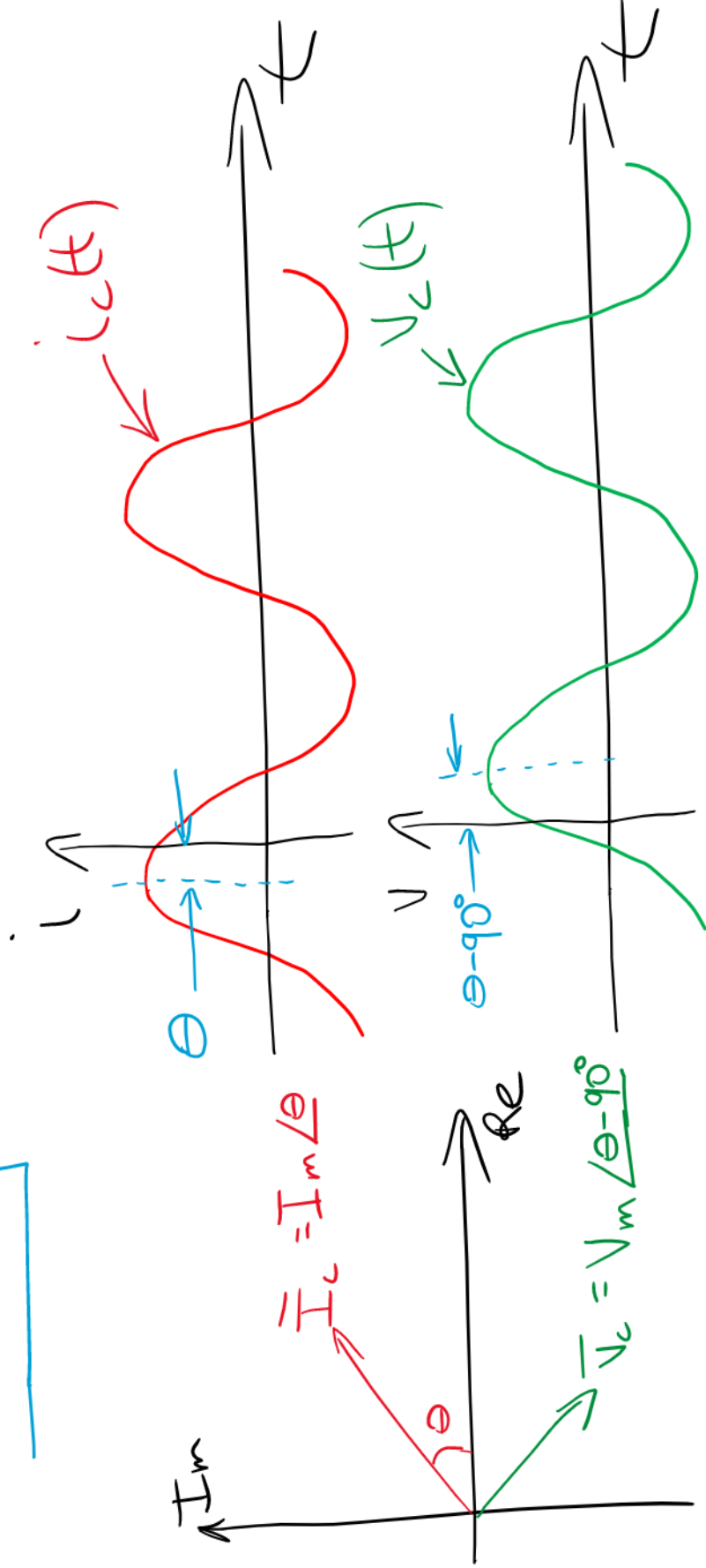Because  $Z_c$  has negative imaginary value, this represents a phase-shift of  $-90^\circ$ . For the capacitor, the current waveform will be shifted  $90^\circ$  ahead of the voltage waveform.



\* Current leads voltage in a capacitor by  $90^\circ$ .

# Capacitors

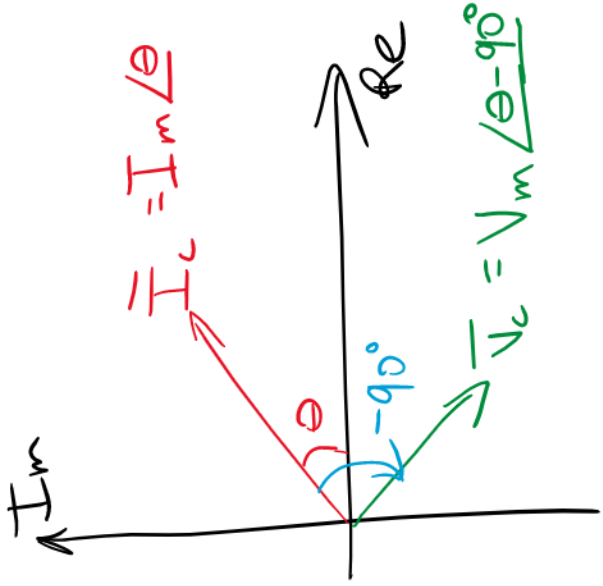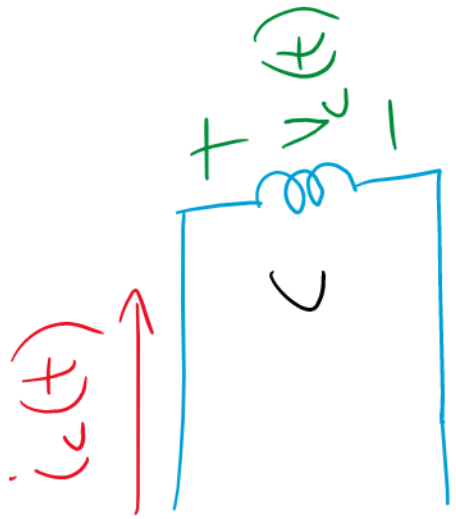

$$\bar{V}_c = Z_c \bar{I}_c = \frac{1}{j\omega C} \bar{I}_c = \frac{1}{\omega C} \bar{I}_c \angle -90^\circ$$

Other formulations

$$\bar{I}_c = \frac{\bar{V}_c}{Z_c} = \frac{\bar{V}_c}{\frac{1}{j\omega C}} = j\omega C \bar{V}_c = \omega C \bar{V}_c \angle 90^\circ$$


$$\text{or } Z_c = \frac{\bar{V}_c}{\bar{I}_c}$$

Memory aid




Current leads voltage in a capacitor.

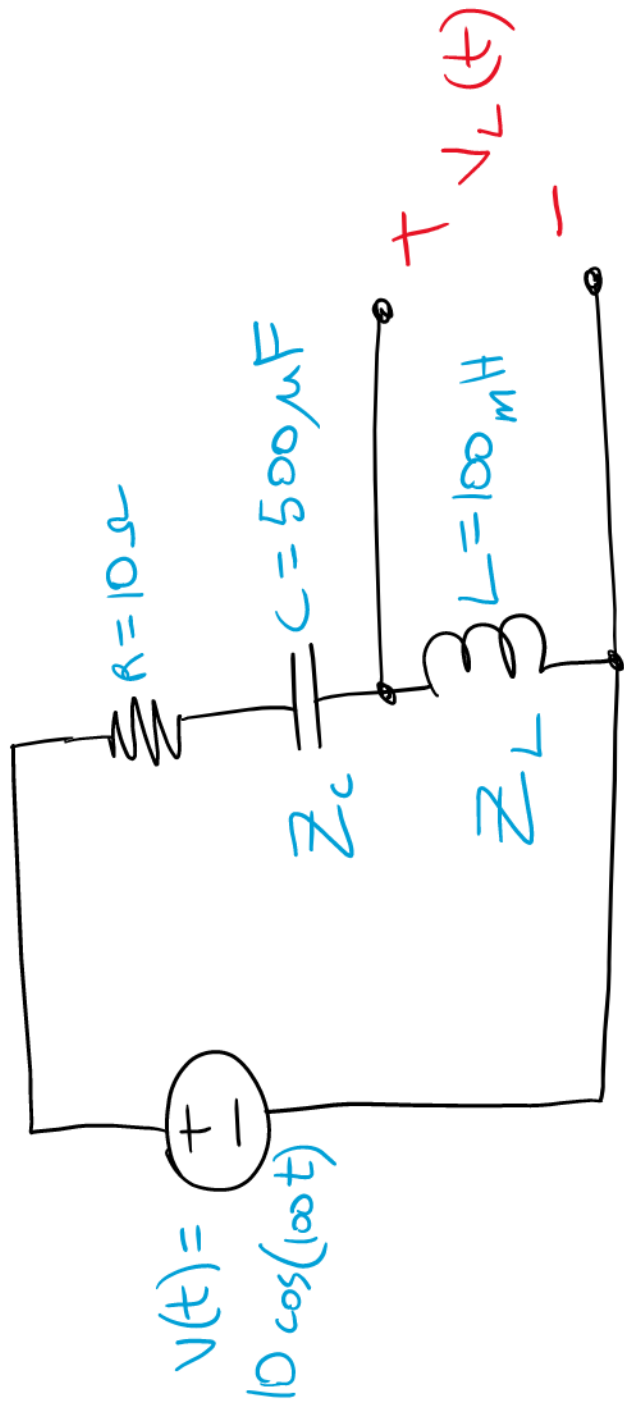Example Find  $v_L(t)$  given  $v(t) = 10 \cos(100t)$ .



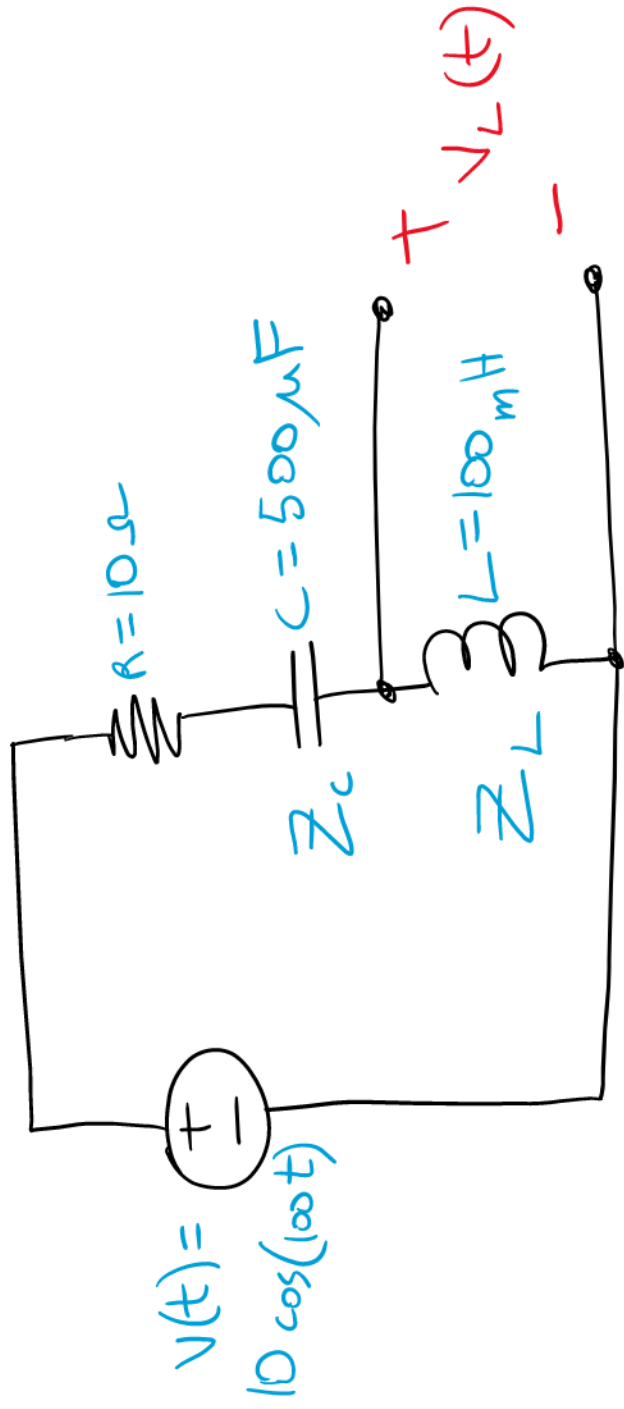Example Find  $V_L(t)$  given  $v(t) = 10 \cos(100t)$ .



Solution

Recognize this is a voltage divider.

$$\bar{V}_L = \frac{Z_L}{R + Z_C + Z_L} \times \bar{V}$$

↓ Plug in values

$$\bar{V}_L = \frac{j10}{10 + (-j20) + j10} \times 10$$

$$\bar{V}_L = \frac{j100}{10 - j10}$$

$$R = 10 \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 100 \times 500 \times 10^{-6}} = -j20 \Omega$$

$$Z_L = j\omega L = j \times 100 \times 100 \times 10^{-3} = j10 \Omega$$


$$\bar{V} = 10 \angle 0^\circ = 10 V$$

$$\bar{V}_L = \frac{j100}{10 - j10}$$

$$= \frac{j100}{10 - j10} \times \frac{10 + j10}{10 + j10} = \frac{j1000 - 1000}{100 + 100}$$

$$= \frac{-1000 + j1000}{200} = -5 + j5$$

$$\bar{V}_L = -5 + j5$$

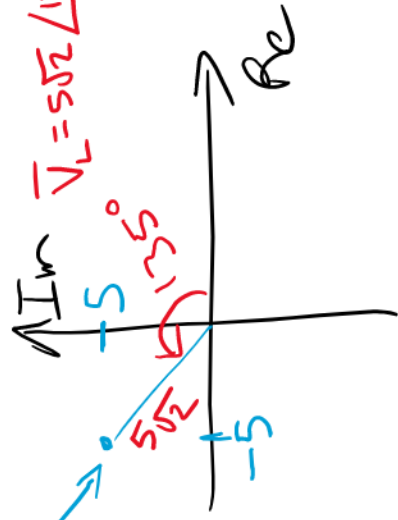

Convert  $\bar{V}_L$  to Polar form so we can easily write the time domain expression for  $V_L(t)$ .

$$\bar{V}_L = \sqrt{5^2 + 5^2} \angle 180^\circ - \tan^{-1}\left(\frac{5}{5}\right)$$

$$\bar{V}_L = 5\sqrt{2} \angle 135^\circ$$

Finally,

$$V_L(t) = 5\sqrt{2} \cos(100t + 135^\circ)$$