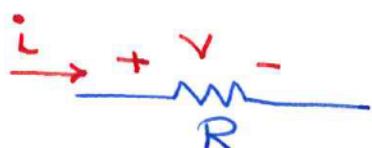


Resistors

- Voltage & current are related by Ohm's Law:
- voltage across the resistor current through the resistor


- i) if the current through the resistor is shown in the direction of voltage drop:



looks like an energy-absorbing element

then use $V = iR$

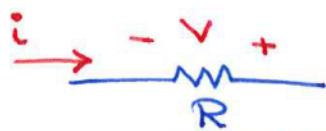- ii) If the current is shown in the direction of voltage rise



then use $V = -iR$

- Conductance : From Ohm's Law , $i = \frac{1}{R} \cdot V$

conductance, G

unit: Siemens (Ω^{-1}) , once called mho (Ω)

Power & Energy

- In electric circuits, power is the product of voltage & current

$$P = V \cdot i$$


but isn't power the rate of energy transfer?

$$P = \frac{dw}{dq_f} \cdot \frac{dq_f}{dt} = \frac{dw}{dt} \quad [J/s]$$

P: power in Watts [W]

. If current is labelled in direction of voltage drop:

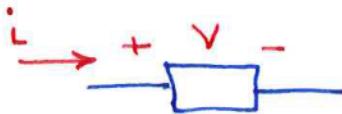this is called the passive reference direction




which implies the element is absorbing power,

then we must use

$$P = Vi$$

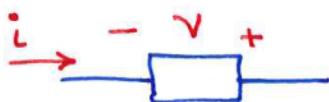. If current is labelled in direction of voltage rise:



then we must use

$$P = -Vi$$


. In both cases (if using $P=Vi$ or $P=-Vi$),

if $P > 0$, then element is absorbing power

if $P < 0$, then element is supplying power.

Ex: Find power for :

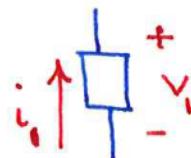a) $V_i = 12 \text{ V}$, $i_i = 10 \text{ A}$



supplies 120 W

$$P = -V_i i_i = -(12 \text{ V})(10 \text{ A}) = -120 \text{ W}$$

↑
current in dir of voltage rise


b) $V_1 = 60V$, $i_1 = -10A$

$$P = -V_1 i_1 = -(60V)(-10A) = 600W$$

\leftarrow absorbs 600W

alternatively, we can change direction of current to match the actual direction

$$P = Vi = (60V)(10A) = 600W$$

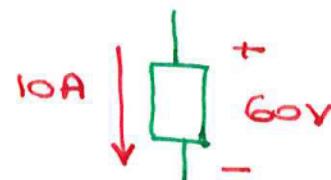

Power in resistors



Power : $P = Vi$

Ohm's Law : $V = iR$

$$\therefore P = i^2 \cdot R$$

or

$$P = \frac{V^2}{R}$$

P is always positive for resistors. They will always absorb power.

Ex: Consider the circuit.


Find power for both elements.

Need to find unknown voltages & currents.

For now, let's logic our way through this.

Later, we will develop systematic ways of finding voltage & current.

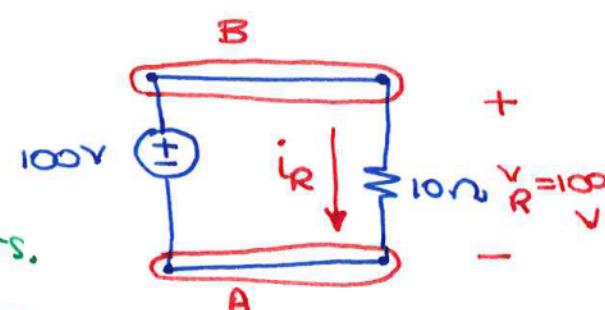Step 1: Find voltage across resistor. It is connected to the same 2 points as the 100V source. (B is higher in potential than A by 100V).




step 2: choose an arbitrary direction for i_R

step 3: From Ohm's Law : $i_R = \frac{V_R}{10\Omega} = \frac{100V}{10\Omega} = 10A$

For the resistor, $P = V_R \cdot i_R = (100V)(10A) = 1000W$
absorbs 1000W ↑

can also use $P = (i_R)^2 \cdot R = \frac{(V_R)^2}{R}$

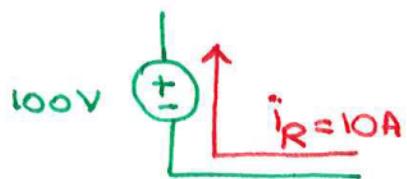step 4: Current i_R will continue to flow through the source:




$$P_{\text{source}} = -V \cdot i_R = -(100V)(10A) = -1000W$$

↑
current sees (-) terminal first
↑
supplies 1000W

What if we chose i_R to be in the opposite direction in step 2?

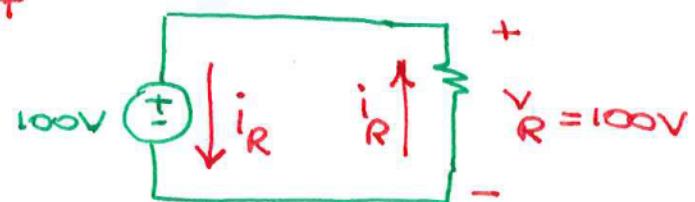Ohm's Law: $V_R = -i_R \cdot R$ current sees (-) first



$$\therefore i_R = \frac{-V_R}{R} = \frac{-100V}{10\Omega} = -10A$$

Same actual current as before


For the resistor, $P = -V_R \cdot i_R = -(100V)(-10A) = 1000W$

for the source, $P_{\text{source}} = (100V) \cdot i_R = (100V)(-10A) = -1000W$

Energy : we have $P = \frac{dW}{dt}$ therefore $W = \int_{t_1}^{t_2} P(t) dt$

- Power companies measure energy to determine monthly bill
i.e. usage of power over time


Ex:

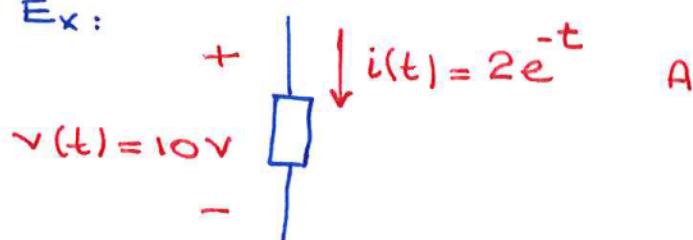

- Compute power
- Compute energy from $t=0 \rightarrow \infty$

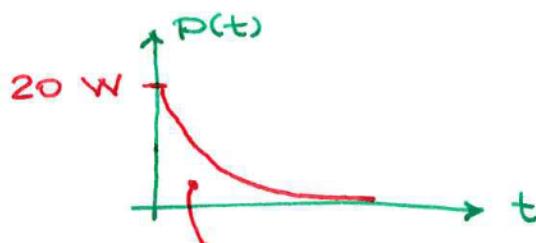a) Current in dir of voltage drop

$$\therefore P(t) = V(t) \cdot i(t) = 10 \times 2e^{-t} = 20e^{-t} W$$



energy from $t=0 \rightarrow \infty$ is the area under the curve

$$b) W = \int_0^{\infty} 20e^{-t} dt = -20 e^{-t} \Big|_0^{\infty} = 0 - (-20) = 20 J$$

$W > 0 \therefore$ absorbs energy

Ex2: Assume energy cost is \$ 0.12 per Kilowatt-hour (kWh)

Electrical bill for 30 days : \$ 60.⁰⁰

Power is constant over this time period. $\therefore 1 W = 1 J/S$

$$= \frac{1}{1000} \text{ kW} \cdot \frac{1}{3600} \text{ h}$$

a) Find power in Watts


$$\therefore 1 \text{ kWh} = 3600 \times 1000 \text{ J}$$

b) Voltage = 120V . Find current.

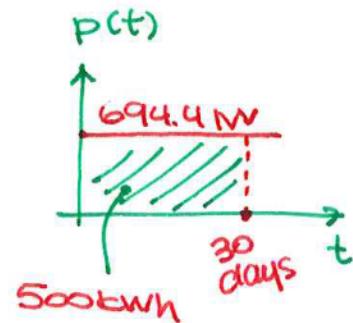a) Total energy consumed in 30 days is:


$$W_{30 \text{ days}} = \frac{\$60.00}{\$0.12/\text{kWh}} = 500 \text{ kWh}$$

$$P = \frac{W_{30 \text{ day}}}{t} = \frac{500 \text{ kWh}}{(30 \times 24) \text{ h}} = 694.4 \text{ W}$$




let's also find $w(t)$:
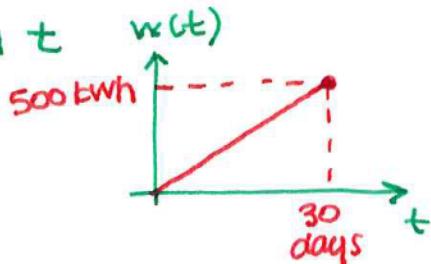
$$w(t) = \int_0^t p(t) dt = \int_0^t 694.4 dt = 694.4 t$$



b)

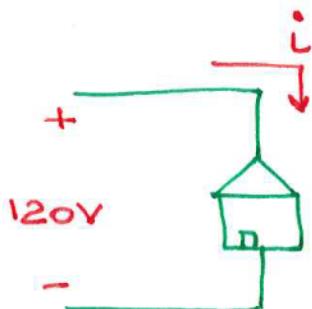

$$P = Vi \quad \therefore i = \frac{P}{V} = \frac{694.4 \text{ W}}{120 \text{ V}} = 5.8 \text{ A}$$


Kirchoff's Laws

So far, we have seen:

- fundamental electrical quantities V, i (and P, w)
 - circuit elements with their own $V \& i$ relationship
- . Kirchoff's Laws define how $V \& i$ distribute in a circuit.


Kirchoff's Current Law (KCL)

- Fluid analogy of KCL:

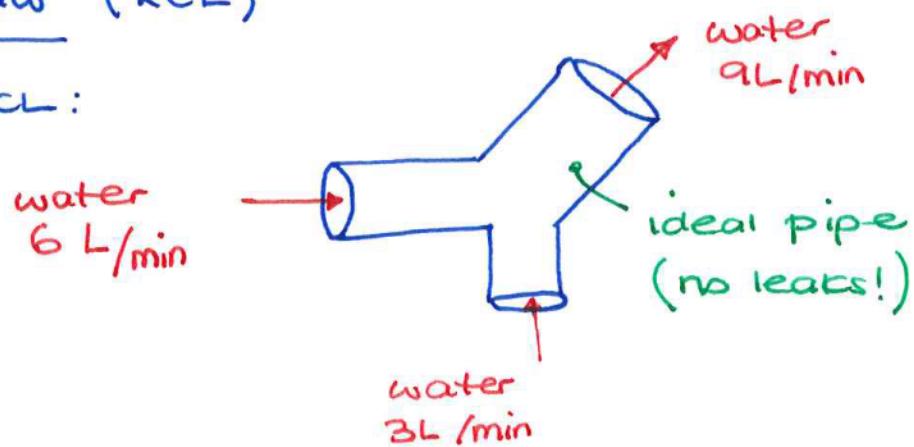


- Consider a node in a circuit:

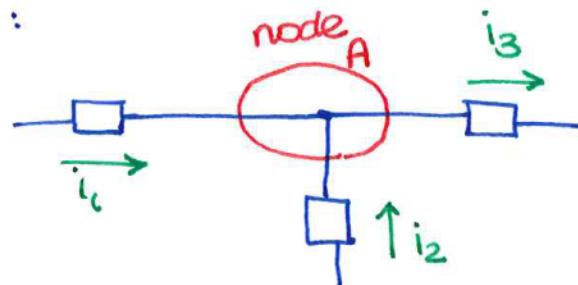node: joining of 2 or more circuit elements




KCL states: Algebraic sum of all currents at a node must be zero.

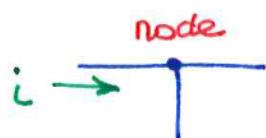- choose a consistent way to distinguish incoming & outgoing currents at a node:



current entering the node adds.

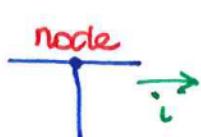

current leaving the node subtracts

Later, in the Node Voltage Method, we will use the opposite convention!

- Sum of currents at node A in the circuit above:


$$\underbrace{i_1 + i_2}_{\text{enter } A} - \underbrace{i_3}_{\text{leave } A} = 0$$

so $i_1 + i_2 = i_3$

Ex: Determine i_1

Note that M is a single node.

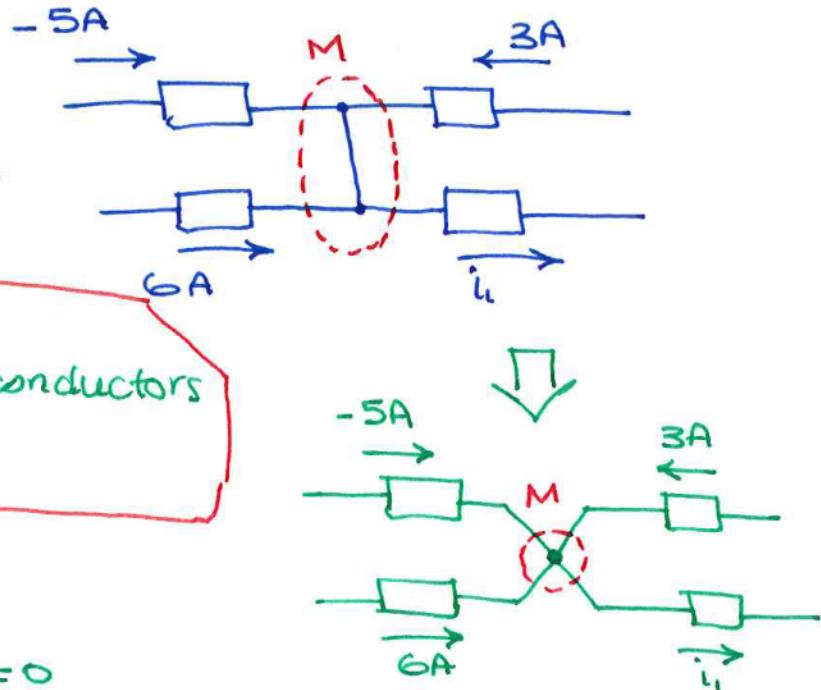Connection points connected directly to each other by conductors constitute one node



KCL at node M:

$$\underbrace{-5 + 3 + 6}_{\text{enter } M} - i_1 \underset{\text{leaves } M}{=} 0$$

$$\therefore i_1 = 4 \text{ A}$$

Alternatively, we can write KCL inside Node M:

Choose an arbitrary direction for i_2


KCL at connection point N:

$$\underbrace{-5 + 3}_{\text{enter } N} - i_2 \underset{\text{leave } N}{=} 0 \quad \therefore i_2 = -2 \text{ A}$$


KCL at connection point P:

$$-2 \circled{i_2} \underbrace{+ 6}_{\text{enter } P} - i_1 \underset{\text{leaves } P}{=} 0 \quad \therefore i_1 = 4 \text{ A}$$

for each connection point

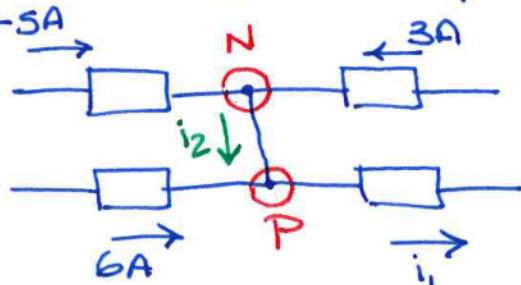

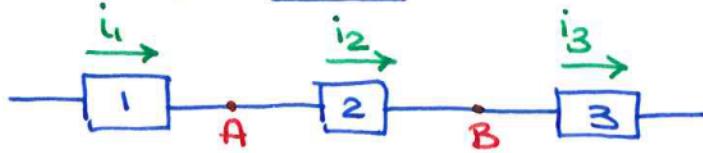. Let's consider series connection of elements



Two elements are in series if they are connected at one node only and there is no other element connected to that node.


$$\text{KCL at node A: } i_1 - i_2 = 0 \quad \therefore i_1 = i_2$$

$$\text{KCL at node B: } i_2 - i_3 = 0 \quad \therefore i_2 = i_3$$

i.e. Elements in series have the same current *

* if the currents are labelled with the same direction

Ex: What's in series here?

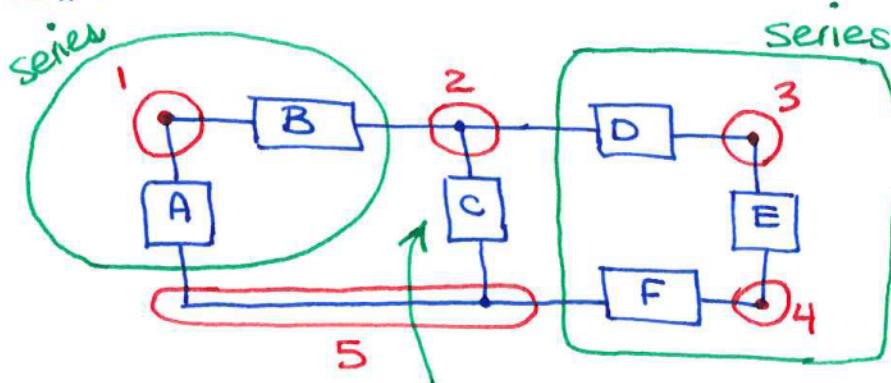


Examine all nodes

&
identify the ones
at which only 2
elements are joined

. Circuits that violate KCL:


KCL at node B:

$$5A - 10A \neq 0$$

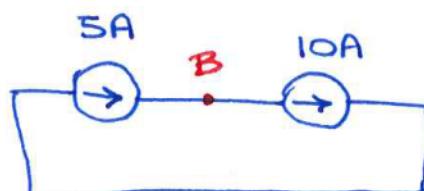

Kirchoff's Voltage Law (KVL)

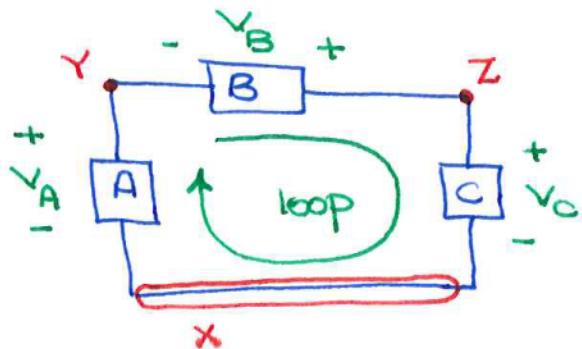- Derived from conservation of energy.
- Consider a loop in a circuit:





loop: a closed path starting at a node & finishing back at the same node

loop: $Y \rightarrow Z \rightarrow X \rightarrow Y$

KVL states: Algebraic sum of all voltages around a loop must be zero.


- Loop direction is chosen arbitrarily! It has no relation to current direction
- When summing voltages around a loop, by convention:

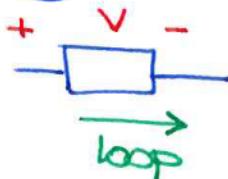1) if  then add V

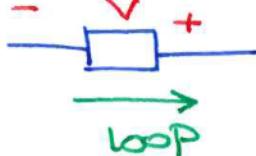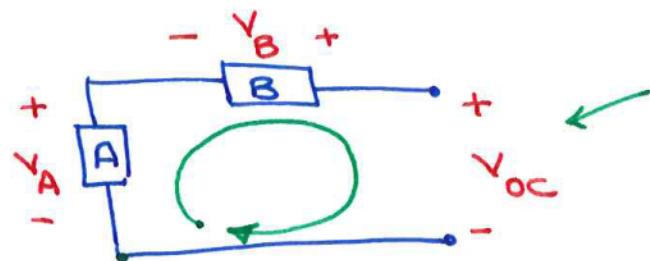2) if  then subtract V

• KVL around the example circuit gives: $-V_B + V_C - V_A = 0$

- Loops can contain open circuits. For example,




important to account for potential difference across the open circuit

$$KVL: -V_A - V_B + V_{oc} = 0$$

- Circuits prohibited by KVL:



- Consider parallel elements:

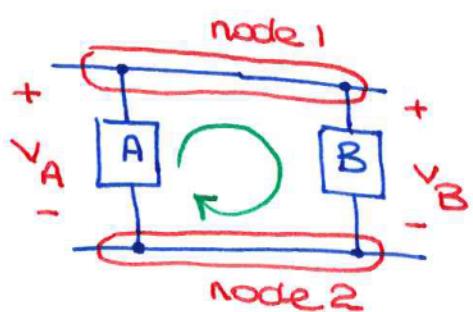

Two elements are parallel if their terminals are directly connected to each other

in other words,


they are connected to the same 2 nodes

$$KVL \text{ around the loop: } -V_A + V_B = 0 \quad \therefore V_A = V_B$$

- Elements in parallel have the same voltage *


* if the polarities are labelled consistently.

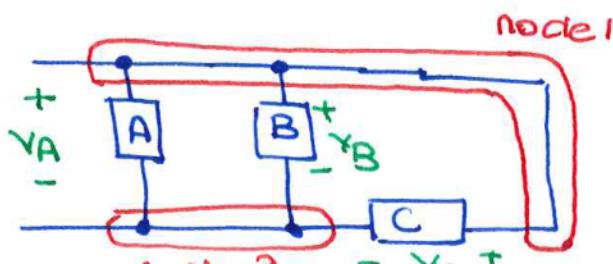- We can have more than 2 elements in parallel:



$$V_A = V_B = V_C$$

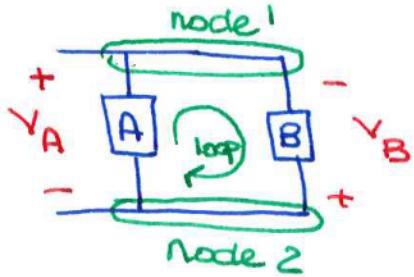What if the polarities were not labelled consistently?



$$V_A = -V_B$$


can confirm with KVL:

$$-V_A - V_B = 0$$

$$\therefore V_A = -V_B$$


Ex:

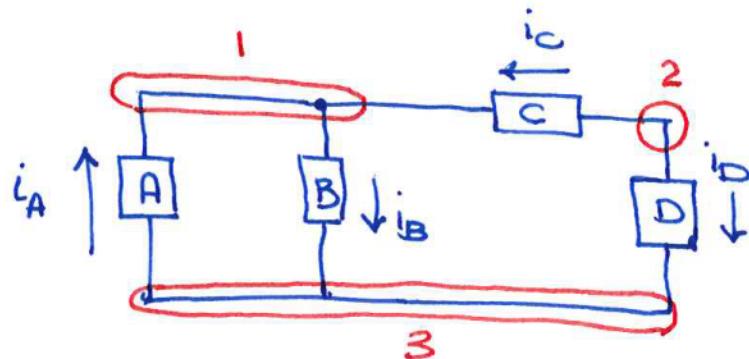- a) What's in series, parallel?
- b) i_C in terms of i_D
- c) $i_A = 3A$, $i_C = 1A$. Find i_B, i_D .



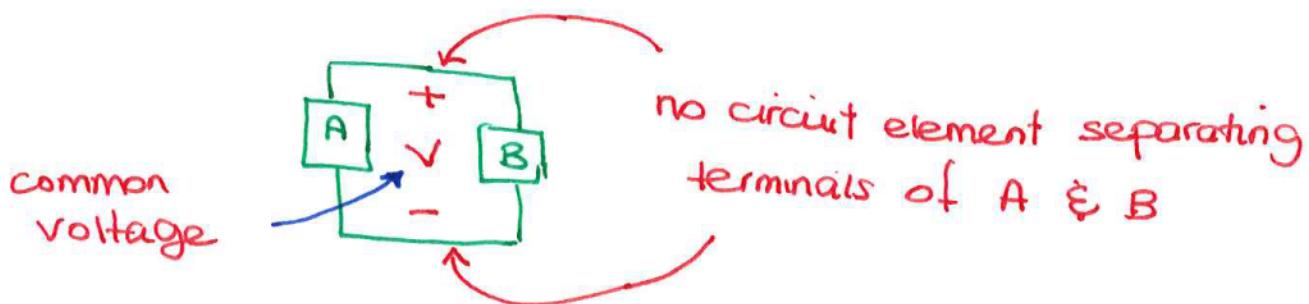a) Series: C & D. Connected at one node only,
nothing else connected there.

Parallel: A & B. Connected to the same 2 nodes (1 & 3)





- b) C & D are in series \therefore must have the same current
paying attention to directions: $i_C = -i_D$
or, from KCL at node 2: $-i_C - i_D = 0 \therefore i_C = -i_D$

c) $i_B = -i_C = -1A$


KCL at node 1: $i_A - i_B + i_C = 0 \therefore i_B = 4A$

$i_A = 3A$ $i_C = 1A$

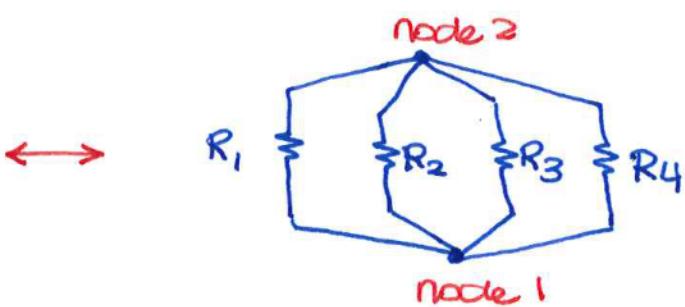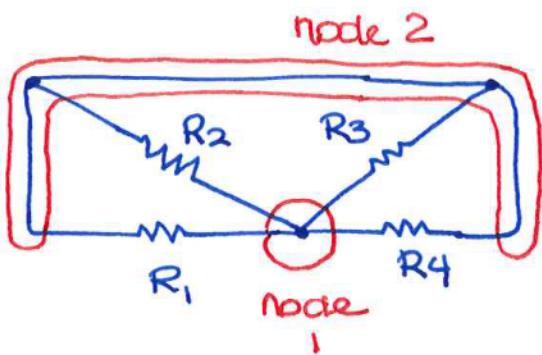- Watch for parallel connections that may not appear like parallel elements at first glance



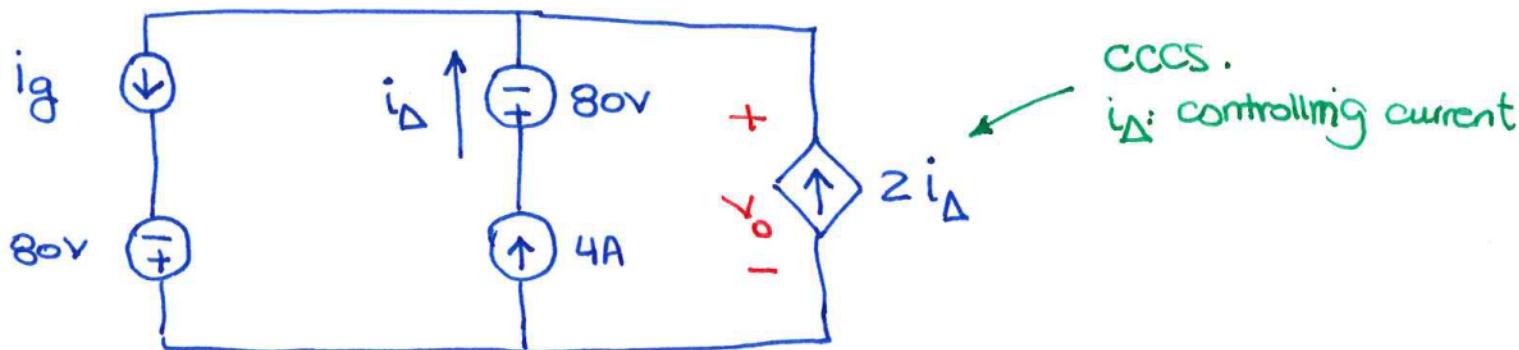Ex: Let $V_o = 100V$. Find the power for each element:



Strategy:

- Need all voltages & currents to calculate power
- Use KVL & KCL to find unknown voltages & currents. Assume polarity/direction if unknown.