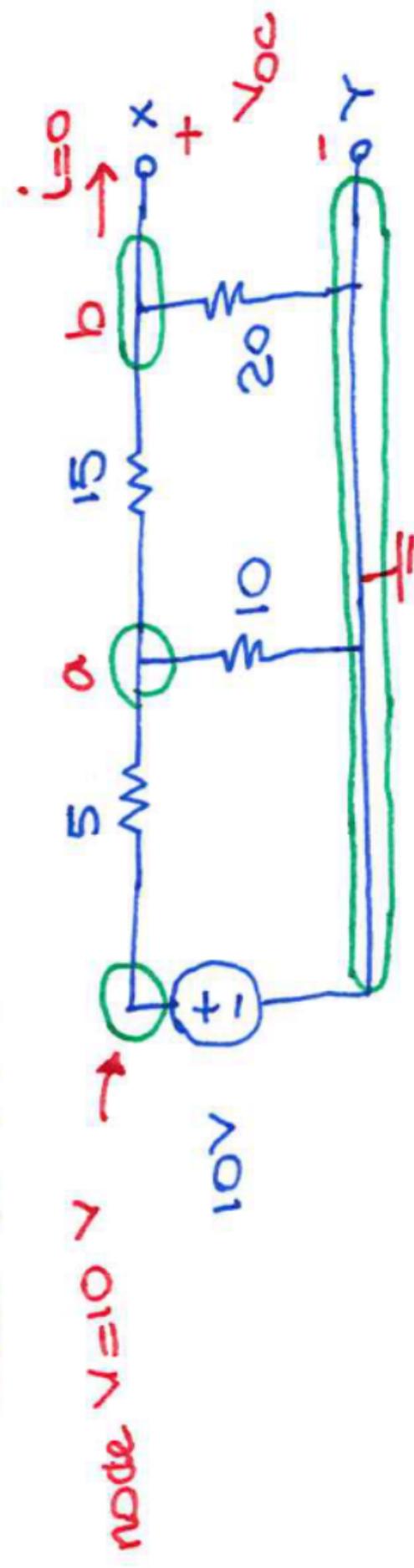


Ex: Find thevenin Equivalent of the following circuit as seen from X & Y:

note  $V = 10$  V



Determining a thevenin Equivalent is two separate analysis problems: Find  $v_{oc}$  & find  $i_{sc}$

1) Find  $V_{oc}$  using method of your choice.

$V_{oc}$  is the voltage across the  $20\Omega$  resistor in this circuit.

Let's try Nodal.  $V_{oc}$  is the node voltage at b (terminal X is part of node b, terminal Y is part of ref node)


$$\text{KCL at } a : \frac{V_a - 10}{5} + \frac{V_a}{10} + \frac{V_a - V_b}{15} = 0$$
$$\therefore 11V_a - 2V_b = 60 \quad (\text{i})$$

$$\text{KCL at } b : \frac{V_b - V_a}{15} + \frac{V_b}{20} + 0 = 0$$
$$\therefore -4V_a + 7V_b = 0 \quad (\text{ii})$$

Solve (i) & (ii). Only interested in  $V_b$ .  $V_b = 3.48 \text{ V}$

$$V_t = V_{oc} = V_{XY} = V_b = 3.48 \text{ V}$$

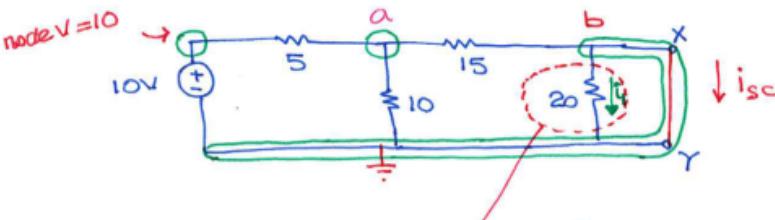2) Now, find  $i_{sc}$  using any method. Let's try Nodal again



"Shorted out". It can be removed from our analysis

why? 1)  $i_c = 0$  since potential difference across the resistor =  $V_b - V_b = 0 \text{ V}$ . It is connected to the same node on both sides


or 2) It is parallel with a short circuit between X & Y ( $R=0$ )

$$R_{eq} = \frac{0 \times 20}{0 + 20} = 0$$

- What happened to  $v_b$ ? Node b now directly connected to ref node (part of ref node)  $\therefore v_b = 0$

important: SC changes the circuit. Must treat circuit as a whole new analysis problem

redraw:

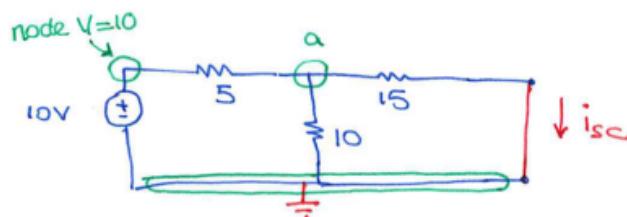

$$\text{KCL at } a: \frac{v_a - 10}{5} + \frac{v_a}{10} + \underbrace{\frac{v_a}{15}}_{i_{SC}} = 0$$


Note: this is  $i_{SC}$ . Current from node a to ref node through  $15\Omega$  resistor

$$\therefore v_a = 5.45 \text{ V}$$


$$i_{SC} = \frac{v_a - 0}{15} = 0.364 \text{ A}$$

$$\text{Finally, } R_t = \frac{v_{oc}}{i_{SC}} = \frac{3.48 \text{ V}}{0.364 \text{ A}} = 9.56 \text{ Ω}$$

Thevenin Eq Circuit:

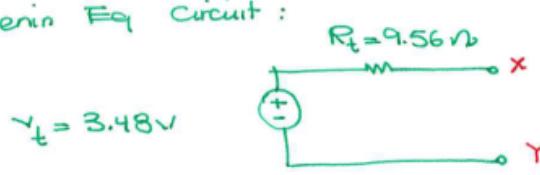

Ex2. Find thevenin Equivalent of:

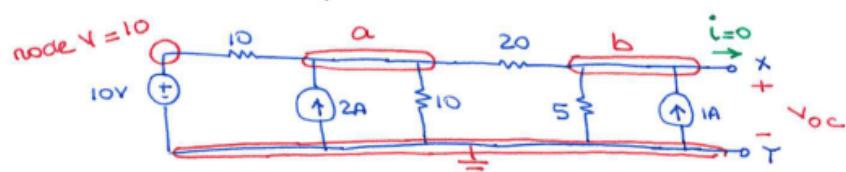

1) Find  $V_{oc}$ . Let's use node voltage.

$$V_{oc} = V_{Y\bar{Y}} = V_b - 0 = V_b$$

$$\text{KCL at node } a: \frac{V_a - 10}{10} - 2 + \frac{V_a}{10} + \frac{V_a - V_b}{20} = 0$$

$$\therefore 5V_a - V_b = 60 \quad (\text{i})$$


$$\text{KCL at node } b: \frac{V_b - V_a}{20} + \frac{V_b}{5} - 1 = 0$$

$$\therefore -V_a + 5V_b = 20 \quad (\text{ii})$$

Solve (i) and (ii). Only interested in  $V_b$ .  $V_b = 6.6 \text{ V}$

$$V_t = V_{oc} = V_b = 6.6 \text{ V}$$

2) Now, find  $i_{sc}$

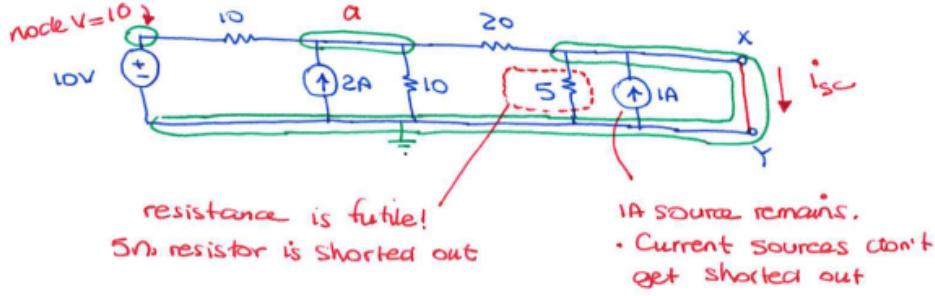


Let's try node voltage again to find  $v_a$ :

KCL at a:  $\frac{v_a - 10}{10} - 2 + \frac{v_a}{10} + \frac{v_a}{20} = 0$

Solve this to get  $v_a = 12 \text{ V}$


Use KCL at a connection point to find  $i_{sc}$ :
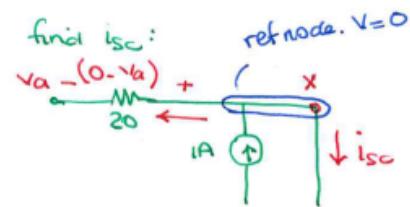
$$\frac{12 \text{ V}}{20} - 1 + i_{sc} = 0$$
$$\therefore i_{sc} = 1.6 \text{ A}$$



. Finally,  $R_t = \frac{v_{oc}}{i_{sc}} = \frac{6.6 \text{ V}}{1.6 \text{ A}} = 4.16 \text{ }\Omega$

. Thevenin Equivalent circuit:

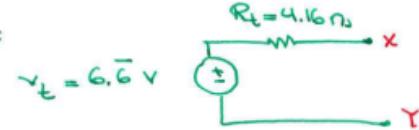


### Finding $R_t$ Directly

. If a circuit has no dependent sources, then we may use an alternative method to find  $R_t$  by zeroing the sources:

. How to zero sources?



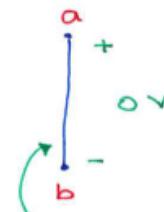
if we let  $V=0$ ,  
the voltage source  
becomes a short circuit



effective resistance =  $0\Omega$



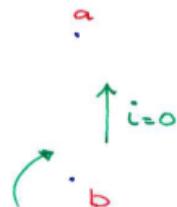If we let  $i=0$ ,  
the current source  
becomes an open  
circuit




effective resistance =  $\infty$

- Now, find resistance as seen by the terminals by combining series & parallel resistors


- Repeat previous example. Find  $R_t$  by zeroing sources:

two current sources are now SC

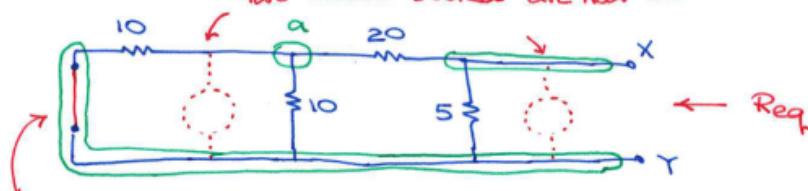

voltage source is now SC


Three nodes:  $a$ ,  $X$ , and  $Y$

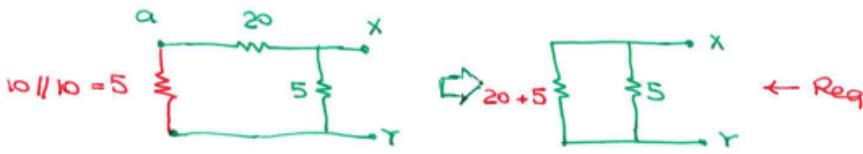

$$Req = R_t = 5 // 25 = \frac{5 \times 25}{5 + 25} = 4.16 \text{ ohms}$$

- Reminder: this method cannot be used if a circuit has dependent sources. Must determine  $i_{sc}$ ,  $R_t = \frac{V_{oc}}{i_{sc}}$  for those circuits.

Ex: Find thevenin Eq of:

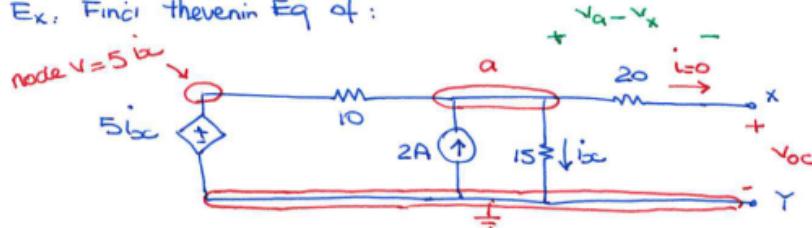

Let's find  $V_{oc}$  using node voltage

with terminals  $X \& Y$  open, no current flows through  $20\Omega$  resistor  
 $\therefore$  Voltage across  $20\Omega$  resistor = 0

$$V_a - V_x = 0 \quad \therefore V_a = V_x$$

$$V_a = V_x = V_{XY} = V_{oc} = V_t$$

$\uparrow$   
Y is part of ref node

• Node eq at a:


$$\frac{V_a - 5i_o}{10} - 2 + \frac{V_a}{15} + 0 = 0$$

this is also  $i_o$

Solve to get  $V_a = V_{oc} = V_t = 15 V$

• Now, find  $i_{sc}$

• Nothing is shorted out

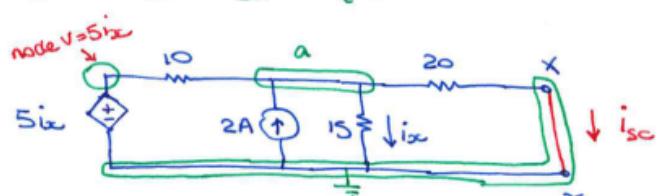

Let's use node voltage again

$$\text{Node eq at } a : \frac{V_a - 5i_o}{10} - 2 + \frac{V_a}{15} + \frac{V_a - 0}{20} = 0$$


$i_o$        $\downarrow$   
this is  $i_{sc}$

Solve for  $V_a$  to get:  $V_a = 10.91 V$

$\leftarrow$  Note that  $V_a$  is different from the OC condition

$$\text{then } i_{sc} = \frac{V_a - 0}{20} = 0.545 A$$
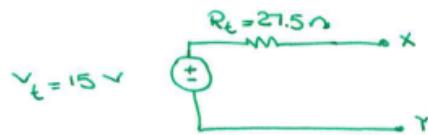
$$\text{Finally, } R_t = \frac{V_{oc}}{I_{sc}} = \frac{15 \text{ V}}{0.545 \text{ A}} = 27.5 \text{ }\Omega$$



### Summary of Thevenin Equivalents


1) Find  $V_t$ . Have to find  $V_{oc}$

2) Find  $R_t$ : . Find  $I_{sc}$  .  $R_t = \frac{V_{oc}}{I_{sc}}$

OR . if no dep. sources, turn off indep. sources, find  $R_{eq}$  by combining series/parallel resistors
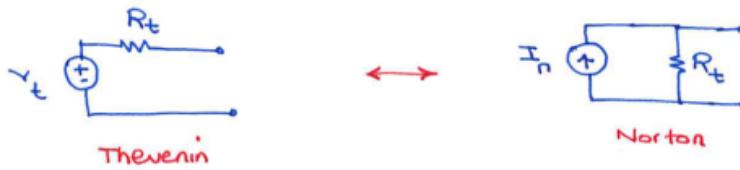
### Norton Equivalent

• Provides an alternative form to Thevenin Equivalent:



$$V_t = V_{oc}$$

$$R_t = \frac{V_{oc}}{I_{sc}}$$

$$I_n = I_{sc}$$

$$= \frac{V_t}{R_t}$$


- Check to see if Thevenin & Norton have the same OC & SC characteristics:



$V_{oc}$  is the voltage across  $R_t$ .



From Ohm's Law:
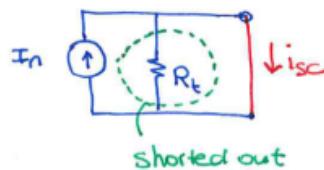
$$V_{oc} = I_n \cdot R_t = I_{sc} \cdot R_t = \frac{V_t}{R_t} \cdot R_t \\ = V_t \quad \leftarrow \text{same as Thevenin Eq Circuit}$$



$$I_{sc} = I_n = \frac{V_t}{R_t} \quad \leftarrow \text{same as } I_{sc} \text{ for Thevenin Eq Circuit}$$


- Last example, re-visited:

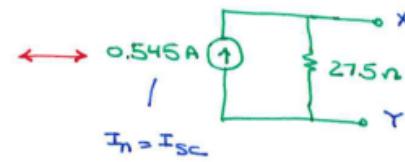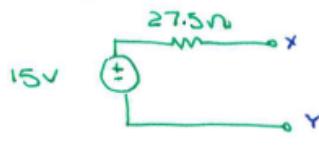

- Thevenin & Norton are related by Source Transformation:




Voltage source in series with resistor

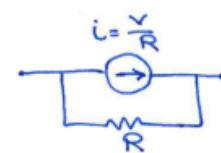

current source in parallel with resistor

- Source transformation can be applied to any circuit, i.e. it is not exclusive to Thevenin / Norton
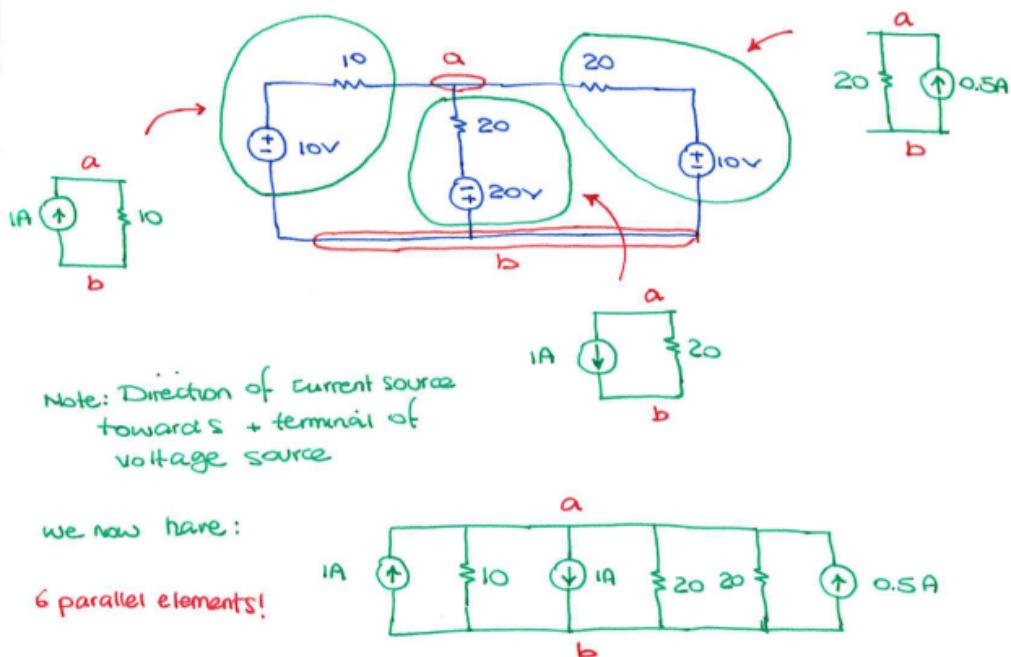
## Source Transformation as a handy simplification



$$R_{eq} = 20\Omega \parallel 20\Omega \parallel 10\Omega = 5\Omega$$

We can combine current sources in parallel (paying attention to directions)

∴ equivalent circuit is :


$$1 - 1 + 0.5 = 0.5A$$

We can also combine voltage sources in series :



## Principle of superposition in circuit analysis

- Given a circuit

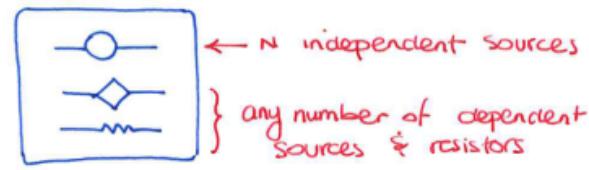

an important (and often required method in AC analysis) is superposition. We first present it in DC circuits.


- Method:
- Let only one independent source be active
  - Zero all other  $N-1$  independent sources
  - Determine the response (voltage or current) at desired location in the circuit. Let this be  $m'$
- Repeat this one independent source at a time to find  $m'', m''', \dots$
- Keep dependent sources ON at all times

Superposition: The total response (voltage or current)  $m$  is the sum of  $N$  individual responses  $m' + m'' + \dots + m^N$


- Ex: Find  $i_x$  by superposition

We have 3 independent sources

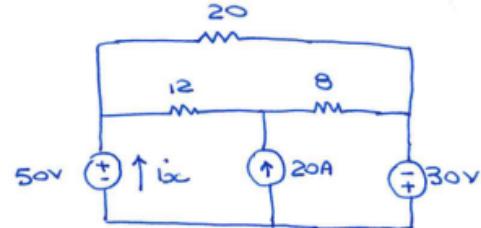
Activate one source at a time, zero the other two.



i) 50V source by itself

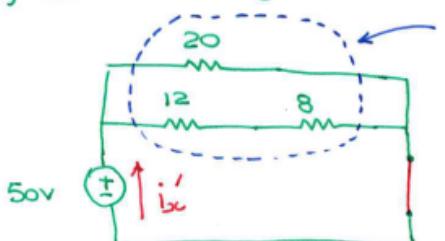


$$(8+12)/20 = 10\Omega$$

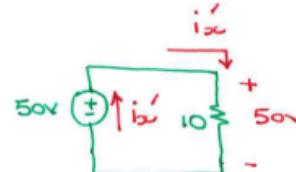

$$i'bx = \frac{50V}{10} = 5A$$

ii) 20A source by itself

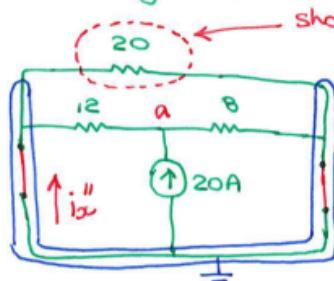

shorted out! Connected to the same node on both ends.


Find  $i''bx$  using method of your choice.

Let's try nodal


$$\text{Node eq at } a: \frac{Va - 0}{12} + \frac{Va - 0}{8} - 20 = 0 \therefore Va = 96V$$

To find  $i''bx$ , use KCL:
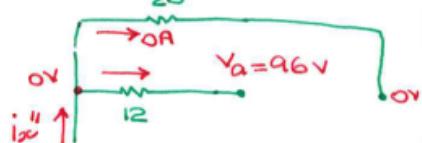
$$-i''bx + \frac{0 - 96}{12} + 0 = 0 \\ \therefore i''bx = -8A$$



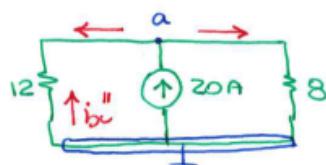• Aside: this circuit can be re-drawn as:




we can find  $i''bx$  using current division:

$$i''bx = -\frac{8}{8+12} \times 20A = -8A$$

direction of  $i''bx$  w.r.t 20A source

iii) 30V source by itself

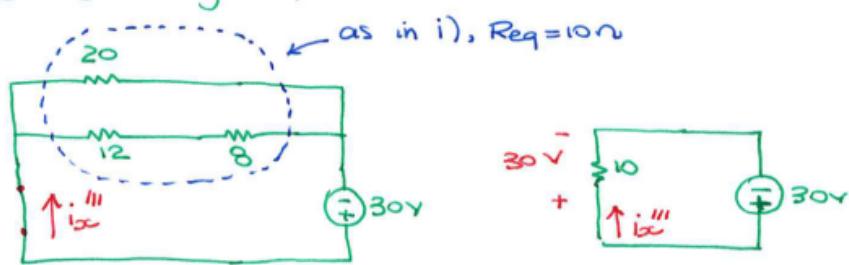

$$i_x''' = \frac{30V}{10\Omega} = 3A$$

Finally, by superposition:  $i_x = i_x' + i_x'' + i_x'''$

$$= 5 - 8 + 3$$
$$= 0 A$$