

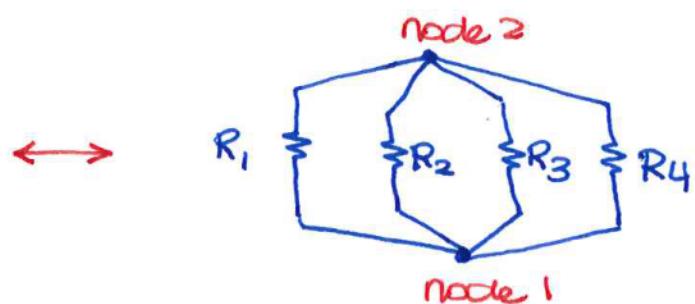


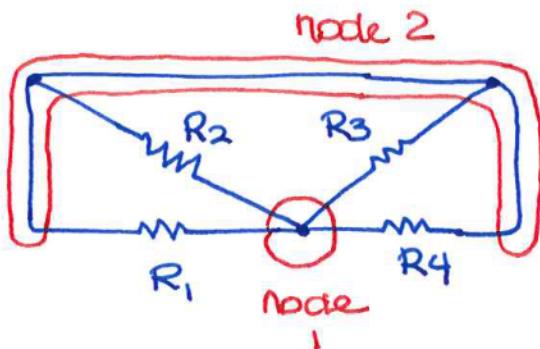- Watch for parallel connections that may not appear like parallel elements at first glance



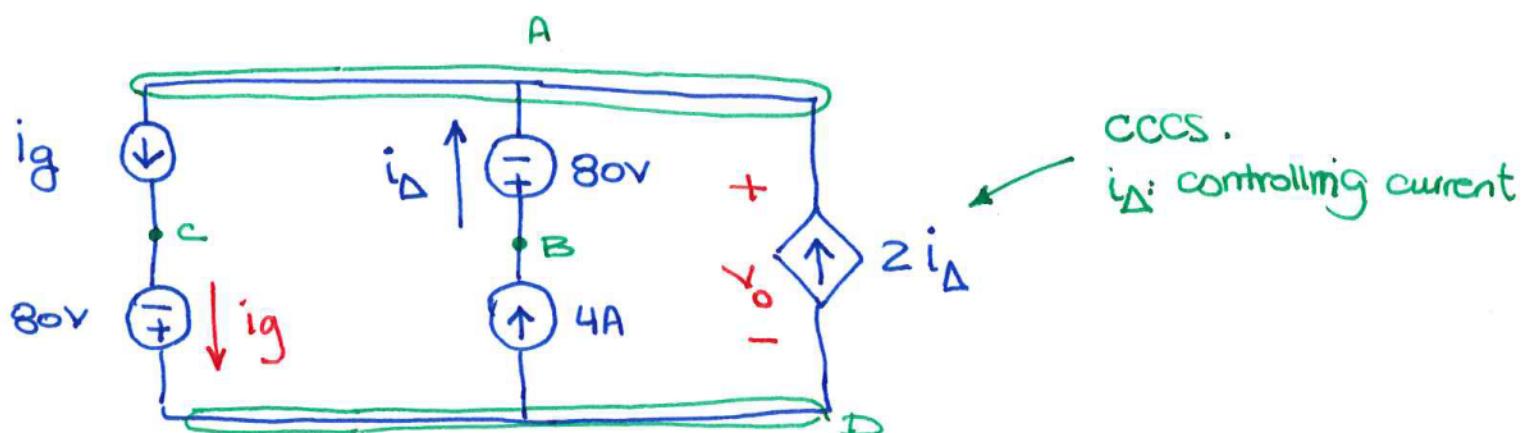Ex: Let  $V_o = 100V$ . Find the power for each element:



Strategy:

- Need all voltages & currents to calculate power
- Use KVL & KCL to find unknown voltages & currents. Assume polarity/direction if unknown.
- Use  $P = vi$  or  $P = -vi$  based on direction of  $i$  & polarity of  $v$  for each element.

$$\text{KCL at node B: } 4 - i_D = 0 \quad \therefore i_D = 4 \text{ A}$$


↑ enter      ↑ leave

$$\text{KCL at node A: } 2i_D + i_D - ig = 0 \quad \therefore ig = 12 \text{ A}$$

↑ enter A from CCCS      ↓ enter A from 80V src      ↓ leaves A

We now have all the currents. Two unknown voltages:

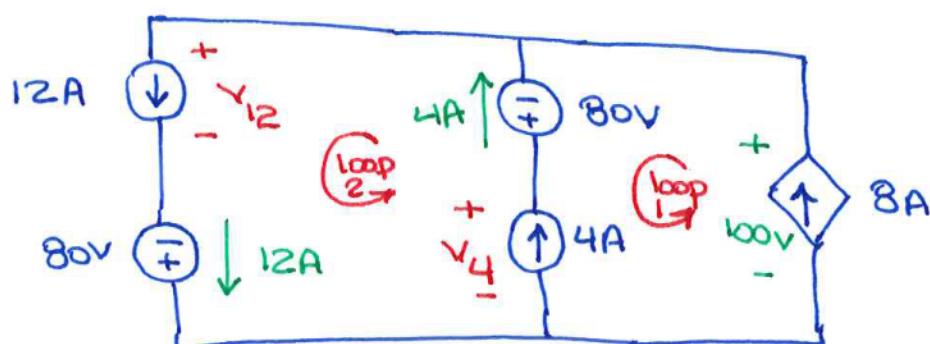$v_4$  &  $v_{12}$ . Assumed a polarity for them.



Choose loop directions arbitrarily.

$$\text{KVL around loop 1: } -100 - 80 + v_4 = 0 \quad \therefore v_4 = 180 \text{ V}$$

$$\text{KVL around loop 2: } -v_4 + 80 + v_{12} = 80 \quad \therefore v_{12} = 180 \text{ V}$$

Element	Power
12 A source	$P = v \cdot i = v_{12} \times 12A = 2160 \text{ W} \leftarrow P > 0.$ Source is absorbing power
left 80V src	$P = -v \cdot i = -(80V)(12A) = -960 \text{ W}$
mid 80V src	$P = v \cdot i = (80V)(4A) = 320 \text{ W}$
4A src	$P = -v \cdot i = -v_4 \times 4A = -720 \text{ W}$
CCCS	$P = -v \cdot i = -(100)(8A) = -800 \text{ W}$
$\sum p = 0 \quad \checkmark \text{ YASSSS}$	
conservation of power/energy	

## Resistive Circuits

We now have all the tools to begin circuit analysis

### Resistors in series

By KVL:

$$-V + V_1 + V_2 + V_3 = 0$$

By Ohm's Law:

$$V_1 = i \cdot R_1$$

$$V_2 = i \cdot R_2$$


$$V_3 = i \cdot R_3$$

$$\therefore -V + iR_1 + iR_2 + iR_3 = 0$$

$$\therefore V = i(R_1 + R_2 + R_3) \xrightarrow{\text{looks like}} V = iR$$


therefore we can replace all resistors in series with an equivalent resistor  $R_{eq}$

Resistors in series add

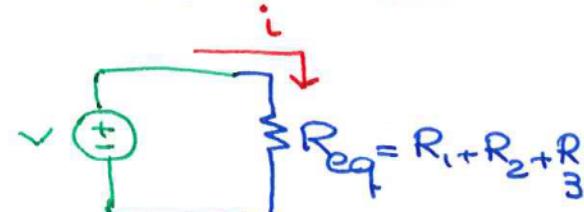
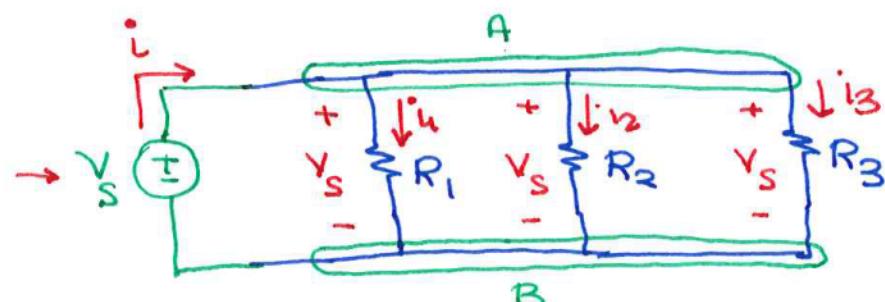
### Resistors in Parallel

common voltage for parallel elements  $\rightarrow V_s$



KCL at node A:  $i - i_1 - i_2 - i_3 = 0$

From Ohm's Law:  $i_1 = \frac{V_s}{R_1}$ ,  $i_2 = \frac{V_s}{R_2}$ ,  $i_3 = \frac{V_s}{R_3}$

$$\therefore i - \frac{V_s}{R_1} - \frac{V_s}{R_2} - \frac{V_s}{R_3} = 0 \quad \therefore i = V_s \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$


common current for series element

$$\therefore V_s = i \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

*Req*

looks like

$$V_s = iR$$




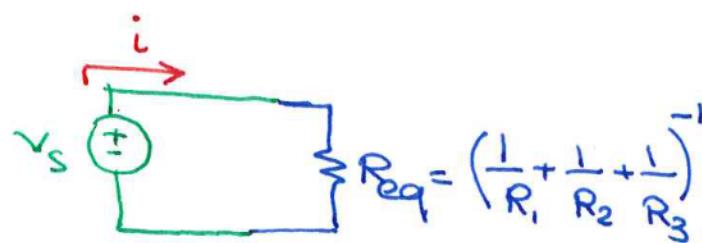


- For 2 resistors in parallel:

$$R_{\text{req}} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

← product  
← sum

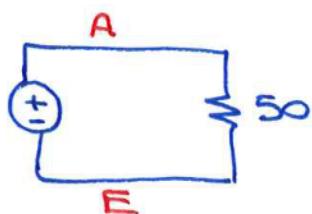
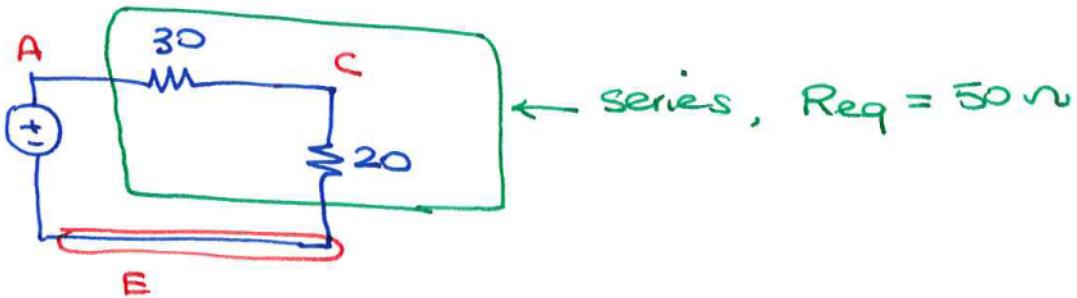
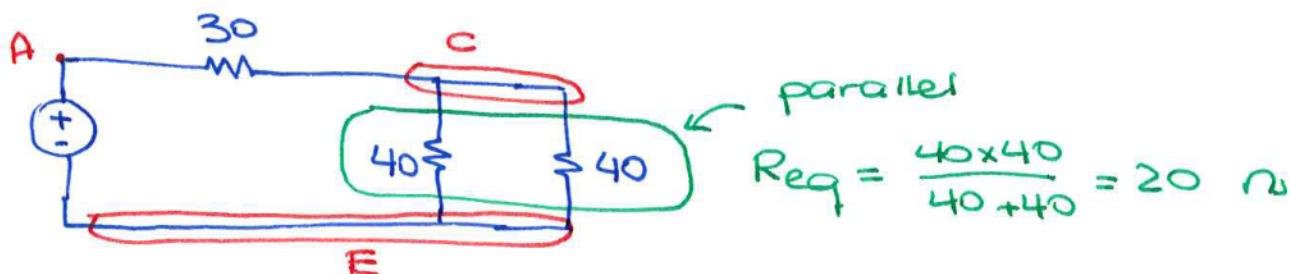
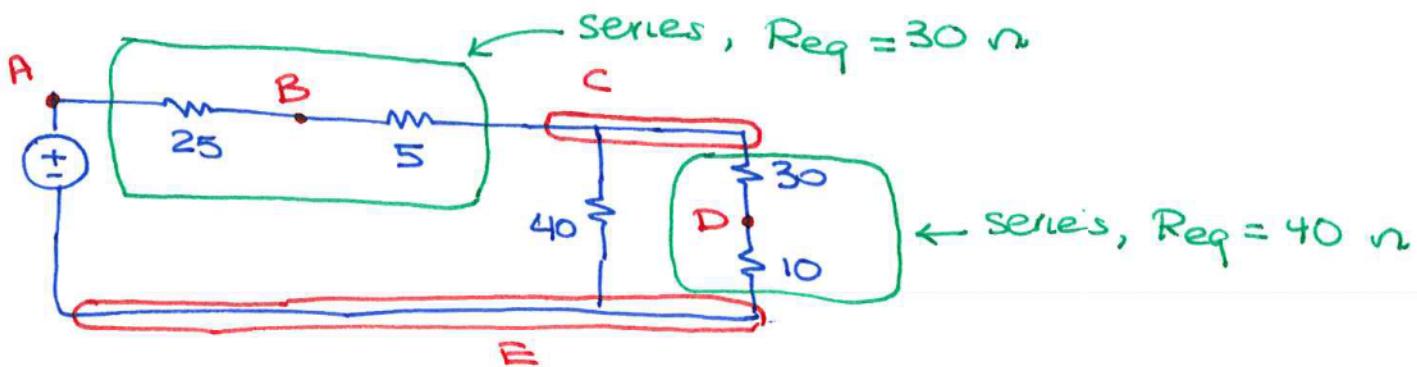
Ex: Find a single equivalent resistance for:



## Circuit Analysis using series /parallel equivalents

- Circuit analysis : Procedure for determining all voltages & currents in every circuit element
- We may use the above resistor equivalents to analyze a circuit.

Ex: Find power in each element

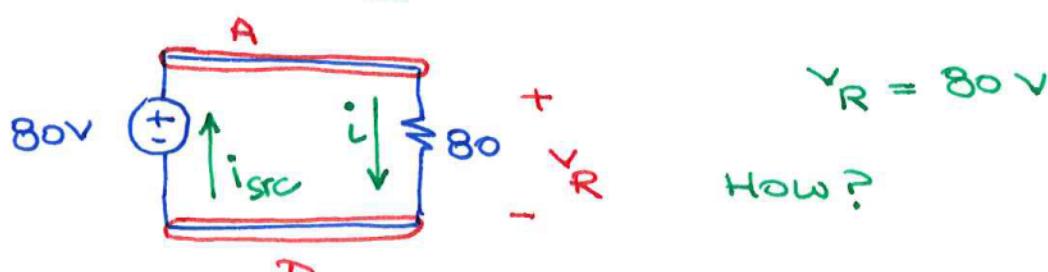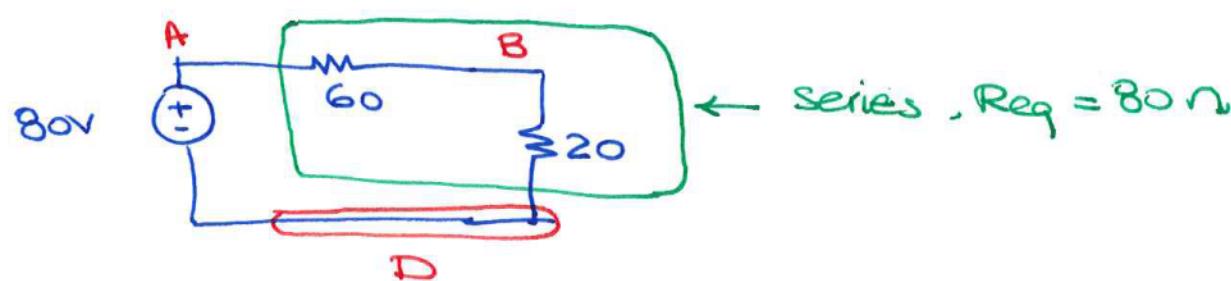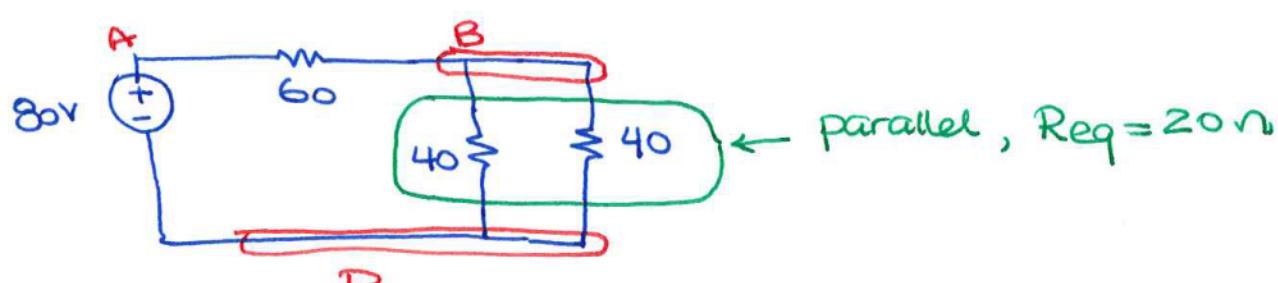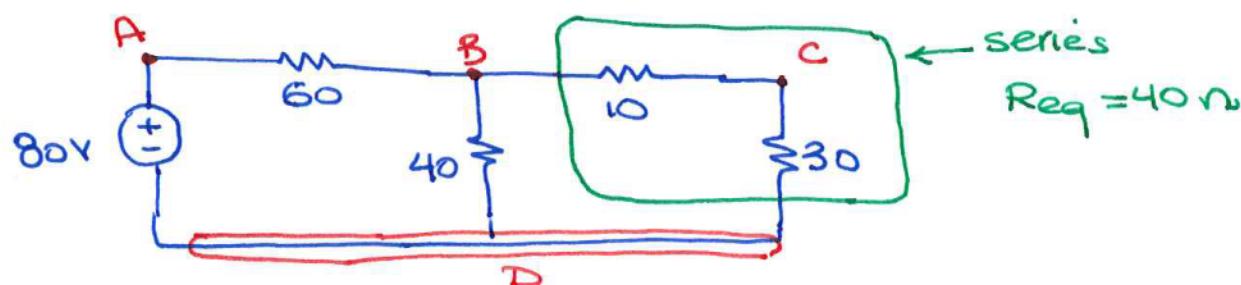


- i) KVL around loop:  $-80 + V_R = 0 \therefore V_R = 80\text{ V}$
- or
- ii) Because of the voltage source, node A is higher than node D by 80V, i.e.  $V_{AD} = 80\text{ V}$   
therefore,  $V_R = V_{AD} = 80\text{ V}$

Now, from Ohm's Law :  $i = \frac{V_R}{80\Omega} = 1 \text{ A}$

To find  $i_{src}$ ; KCL at node A :  $i_{src} - i = 0 \therefore i_{src} = 1 \text{ A}$

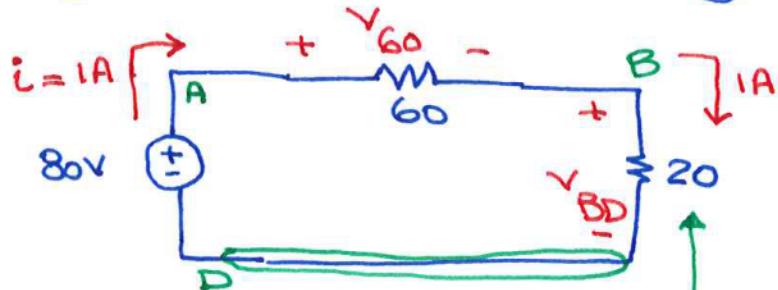Key idea : back to the original circuit, step by step :



this is a combo  
of 3 R's.


When replacing  $R_{eq}$  with original series resistors, these resistors will have the same current as  $R_{eq}$

$$\text{From Ohm's Law: } V_{60} = 60\Omega \times 1\text{ A} = 60\text{ V}$$

$$V_{BD} = 20\Omega \times 1\text{ A} = 20\text{ V}$$

KVL check:
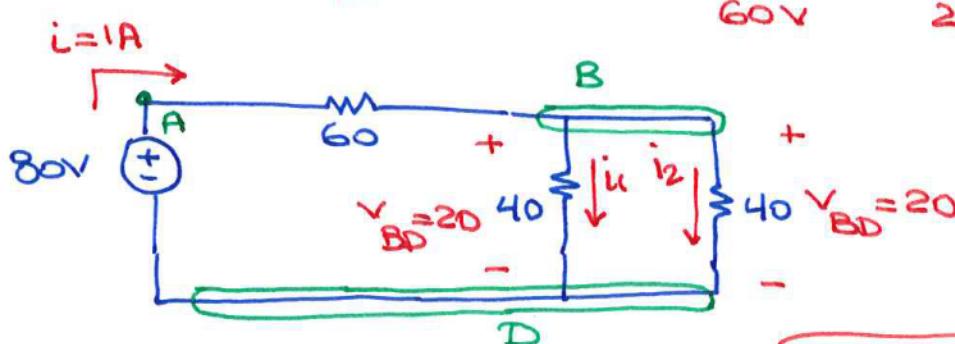
$$-80 + \underbrace{V_{60}}_{60\text{ V}} + \underbrace{V_{BD}}_{20\text{ V}} = 0 \quad \checkmark$$



From Ohm's Law:

$$i = \frac{V_{BD}}{40\Omega} = \frac{20\text{ V}}{40\Omega} = 0.5 \text{ A}$$


$$i_2 = \frac{V_{BD}}{40\Omega} = 0.5 \text{ A}$$

When replacing  $R_{eq}$  with original parallel resistors, they have the same voltage

KCL check at node B:  $\underbrace{i}_{1\text{ A}} - \underbrace{i_1}_{0.5\text{ A}} - \underbrace{i_2}_{0.5\text{ A}} = 0 \quad \checkmark$

replace the right  $40\Omega$  resistor with series  $10\Omega$  &  $30\Omega$  resistors

from orig circuit:

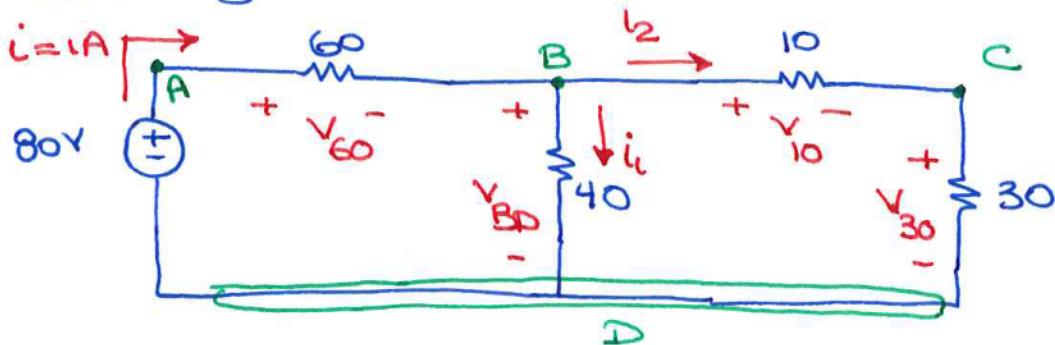

$$\text{From Ohm's Law: } V_{10} = i_2 \times 10 = 5 \text{ V}$$

$$V_{30} = i_2 \times 30 = 15 \text{ V}$$

KVL check around right loop:  $-V_{BD} + V_{10} + V_{30} = 0$  ✓

Now, power:

Element	power	
80V src	$P = -Vi = -(80V)(1A) = -80W$	supplies 80W
$60\Omega$	$P = V_{60} \cdot i = \frac{(V_{60})^2}{60\Omega} = i^2(60\Omega) = 60W$	
$40\Omega$	$P = V_{BD} \cdot i_1 = \frac{V_{BD}^2}{40\Omega} = i_1^2(40\Omega) = 10W$	
$10\Omega$	$P = V_{10} \cdot i_2 = \frac{(V_{10})^2}{10\Omega} = i_2^2(10\Omega) = 2.5W$	
$30\Omega$	$P = V_{30} \cdot i_2 = \frac{(V_{30})^2}{30} = i_2^2 \cdot (30\Omega) = 7.5W$	


$$\sum P = 0 \quad \checkmark$$

Energy balance.

- Later, we will use well-established, systematic methods for analysis: Node Voltage & Mesh Current
- Other simple resistive circuit analysis tools:  
voltage division & current division
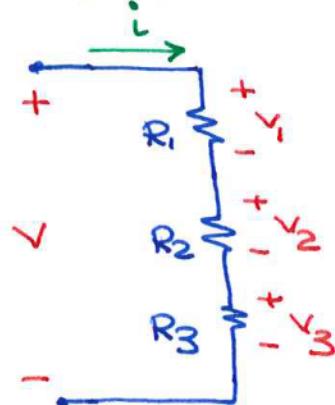
## Voltage Division :


In a series connection of resistors, the total voltage across the series branch of resistors divides among them proportional to their size:



$$R_{\text{eq}} = R_1 + R_2 + R_3$$

Ohm's Law on the right circuit:
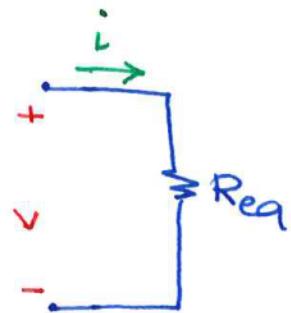
$$i = \frac{V}{R_{\text{eq}}} = \frac{V}{R_1 + R_2 + R_3}$$




Ohm's Law for the left circuit:

$$V_1 = i \cdot R_1 = \frac{V}{R_1 + R_2 + R_3} \cdot R_1 = \frac{R_1}{R_1 + R_2 + R_3} \cdot V$$

i.e.  $R_1$ 's portion of total voltage  $V$  is the same as its portion of total resistance



- total voltage  $V = V_1 + V_2 + V_3$
- If  $V_1, V_2$ , or  $V_3$  have opposite polarity to  $V$ , then add a (-) sign, e.g.
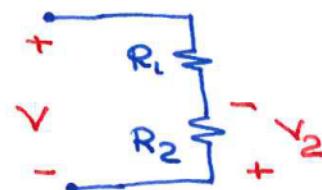
$$V_2 = - \frac{R_2}{R_1 + R_2} \cdot V$$


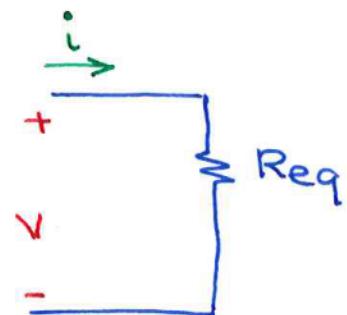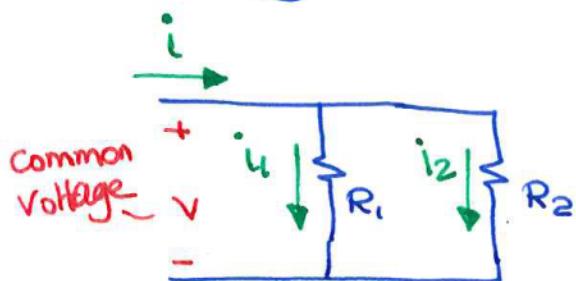
## Current Division

In a parallel connection of resistors, the total current available to the parallel resistors divides among them inversely proportional to their size:



$i$ : total current,  
it can only go through parallel  
resistors  $R_1$  &  $R_2$

$$i = i_1 + i_2$$

$$Req = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$\text{Ohm's Law on the right circuit: } V = i \cdot Req = i \cdot \frac{R_1 \cdot R_2}{R_1 + R_2}$$

Ohm's Law for  $R_1$  on the left circuit:


$$i_1 = \frac{V}{R_1} = \frac{i \cdot \frac{R_1 \cdot R_2}{R_1 + R_2}}{R_1} = \frac{R_2}{R_1 + R_2} \cdot i$$

other branch

i.e.  $R_1$ 's portion of total current  $i$  is the same as  $R_2$ 's portion of total resistance


- Not as easy to apply when there are more than 2 resistors in parallel. We can group resistors to apply current division in this case.

Ex: Find  $i_3$

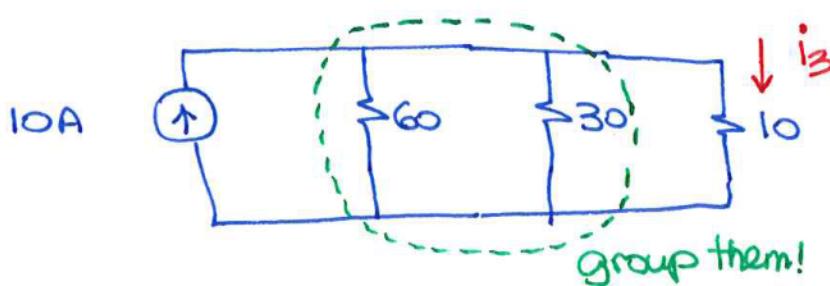

We can't use  $i_3 = \frac{60+30}{60+30+10} \times 10A$

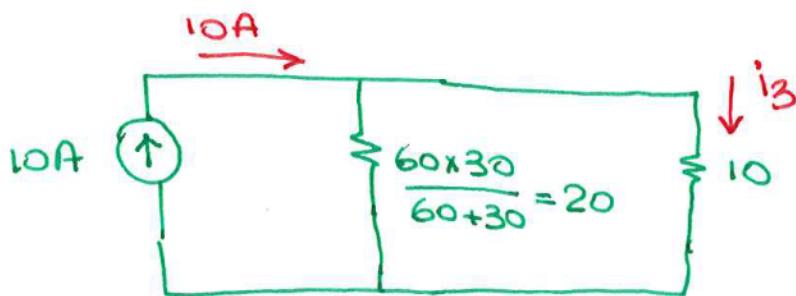
Combine  $60\Omega$  &  $30\Omega$  in parallel:



current division gives:

$$i_3 = \frac{20}{10+20} \times 10A = 6.6A$$

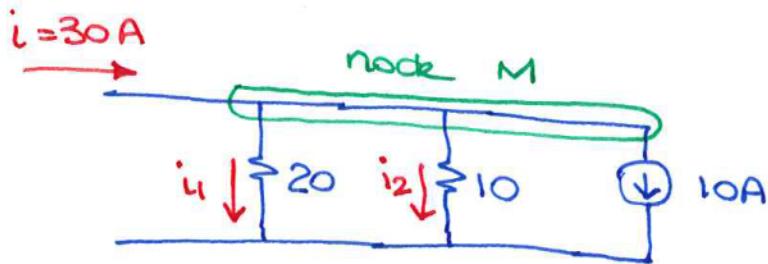Ex 2: How to apply current division here?



To apply current division, we need total current going through parallel resistors:  $\underbrace{i_1 + i_2}_{i_{\text{total}}}$


let's call this  $i_{\text{total}}$

$$\text{KCL at node } M : +30 - i_1 - i_2 - 10 = 0$$

$$\therefore i_{\text{total}} = i_1 + i_2 = 20A$$

$$\text{Now, we can use current div : } i_1 = \frac{10}{10+20} \times i_{\text{total}} = 6.6A$$

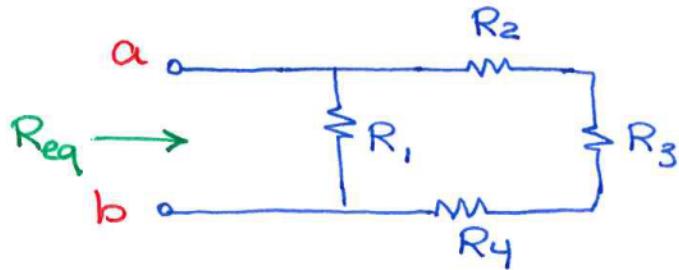Aside: Finding resistance between 2 nodes / points :



can't say  $R_1$  &  $R_2$  are in series because there could be other circuit elements connected to the left side of a & b.

$$Req = R_1 \parallel (R_2 + R_3 + R_4)$$