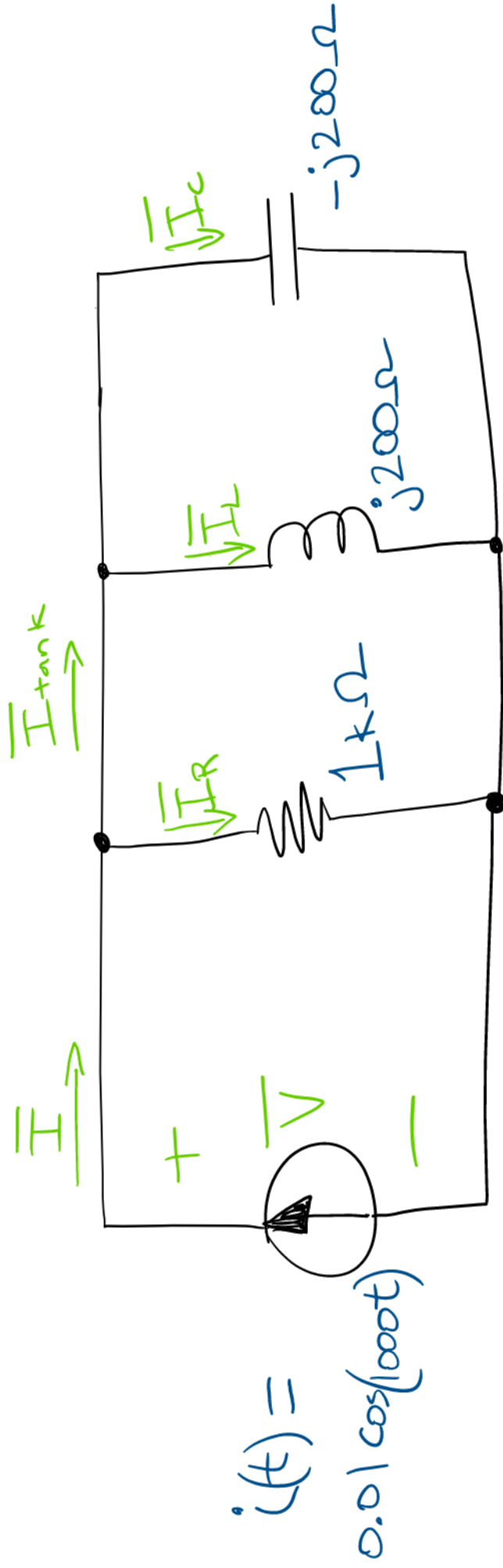


Example

Find the phasor voltage \bar{V} and the phasor currents \bar{I} , \bar{I}_R , \bar{I}_L , \bar{I}_C , and \bar{I}_{tank} .




Example Find the phasor voltage \underline{V} and the phasor currents \underline{I} , \underline{I}_R , \underline{I}_L , \underline{I}_C , and $\underline{I}_{\text{tank}}$.

Solution:


Note: we can observe that

1. The impedances for L and C are given directly ($j200\Omega$ and $-j200\Omega$), so no need to use $\omega = 1000$.

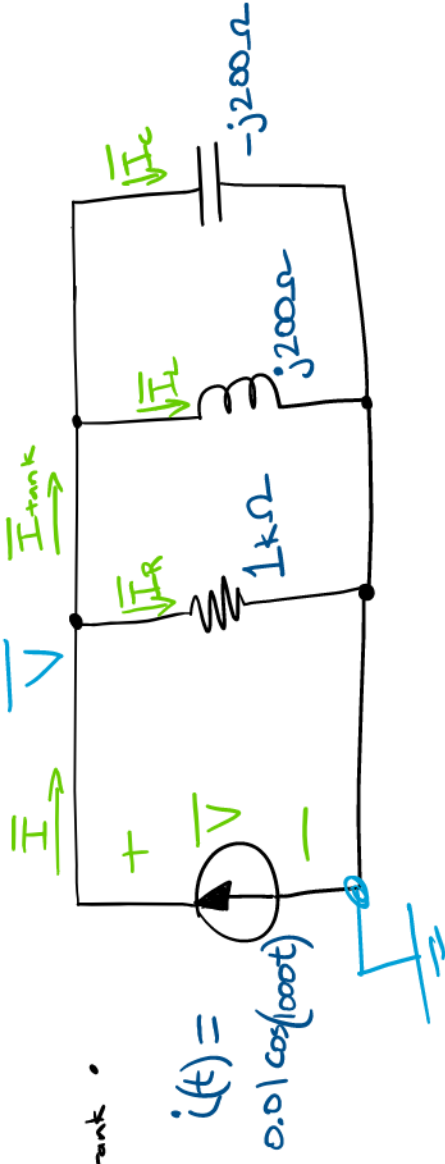2. For node voltage analysis, we can just use \underline{V} to denote the node voltage.



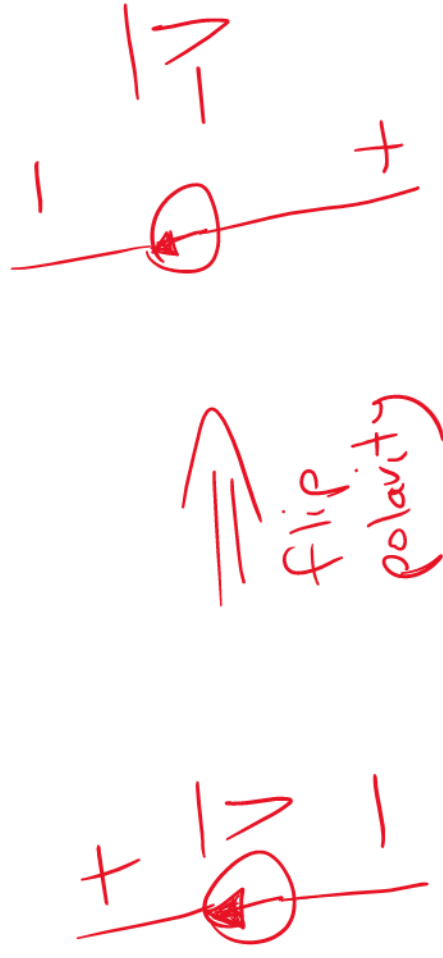Conceptual question:
Does the polarity of \underline{V} matter?



See previous video to understand the difference between \underline{V} and $-\underline{V}$

Example Find the phasor voltage \bar{V} and the phasor currents \bar{I} , \bar{I}_R , \bar{I}_L , \bar{I}_C , and \bar{I}_{tank} .

Convert $i(t)$ to a phasor:

$$i(t) = 0.01 \cos(1000t)$$

$$\bar{I} = 0.01 \angle 0^\circ$$

$$= 0.01$$


Use node voltage analysis to find \bar{V} :

$$-0.01 + \frac{\bar{V}}{1000} + \frac{\bar{V}}{j200} + \frac{\bar{V}}{-j200} = 0$$

$\xrightarrow{1000 \times \frac{1}{-j200} = 1000 \times \frac{j}{200} = j5}$

$$(-1000) \quad -10 + \bar{V} - j5\bar{V} + j5\bar{V} = 0$$

$$\bar{V} = 10 = 10 \angle 0^\circ$$

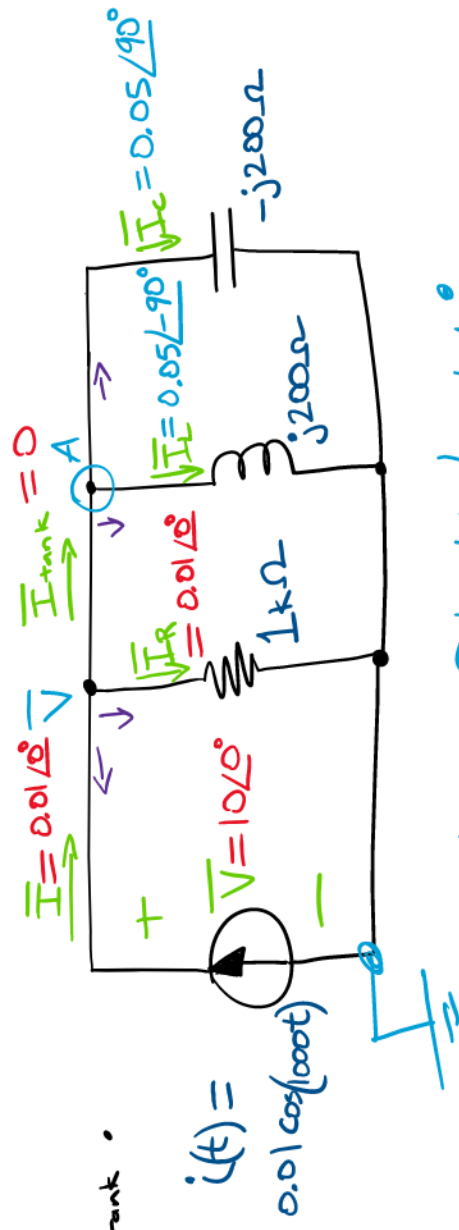

Use Ohm's Law:

$$\bar{I}_R = \frac{\bar{V}}{R} = \frac{10V}{1000\Omega} = 0.01A = 0.01 \angle 0^\circ$$

$$\bar{I}_L = \frac{\bar{V}}{Z_L} = \frac{10V}{j200\Omega} = -j0.05A = 0.05 \angle -90^\circ$$

$$\bar{I}_C = \frac{\bar{V}}{Z_C} = \frac{10V}{-j200\Omega} = j0.05A = 0.05 \angle 90^\circ$$


Use KCL at the connection point A:

$$\bar{I}_{\text{tank}} = \bar{I}_L + \bar{I}_C$$

$$= -j0.05A + j0.05A$$

$$\bar{I}_{\text{tank}} = 0A$$

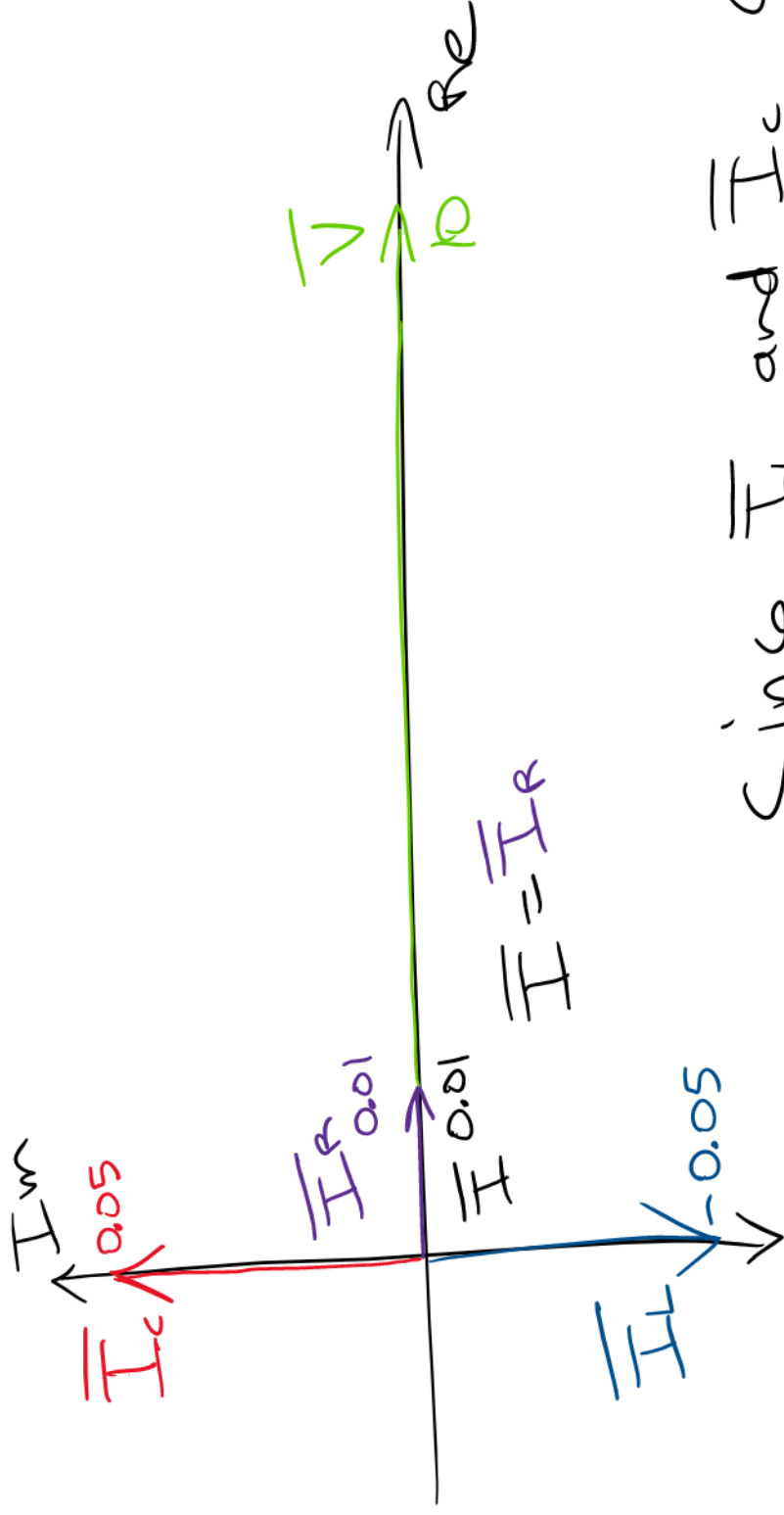Let's draw the current and voltage phasors:



$$\vec{V} = 10 \angle 0^\circ$$

$$\vec{I} = 0.01 \angle 0^\circ$$

$$\vec{I}_R = 0.01 \angle 0^\circ$$

$$\vec{I}_L = 0.05 \angle -90^\circ$$


$$\vec{I}_C = 0.05 \angle 90^\circ$$

$$\vec{I}_{\text{tank}} = 0$$

Since \vec{I}_L and \vec{I}_C cancel each other out,
 \vec{I}_{tank} is 0.

$$\vec{I}_{\text{tank}} = \vec{I}_L + \vec{I}_C = -j200 + j200$$

$$\vec{I}_{\text{tank}} = 0$$

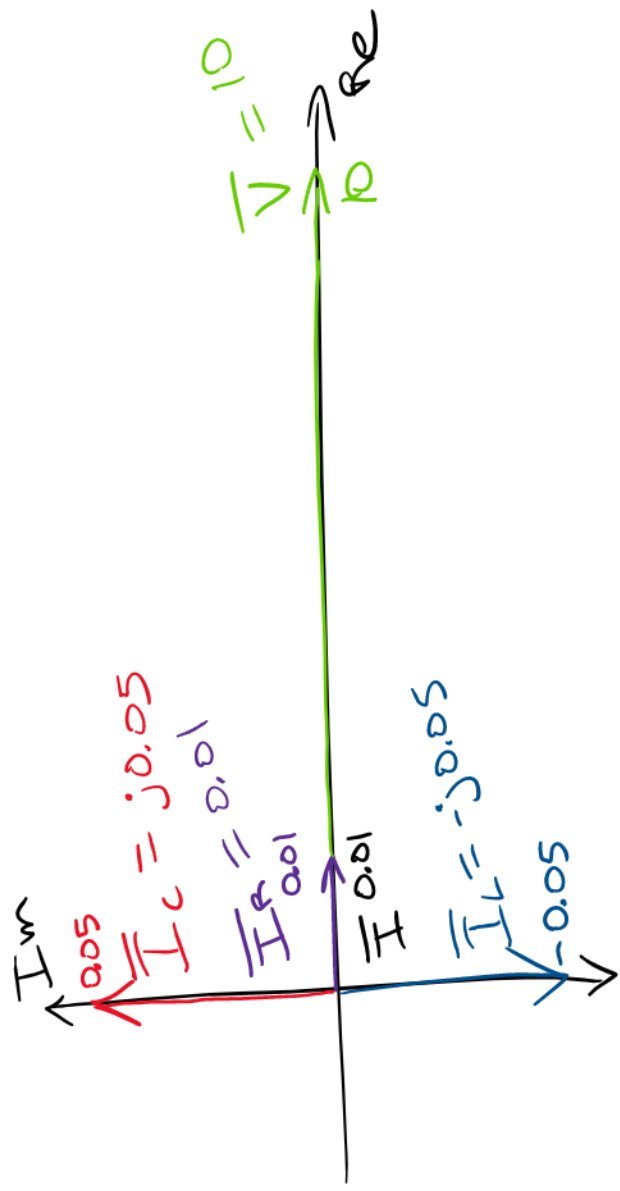

$$\bar{V} = 10 \angle 0^\circ$$


$$\bar{I} = 0.01 \angle 0^\circ$$

$$\bar{I}_R = 0.01 \angle 0^\circ$$

$$\bar{I}_L = 0.05 \angle -90^\circ$$

$$\bar{I}_C = 0.05 \angle 90^\circ$$

$$\bar{I}_{\text{tank}} = 0$$

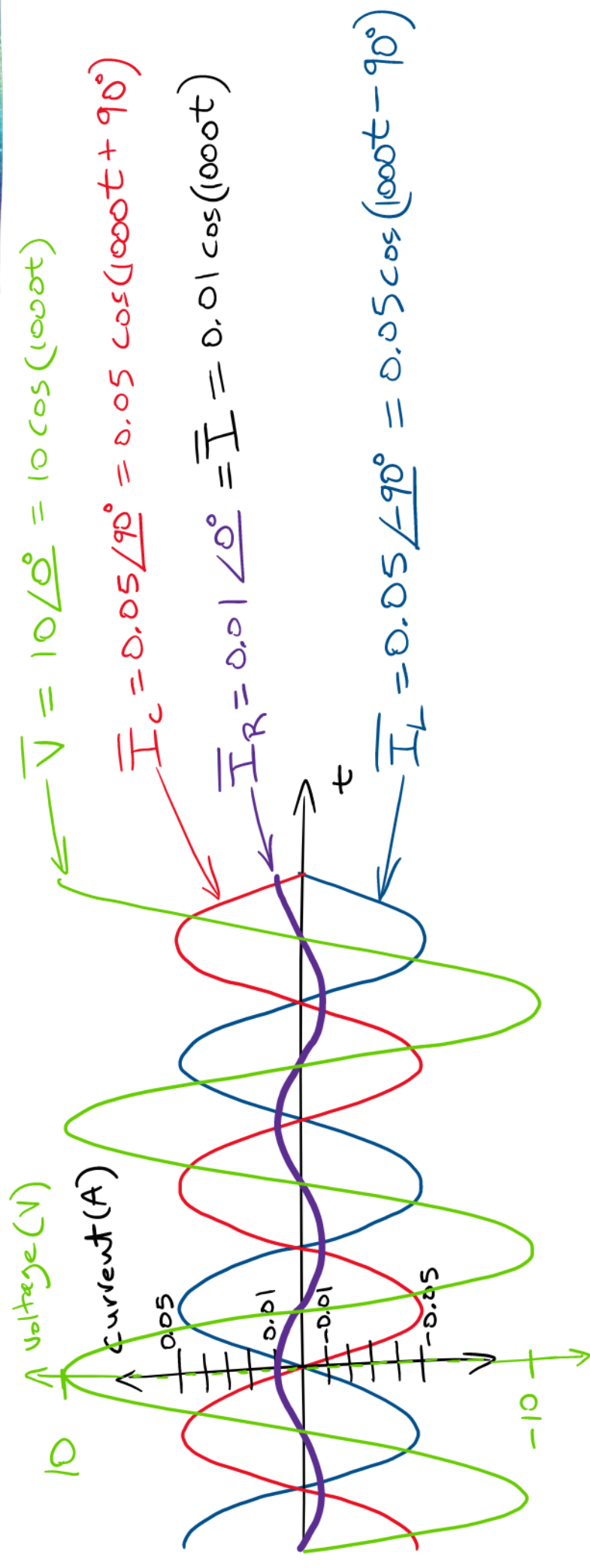


$$\bar{V} = 10 \angle 0^\circ = 10 \cos(1000t)$$

$$\bar{I}_C = 0.05 \angle 90^\circ = 0.05 \cos(1000t + 90^\circ)$$

$$\bar{I}_R = 0.01 \angle 0^\circ = \bar{I} = 0.01 \cos(1000t)$$

$$\bar{I}_L = 0.05 \angle -90^\circ = 0.05 \cos(1000t - 90^\circ)$$

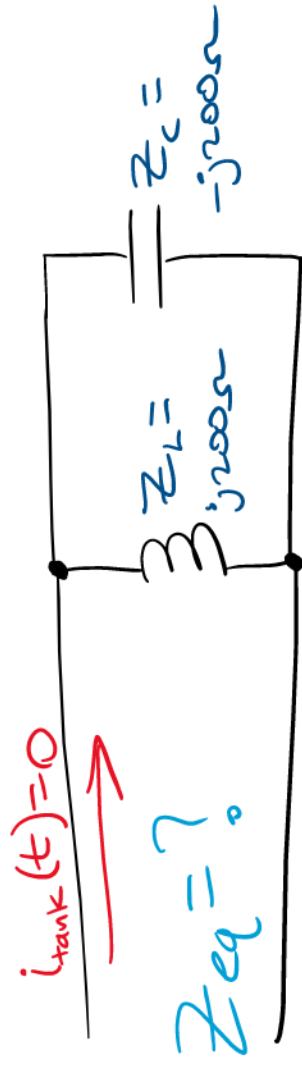Let's consider only the inductor and capacitor in this circuit



How can we
have 0 A current
going into the
L-C circuit?

$$Z_{eq} = \frac{j200 \times (-j200)}{j200 + (-j200)} = \frac{40000}{0} = \frac{1}{0} = \infty$$

So, the parallel combination of the L-C circuit is $\frac{1}{0} = \infty \Omega \Rightarrow$ appears as open-circuit.

But, this is only at the frequency $\omega = 1000$.

This is a special case called parallel resonance.

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{or} \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

where does $\omega_0 = \frac{1}{\sqrt{LC}}$ come from?

For an L-C circuit, the

Z_L is equal in magnitude to Z_C

or

$$Z_L = -Z_C$$

$$Z_L = j\omega L, \quad Z_C = \frac{1}{j\omega C}$$

At resonance frequency, ω_0 ,

Then,

$$j\omega_0 L = -\frac{1}{j\omega_0 C}$$

(x ω_0)

$$\omega_0^2 jL = -\frac{1}{jC}$$


(x -j)

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

→

$$Z_{eq} = +\infty \Omega \text{ at } \omega_0$$

(open-circuit)

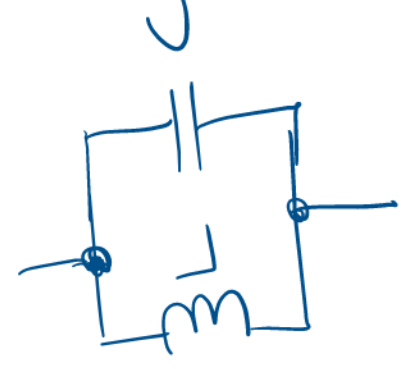

$$Z_{eq} =$$

condition for

$$Z_{eq} = \frac{Z_L Z_C}{Z_L + Z_C}$$

denominator goes to zero.

A series L-C is also interesting



at $\omega_0 = \frac{1}{\sqrt{LC}}$ \rightarrow Series resonance

This L-C circuit appears as a Short-circuit

E.g. $Z_L = j200\Omega$, $Z_C = -j200\Omega$

$$Z_{eq} = Z_L + Z_C = j200 - j200 = 0\Omega$$