
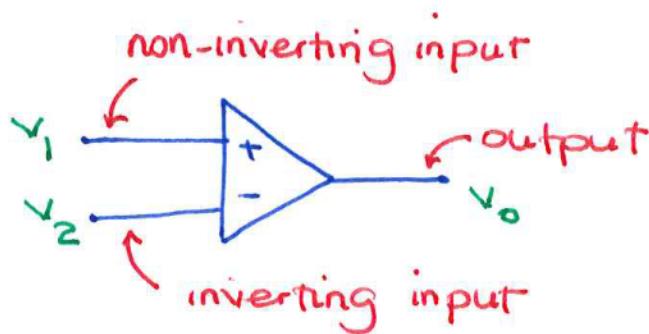


Operational Amplifier

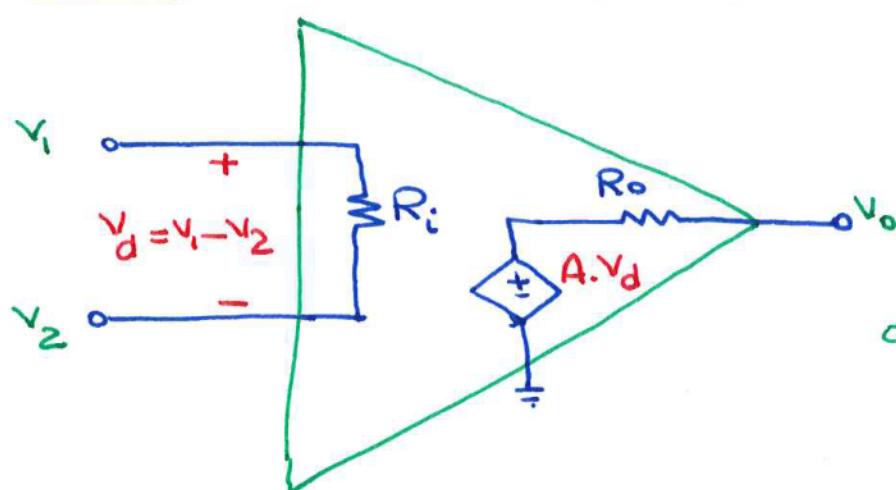- An operational amplifier (op amp) is a complex electronic circuit element that implements a VCVS.
- Many engineering applications:
 - video / audio amplifier
 - Telecommunication
 - Instrumentation (precise measurement devices)
- Circuit symbol:



- The op amp amplifies the difference between input voltages v_d (where $v_d = v_1 - v_2$) : $v_o = A \cdot v_d$
big number!
- The model for a real op amp:




input resistance $R_i \approx 1M\Omega$

output resistance $R_o \approx 50\Omega$

open loop gain $A \approx 10^5$

- The model for an ideal op amp:

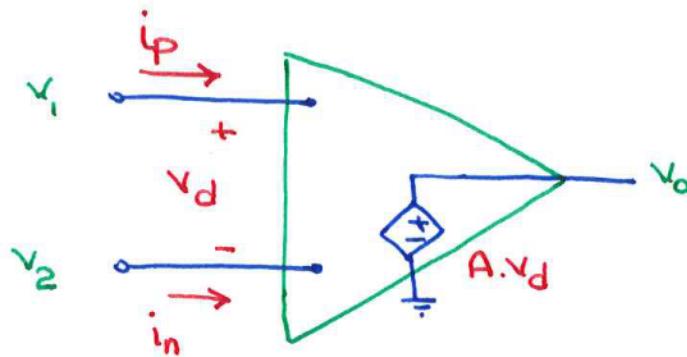

$$R_i = \infty$$


i.e. open circuit seen from the inputs

$$\therefore i_n = i_p = 0$$

$$R_o = 0 \quad (\text{zero output resistance})$$

$$A = \infty \quad (\text{infinite open loop gain})$$

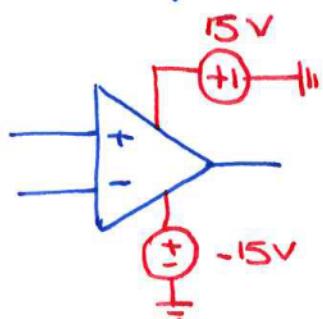- Same behaviour for AC or DC. For now, we will use DC only.
- Since op amp is an electronic circuit, it requires an external source to operate:



when we draw op amp circuits, we seldom draw external power sources. We simply assume they're there!

The Summing Point Constraints


KEY!

- 1) The virtual open circuit: For an ideal op amp, $R_i = \infty$ (open circuit)

therefore, $i_n = i_p = 0$

- 2) the virtual short circuit: For ideal op amp circuits with negative feedback, the 2 input terminals are at the same voltage:


$$v_1 = v_2$$

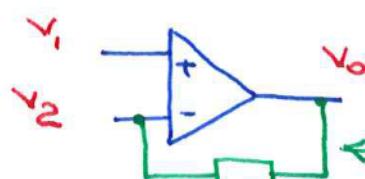

negative feedback (output connected back to - input)

Example: Summing Point Constraints


1) Find v_o

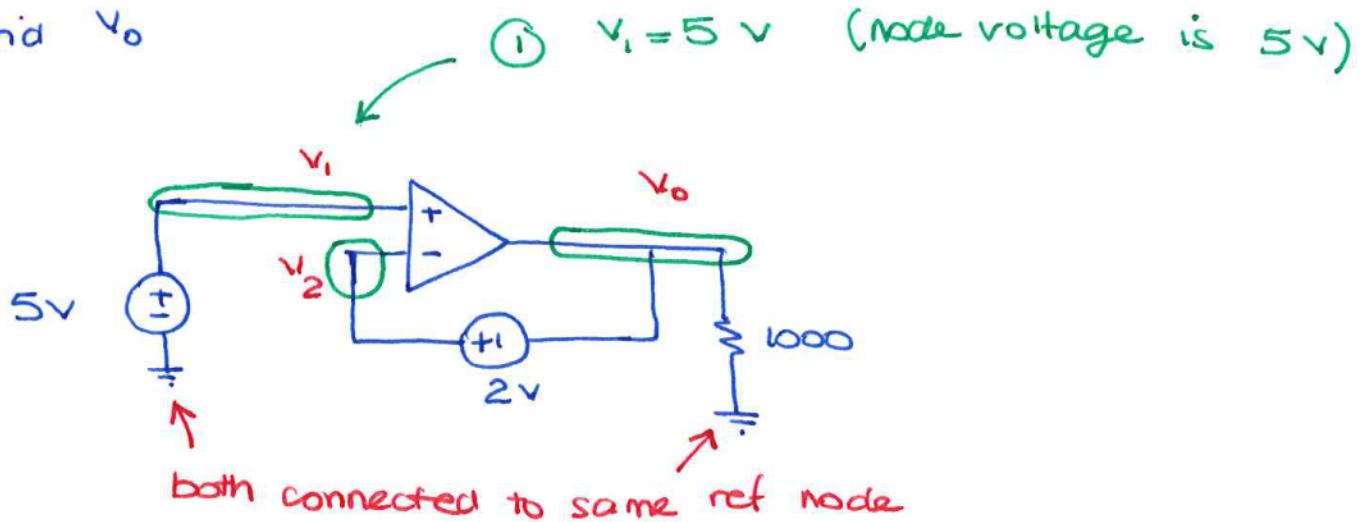

$$② v_2 = 5 \text{ V} \text{ from virtual short } (v_1 = v_2)$$

$$③ v_2 - v_o = 2 \text{ V} \quad \therefore v_o = 5 - 2 = 3 \text{ V}$$

2) Find v_o

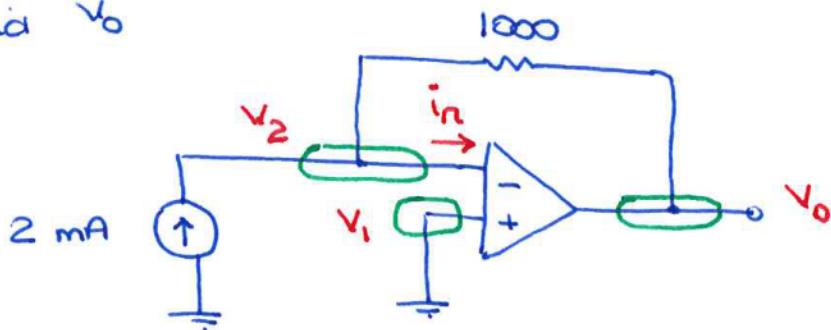

Node 1: + input of op amp

Node 2: - input of op amp

$$① v_1 = 0 \text{ connected directly to ref node}$$

$$② v_2 = v_1 \text{ from virtual short } \therefore v_2 = 0 \text{ V}$$

③ Node eq at 2:

$$-2 \text{ mA} + \frac{v_2 - v_o}{1000} + i_{in} = 0$$

from virtual open

$$\therefore v_o = -2 \text{ V}$$

voltage of output node w.r.t ref

- Easiest way to analyze amplifier circuits:

Tip 1: All the interesting stuff happens at the op amp input terminals. Start there! Take advantage of summing point constraints.

$$V_1 = V_2$$


$$i_n = i_p = 0$$

Tip 2: Node equations at the input terminals tend to simplify the job

Tip 3: Seldom need to write node eq at output node when solving the circuit.

- many interesting & useful circuits can be made with op amps. Some of the basic configurations:

The Inverting Amplifier

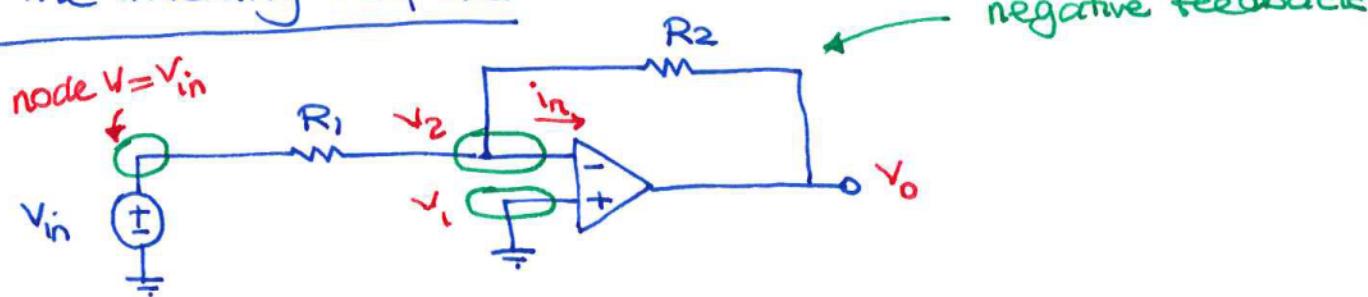

$V_1 = 0$ directly connected to ref node

$V_2 = V_1$ from virtual short $\therefore V_2 = 0$

Node eq at 2: $\frac{V_2 - V_{in}}{R_1} + \frac{V_2 - V_o}{R_2} + \cancel{i_n} = 0$
 0 (virtual open)

$$\therefore -\frac{V_{in}}{R_1} = \frac{V_o}{R_2}$$


$$\boxed{V_o = -\frac{R_2}{R_1} \cdot V_{in}}$$

We often use closed loop gain A_v to define performance of an amplifier circuit

$$A_v = \frac{V_o}{V_{in}}$$

For inverting amplifier circuit, $A_v = \frac{V_o}{V_{in}} = \frac{-R_2}{R_1}$

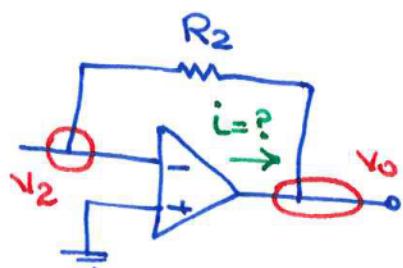Why didn't we write node eq at output node?




$$\frac{V_o - V_2}{R_2} - i = 0$$

↑
an extra unknown.

If we need to find i , we can use this equation after we've found all the node voltages.

Another Inverting Amplifier

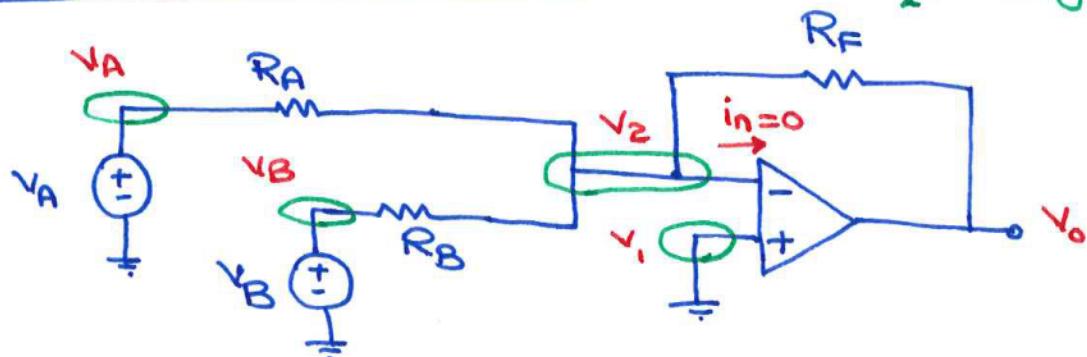

$$v_2 = v_1 = 0$$

virtual short

Node eq at 2:

$$\frac{v_2 - v_A}{R_A} + \frac{v_2 - v_B}{R_B} + \frac{v_2 - v_o}{R_F} + \frac{v_o}{R_F} = 0$$


$$\therefore \frac{v_o}{R_F} = \frac{-v_A}{R_A} - \frac{v_B}{R_B}$$

$$\therefore v_o = \frac{-R_F}{R_A} \cdot v_A + \frac{-R_F}{R_B} \cdot v_B$$

If we choose $R_A = R_B = R$, then $v_o = -\frac{R_F}{R} (v_A + v_B)$

This would be an inverting summing amplifier
e.g. part of an audio mixing circuit

The non-inverting amplifier

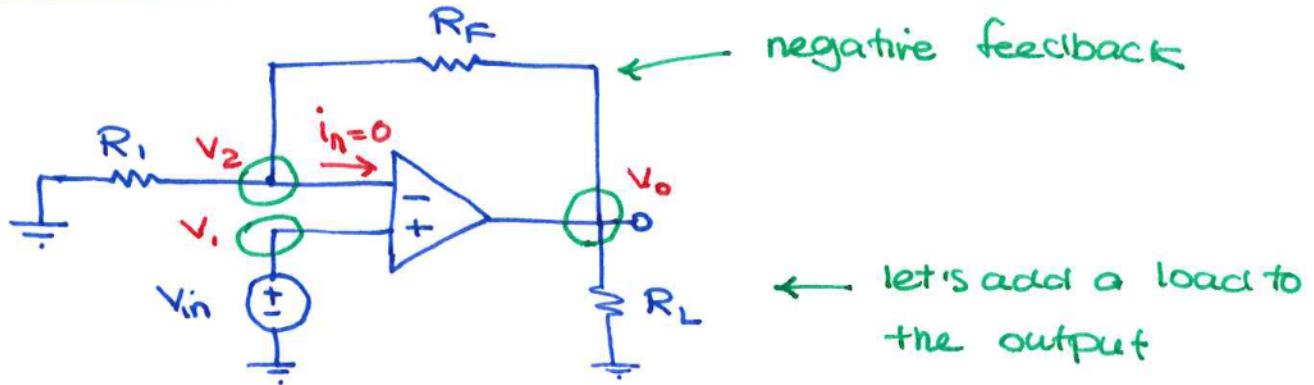

This is similar to the inverting amplifier except V_{in} is moved to the + terminal

voltage source V_{in} between node 1 & ref

$$V_2 = V_1 = V_{in}$$

virtual short

$$\frac{V_{in}}{R_1} - 0$$

$$\frac{V_{in}}{R_F} - V_o + i_n = 0$$


Node eq at 2:

$$\therefore \frac{V_{in}}{R_1} + \frac{V_{in} - V_o}{R_F} = 0 \quad \therefore V_o = \left(1 + \frac{R_F}{R_1}\right) \cdot V_{in}$$

Closed loop gain $A_v = \frac{V_o}{V_{in}} = 1 + \frac{R_F}{R_1}$ ← note:
positive
gain

Note that R_L has no effect on closed loop gain of this (or any other) amplifier circuit

The Differential Amplifier Circuit

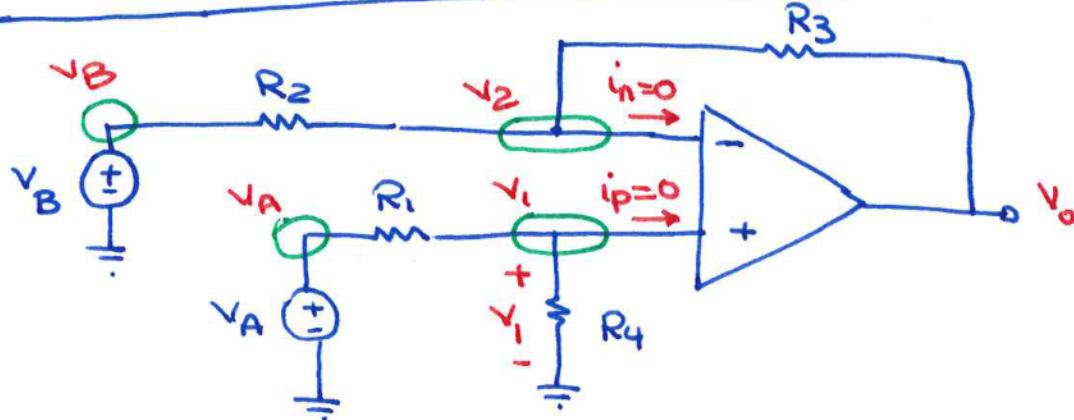


Node eq at 1: $\frac{v_i - v_A}{R_1} + \frac{v_i - 0}{R_4} + \cancel{i_p} = 0$

$$\therefore v_i = v_A \left(\frac{R_4}{R_1 + R_4} \right) \quad (i)$$

Note that this is a voltage division equation

How?

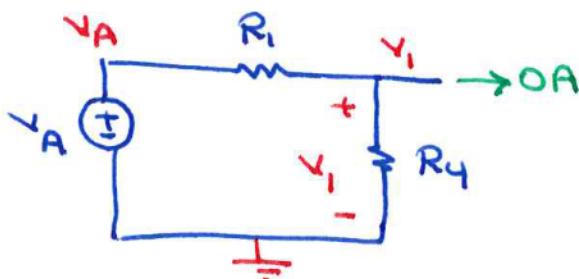

Since $i_p = 0$, R_1 & R_4 share the same current

i.e. look like series resistors $\therefore v_i = \frac{R_4}{R_1 + R_4} \cdot v_A$

Node eq at 2: $\frac{v_2 - v_B}{R_2} + \frac{v_2 - v_o}{R_3} + \cancel{i_h} = 0 \quad (ii)$

$v_1 = v_2$ therefore, we can plug in (i) into (ii) to get:

$$v_o = \left(\frac{R_2 + R_3}{R_2} \right) \left(\frac{R_4}{R_1 + R_4} \right) \cdot v_A - \left(\frac{R_3}{R_2} \right) \cdot v_B$$

If we choose $\frac{R_3}{R_2} = \frac{R_4}{R_1}$, then it can be shown that:

$$v_o = \frac{R_3}{R_2} (v_A - v_B)$$

← amplifies the difference between input voltages
 $v_A \neq v_B$

3. [22 marks.] The op-amps in Fig. P3 are ideal and are operating in their linear regions.

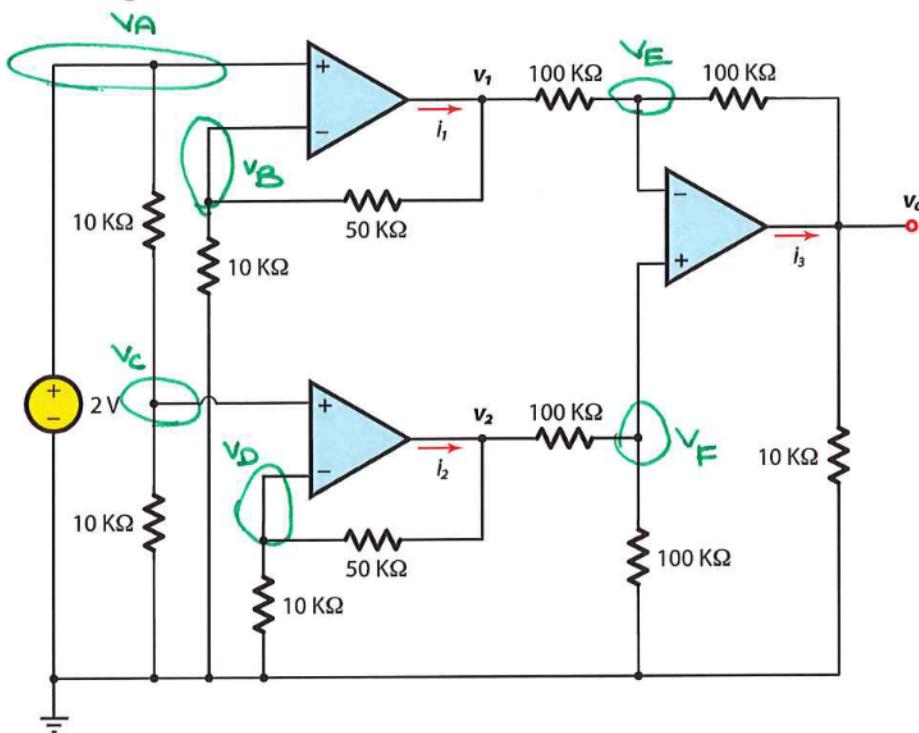


Fig. P3. Find v_1 , v_2 , v_0 , then i_1 , i_2 , i_3 .

- (a) [6] Determine node voltages v_1 and v_2 .
- (b) [8] Determine the output voltage v_0 .
- (c) [8] Determine the op-amp output currents i_1 , i_2 , and i_3 .

Ex: 2013 Final exam, Q3

a) $v_A = 2 \text{ V}$ (2V source between node A & ref node)

$$v_B = v_A = 2 \text{ V}$$

virtual short

Node eq at B: $\frac{2 - v_i}{50\text{K}} + \frac{2 - v_B}{10\text{K}} + 0 = 0$ virtual open

$$\times 50\text{K}: 2 - v_i + 10 = 0 \quad \therefore v_i = 12 \text{ V}$$

Node eq at C: $\frac{v_c - v_A}{10\text{K}} + \frac{v_c - 0}{10\text{K}} + 0 = 0$ virtual open

$$\therefore v_c = 1 \text{ V}$$

$$v_D = v_c = 1 \text{ V} \quad \text{from virtual short}$$

Node eq at D: $\frac{v_D - 0}{10\text{K}} + \frac{v_D - v_2}{50\text{K}} + 0 = 0$

$$\therefore v_2 = 6 \text{ V}$$

b) Node eq at F: $\frac{v_F - v_2}{100\text{K}} + \frac{v_F - 0}{100\text{K}} + 0 = 0$


$$\therefore v_F = 3 \text{ V}$$

$$v_E = v_F = 3 \text{ V} \quad \text{from virtual short}$$

Node eq at E: $\frac{v_E - v_1}{100\text{K}} + \frac{v_E - v_o}{100\text{K}} + 0 = 0$

$$\therefore v_o = -6 \text{ V}$$

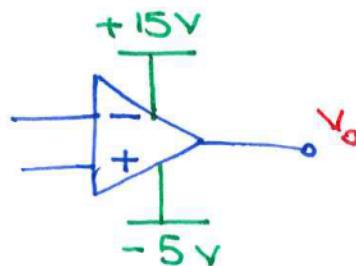Modification: what if op amp 3 looked like this:



the output of this op amp must remain in the range:

$-5 \leq V_o \leq +15$. In this case, op amp 3 is "saturated" (not in linear region) $\therefore V_o = -5 \text{ V}$

c) KCL at node 1:

$$-i_1 + \frac{v_1 - v_E}{100k} + \frac{v_1 - v_B}{50k} = 0$$

$$\therefore i_1 = 0.29 \text{ mA}$$

KCL at node 2:

$$-i_2 + \frac{v_2 - v_F}{100k} + \frac{v_2 - v_D}{50k} = 0$$

$$\therefore i_2 = 0.13 \text{ mA}$$


KCL at V_o node:

$$-i_3 + \frac{v_o - v_E}{100k} + \frac{v_o - 0}{10k} = 0$$

$$\therefore i_3 = -0.69 \text{ mA}$$

Another application of opamps: comparator


• Consider an inverting amplifier:

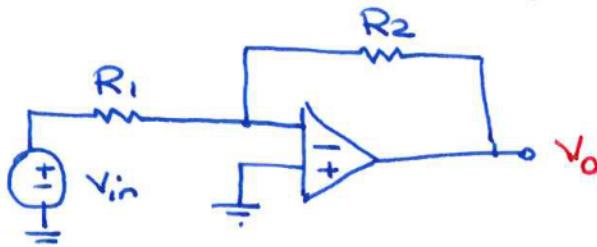

$$\text{we showed that } V_o = \frac{-R_2}{R_1} \cdot V_{in}$$


Resistor R_2 is a critical component here. It provides negative feedback to allow this circuit to operate. (allows us to use) $V_1 = V_2$

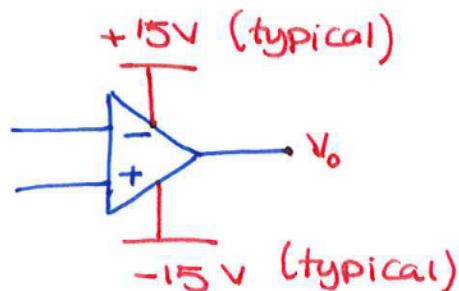- Also, recall that op amp itself requires an external power source to operate:




With external power sources as shown, V_o is allowed to be in the range $-15 \leq V_o \leq 15$

- Now, suppose R_2 is removed:

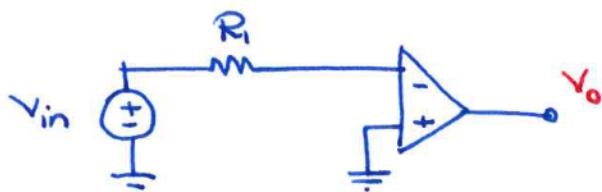


this means that we are operating the op amp open loop.

Using the ideal op amp model:

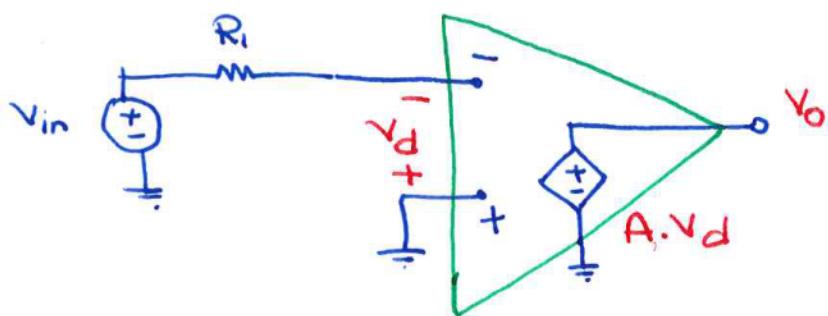

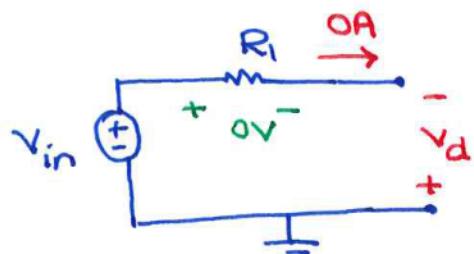KVL : Sum of voltages around the loop connected to the input:



$$-V_{in} - v_d = 0 \quad \therefore \quad v_d = -V_{in}$$

i.e. cannot use virtual short ($V_1 = V_2$ or $v_d = 0$) in open loop operation

Output voltage v_o is given by:

$$v_o = \underbrace{A \cdot v_d}_{\text{open loop gain. Big number!}} = -A \cdot v_{in} \quad (\infty \text{ for ideal op amp})$$

v_{in} between output node & ref node

$$\begin{cases} \text{if } v_{in} < 0, \quad v_o = + [\text{big number}] \\ \text{if } v_{in} > 0, \quad v_o = - [\text{big number}] \end{cases}$$


here, [big number] is limited by external power sources:

$$\therefore \begin{cases} \text{if } v_{in} < 0, \quad v_o = +15 \text{ V} \\ v_{in} > 0, \quad v_o = -15 \text{ V} \end{cases} \quad \text{operates only at extremes.}$$

- This behaviour makes op amps useful as voltage comparators.
(See Lab 3).


Op amp example with voltage signals

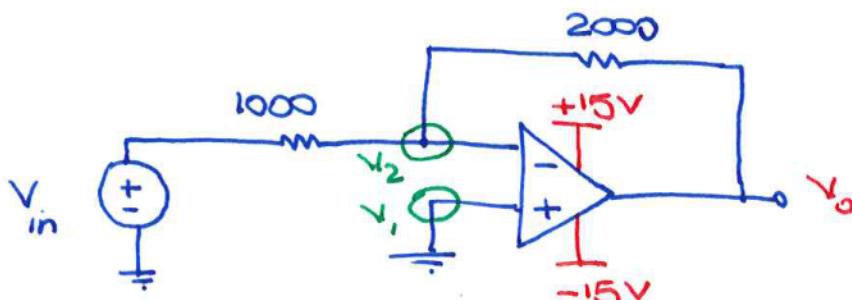- Consider the following inverting amplifier:



$v_{in}(t)$ is given as:

Draw $v_o(t)$.

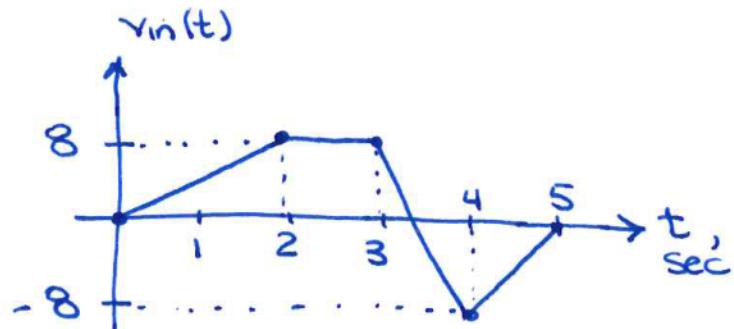

First, write v_o in terms of v_{in} :

direct to GND

$$\underbrace{v_1 = v_2 = 0}_{\text{virtual short}}$$

Node eq at 2 : $\frac{v_2 - v_{in}}{1000} + \frac{v_2 - v_o}{2000} = 0 \therefore v_o = -2v_{in}$

