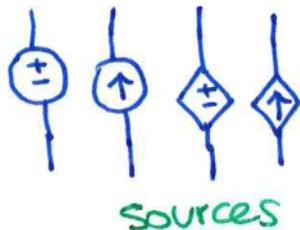


Inductors & Capacitors


- So far, we have considered the following circuit elements:



sources



resistor

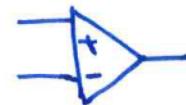



op amp

Inductors & capacitors are dependent on electromagnetic fields:

- capacitor: separation of charge produces electric field
- inductor: Motion of charge produces magnetic field

- Unlike resistors, these devices can store energy & return stored energy, but are not producers of energy.

Capacitor

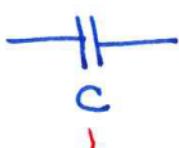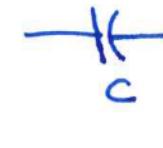- The circuit symbol is  or 

circuit parameter for capacitance

- Voltage-current relationship:



$$i(t) = C \frac{dV(t)}{dt}$$

v: Voltages in Volts (V)

i: Current in Amps (A)

t: time in seconds (s)


C: capacitance in Farads (F)

Capacitor Properties

- 1) Constant voltage across capacitor terminals results in zero current flow. Capacitor looks like open circuit in DC

$$i(t) = C \frac{dv(t)}{dt} = 0 \text{ when } v(t) \text{ is constant, as in DC}$$

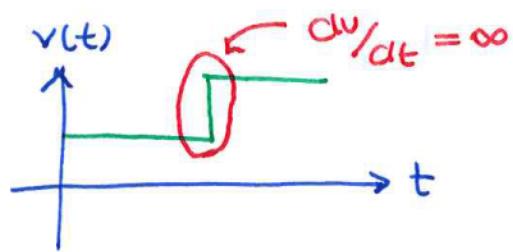- 2) Voltage cannot change instantaneously; current would be infinite



capacitor won't allow this as it would require ∞ current

- . Capacitor voltage in terms of current:

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

τ is just an integration variable. The current will be expressed as a function of time, $i(t)$. In the integral above, we are using t as the end point so we will write current as a function of τ for the integral only.

e.g.: $i(t) = 10t$ then $v(t) = \frac{1}{C} \int_{t_0}^t 10\tau d\tau + v(t_0)$

More on this later!

Power & Energy in capacitor

We can write an expression for power:

$$P(t) = V(t) \cdot i(t)$$



if current is labelled in dir of voltage drop
(Sees + terminal first)

$$= V(t) \cdot C \cdot \frac{dV(t)}{dt}$$

$$= i(t) \left[\frac{1}{C} \int_{t_0}^t i(z) \cdot dz + V(t_0) \right]$$

For energy, recall $P(t) = \frac{dW(t)}{dt}$

$$\text{for capacitors, } P(t) = \frac{dW(t)}{dt} = C \cdot V(t) \cdot \frac{dV(t)}{dt}$$


$$\therefore dW(t) = C \cdot V(t) \cdot dV(t)$$

integrate both sides :

$$W(t) = \frac{1}{2} C V(t)^2$$

Capacitors in Series & parallel

In parallel:

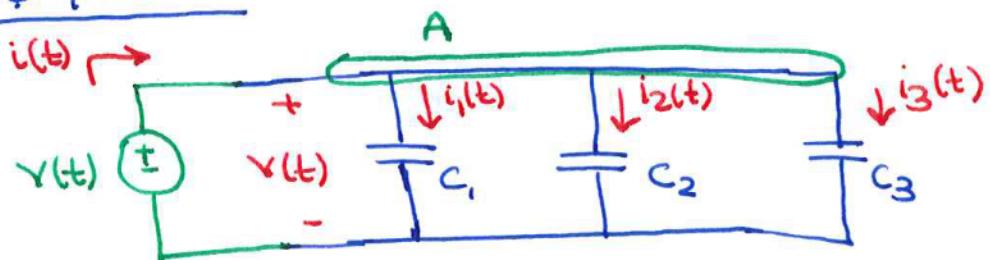


KCL at node A:

$$i = i_1(t) + i_2(t) + i_3(t) = C_1 \frac{dV(t)}{dt} + C_2 \frac{dV(t)}{dt} + C_3 \frac{dV(t)}{dt}$$

$$= (C_1 + C_2 + C_3) \frac{dV(t)}{dt}$$

$$= C_{eq} \cdot \frac{dV(t)}{dt}$$

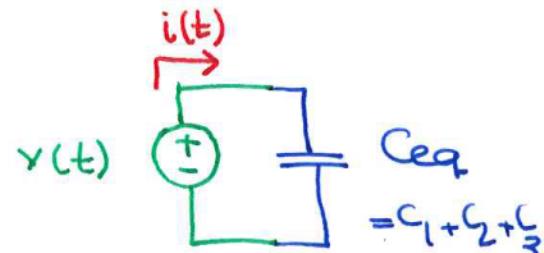

We can write:


$$C_{eq} = C_1 + C_2 + C_3$$

caps in parallel add

In Series :

From KVL :


$$v(t) = v_1(t) + v_2(t) + v_3(t)$$

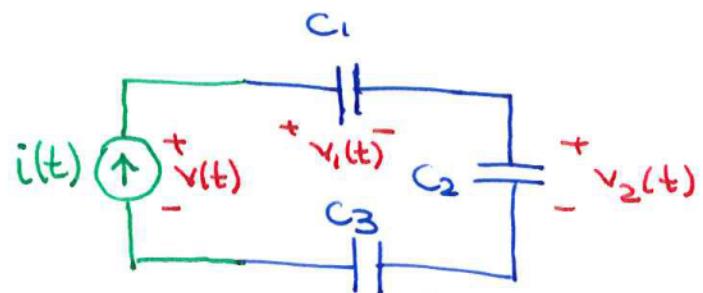



$$\begin{aligned} &= \frac{1}{C_1} \int_0^t i(\tau) d\tau + \frac{1}{C_2} \int_0^t i(\tau) d\tau + \frac{1}{C_3} \int_0^t i(\tau) d\tau \\ &= \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right) \int_0^t i(\tau) d\tau = \frac{1}{C_{eq}} \int_0^t i(\tau) d\tau \end{aligned}$$

$$\therefore C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$$

Add series caps like parallel resistors

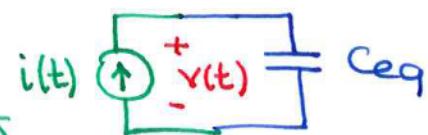

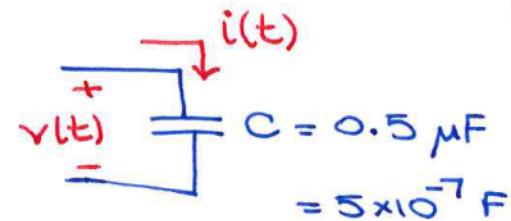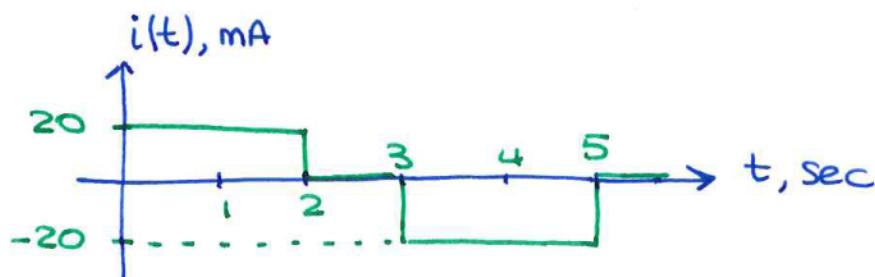Ex: Find cap voltage for given current. Assume no initial voltage on capacitor.



$$\text{For a capacitor, } v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

$$\text{For this capacitor, } i(t) = \begin{cases} 20 \text{ mA} & 0 < t < 2 \\ 0 & 2 < t < 3 \\ -20 \text{ mA} & 3 < t < 5 \\ 0 & t > 5 \end{cases}$$

$0 < t < 2$: $i(t) = 0.02$

$$v(t) = \frac{1}{5 \times 10^{-7}} \int_0^t (0.02) dz + v(0)$$

start of interval

$$= \frac{0.02}{5 \times 10^{-7}} \cdot z \Big|_0^t = 40000(t-0) = 40000t$$

$2 < t < 3$: $i(t) = 0$

$$v(t) = \frac{1}{5 \times 10^{-7}} \int_2^t 0 \cdot dz + v(2)$$

voltage across cap at
start of this interval

from previous interval:

$$v(2) = 40000 \times 2 = 80000 \text{ V}$$

$$\therefore v(t) = 80000 \text{ V}$$

$3 < t < 5$ $i(t) = -0.02$

voltage at the end of last interval = 80000 V

$$v(t) = \frac{1}{5 \times 10^{-7}} \int_3^t (-0.02) dz + v(3)$$

$$= \frac{-0.02}{5 \times 10^{-7}} \cdot z \Big|_3^t + 80000$$

$$= -40000(t-3) + 80000$$


$$= -40000t + 200000$$

$t > 5$ $i(t) = 0$

$v(t)$ remains constant at initial value of $v(5)$

From prev. interval, $v(5) = -40000 \times 5 + 200000 = 0$

Let's sketch $v(t)$, $p(t)$

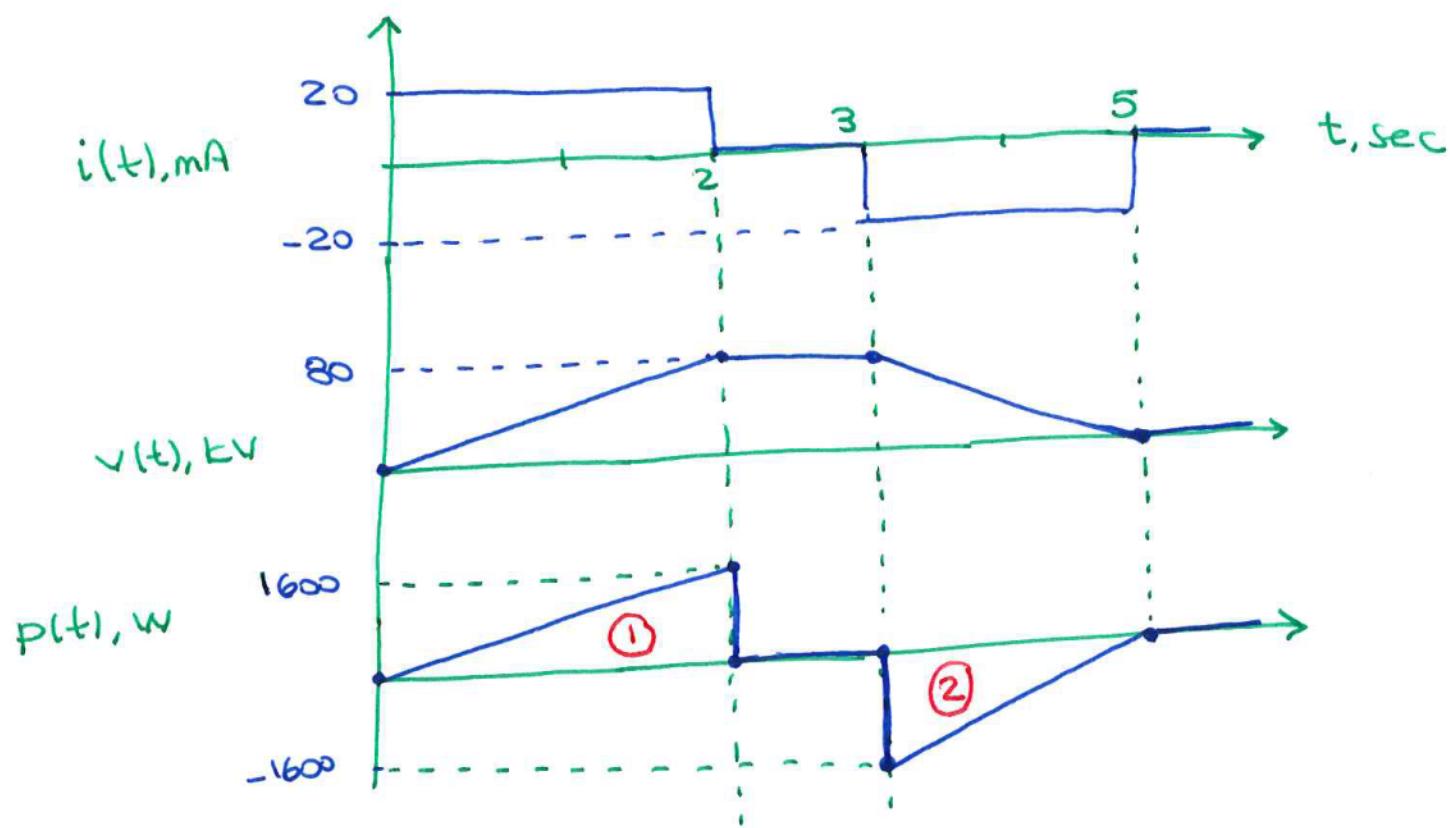


for $0 < t < 2 : p(t) = v(t).i(t) = 0.02 \times 40000t = 800t$

$3 < t < 5 : p(t) = v(t).i(t) = -0.02 (-40000t + 200000)$
 $= 800t - 4000$

interval ① : $p(t) > 0 \therefore$ capacitor is absorbing power during $0 < t < 2$; i.e. it is storing power

interval ② $p(t) < 0 \therefore$ capacitor is supplying power during $3 < t < 5$; i.e. it is returning stored power

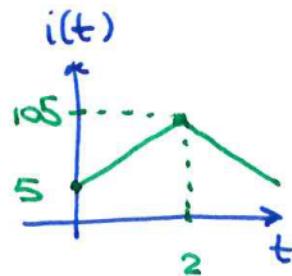• What if $i(t)$ is a 1st order function? e.g.:



To write an expression for $v(t)$, we need an expression for $i(t)$:

$$i(t) = mt + b$$

slope i(t) axis intercept

use 2 points from each interval (e.g. start & end points) to find m & b for that interval

• Suppose $i(t) = 50t + 5$ for $0 < t < 2$, then:

$$\begin{aligned} v(t) &= \frac{1}{C} \int_0^t (50\tau + 5) d\tau + v(0) \\ &= \frac{1}{C} \left(\frac{50\tau^2}{2} + 5\tau \right) \Big|_{\tau=0}^{\tau=t} + v(0) \\ &= \frac{1}{C} (25t^2 + 5t) + v(0) \end{aligned}$$

Inductor


• The circuit symbol is



← circuit parameter
for inductor

• Voltage-current relationship is:

$$V(t) = L \frac{di(t)}{dt}$$

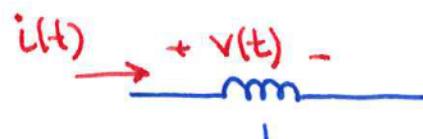

where:

V : voltage in Volts (V)

L : inductance in Henrys (H)

i : current in Amps (A)

t : time in seconds (s)

• Inductor Properties:


- 1) A constant current creates zero voltage drop. So, the inductor looks like a short circuit in DC.

$$v(t) = L \frac{di(t)}{dt}$$

$\stackrel{\text{const } i}{\cancel{L}}$

$= 0$ for constant i

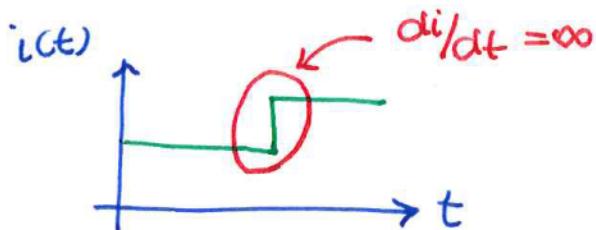- 2) Current through an inductor cannot change instantaneously. This would produce an infinite voltage



• Inductor current in terms of voltage:

$$i(t) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

Power & Energy in Inductors

$$i(t) \rightarrow + v(t) -$$

\cancel{L}

$$P(t) = v(t) \cdot i(t) = L \frac{di(t)}{dt} \cdot i(t)$$

Also $P \triangleq \frac{dW}{dt}$ defined as

$$\therefore dW = L \cdot di(t) \cdot i(t)$$

integrate both sides :

$$W(t) = \frac{1}{2} L i(t)^2$$

Inductors in series



KVL:

$$v(t) = v_1(t) + v_2(t) + v_3(t)$$

$$= L_1 \frac{di(t)}{dt} + L_2 \frac{di(t)}{dt} + L_3 \frac{di(t)}{dt}$$

$$= (L_1 + L_2 + L_3) \frac{di(t)}{dt}$$


$$\therefore L_{eq} = L_1 + L_2 + L_3$$

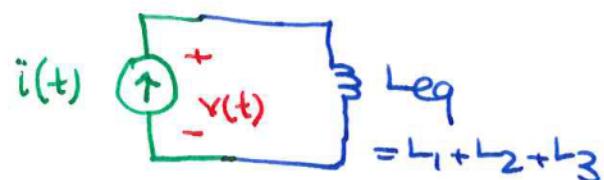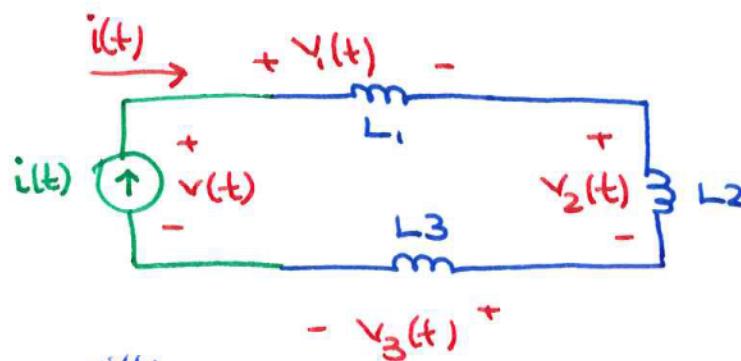

Inductors in series add

Inductors in parallel

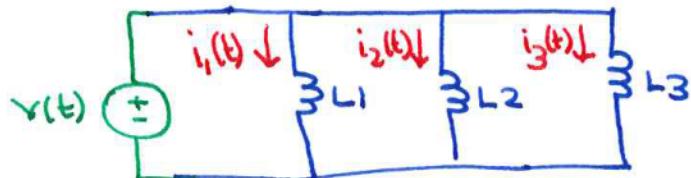Using KCL & $i_L(t) = \frac{1}{L} \int_0^t v(\tau) d\tau$





we can show that:

$$L_{eq} = \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right)^{-1}$$

similar to parallel resistors

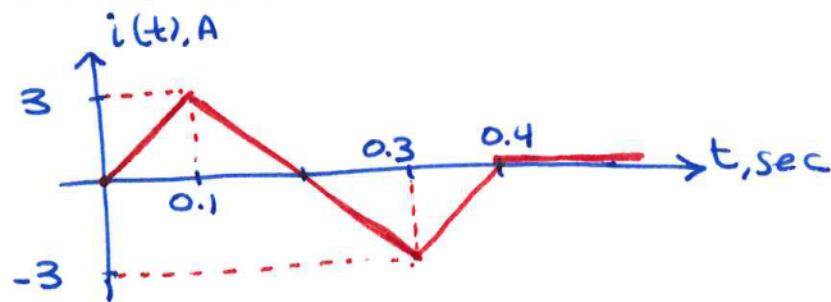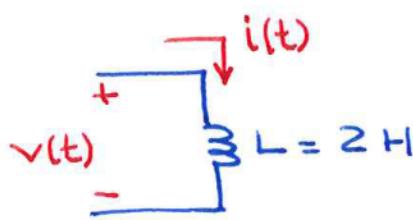Ex: Given $i(t)$ below, find $v(t)$, $P(t)$, $w(t)$



For an inductor, $v(t) = L \frac{di(t)}{dt}$

$0 < t < 0.1$

$$i(t) = m \cdot t + b$$

slope intercept

$b=0$ can be seen from the graph.

$$m = \text{slope} = \frac{\Delta i}{\Delta t} = \frac{3-0}{0.1-0} = 30$$

$$\therefore i(t) = 30t \text{ A}$$

$$v(t) = L \times 30 = 60 \text{ V}$$

$$P(t) = v(t) \cdot i(t) = 60 \times 30t = 1800t$$

$$w(t) = \frac{1}{2} L i(t)^2 = \frac{1}{2} \times 2 \times (30t)^2 = 900t^2$$

$0.1 < t < 0.3$

$$i(t) = m \cdot t + b$$

$$m = \frac{\Delta i}{\Delta t} = \frac{-3-3}{0.3-0.1} = -30$$

$$\therefore i(t) = -30t + b$$

use any point from the interval to find b :

using $i(0.2) = 0$ we can get $b = 6$

$$\therefore i(t) = -30t + 6 \text{ A}$$

$$v(t) = L \times -30 = -60 \text{ V}$$

$$P(t) = v(t) \cdot i(t) = 1800t - 360 \text{ W}$$

$$w(t) = \frac{1}{2} L (-30t + 6)^2$$

$$0.3 < t < 0.4$$

$$m=30 \text{ again} \quad \therefore i(t) = 30t + b$$

using $i(0.4) = 0$ we can get $b = -12$

$$\therefore i(t) = 30t - 12$$


$$v(t) = L \times 30 = 60 \quad v$$

$$p(t) = v(t) \cdot i(t) = 1800t - 720 \quad w$$

$$w(t) = \frac{1}{2} (\cancel{L}) (30t - 12)^2$$

$$t > 0.4$$
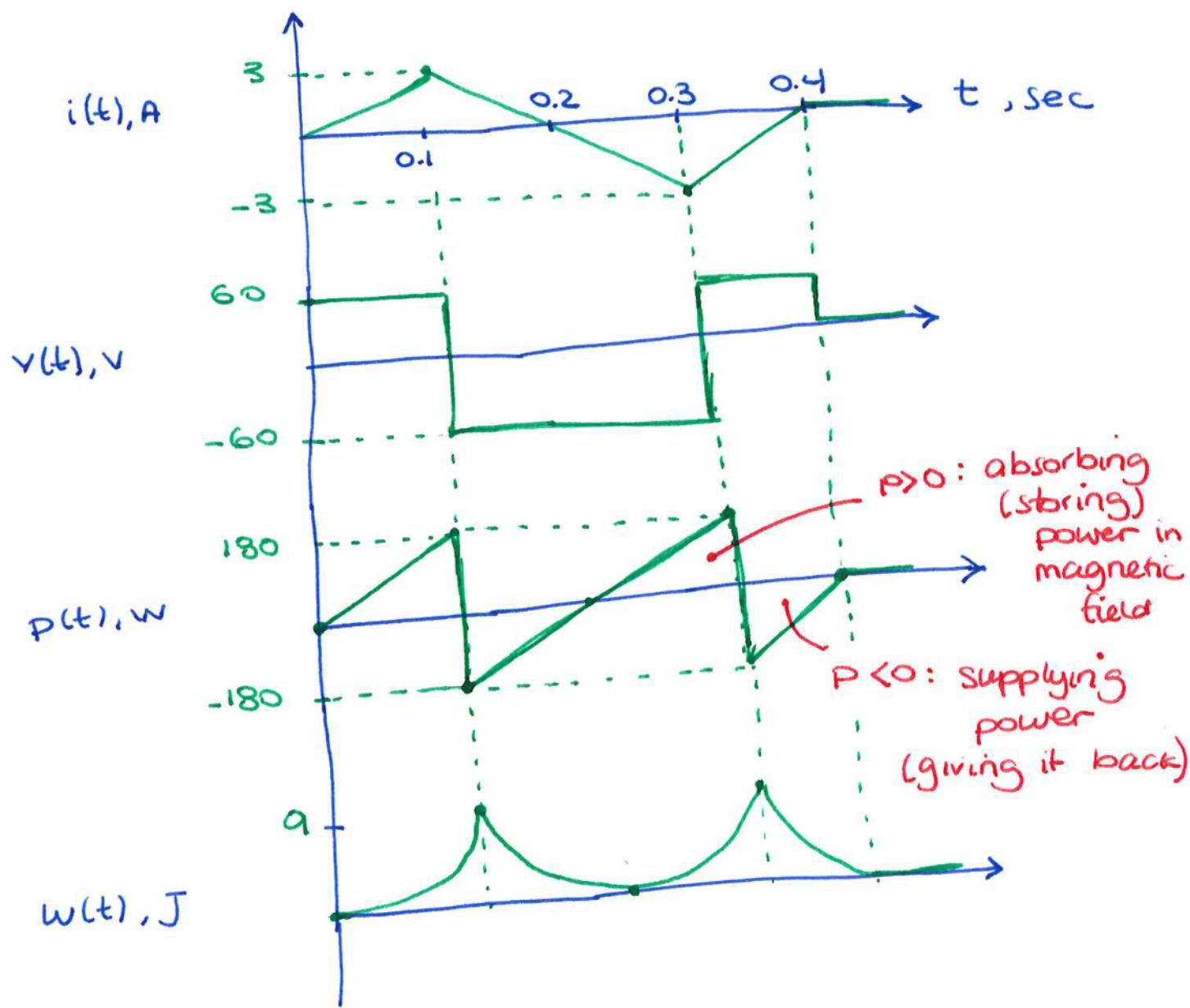
$$i(t) = 0 \quad \therefore v(t) = p(t) = w(t) = 0$$



Steady-State Sinusoidal Analysis


- So far, we have investigated circuits with DC sources. We now investigate circuits where sources deliver sinusoidal (AC) voltages & currents.

Sinusoidal voltages & currents

Let $v(t) = \underline{v_m} \cos(\omega t + \theta_v)$

peak ω : angular frequency (radians/sec)

↑ phase angle (radians)

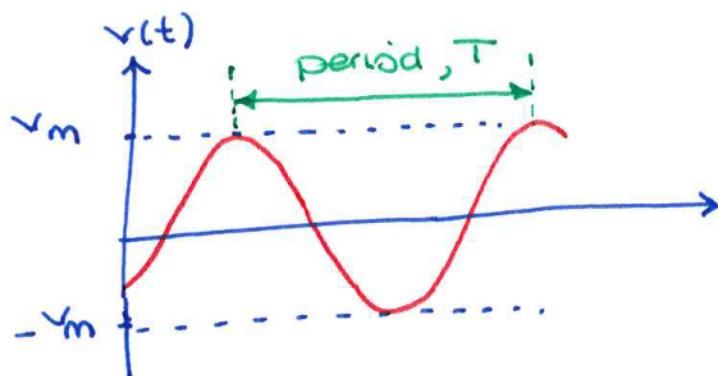

This sinusoid is periodic with period T . We have one complete period when phase angle changes by 2π .

- Frequency is defined as the number of complete periods (cycles) per second
- $$f = \frac{1}{T}$$
- frequency in Hertz (Hz)

we also have $\omega = 2\pi f$ (rad/s)

- We will cosine to express voltages & currents, not sine. They are related by:
- $$\begin{aligned}\sin(\omega t) &= \cos(\omega t - \pi/2) \\ &= \cos(\omega t - 90^\circ)\end{aligned}$$

we say sine has a phase angle of -90°