
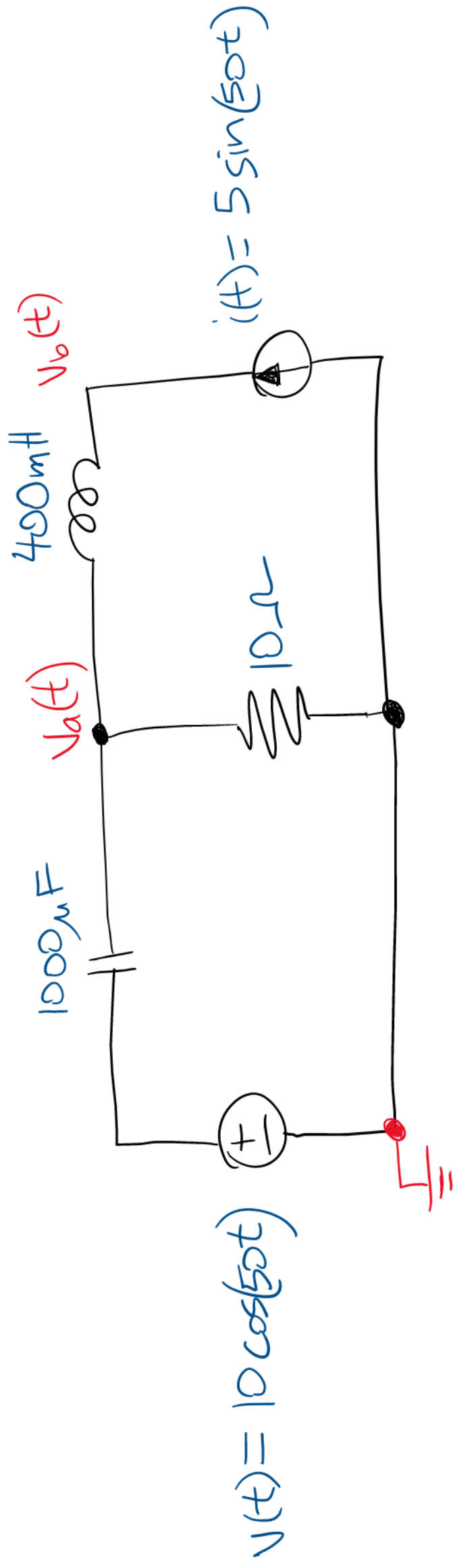


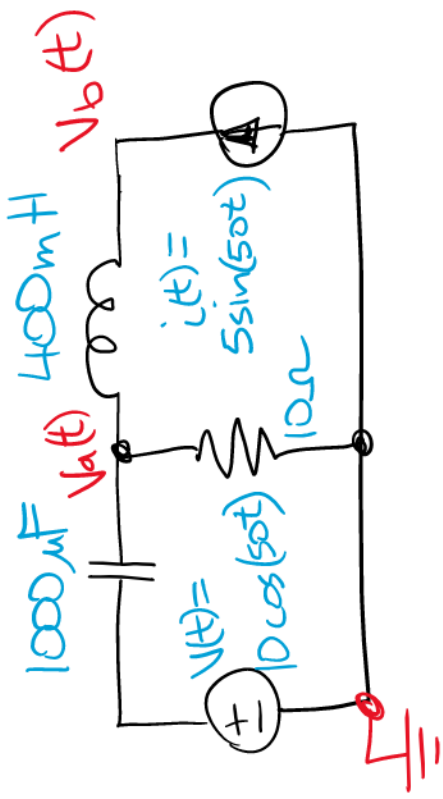Example:

Find the node voltages $V_a(t)$ and $V_b(t)$.



Example: Find the node voltages $V_a(t)$ and $V_b(t)$.




Let's write the node voltage equations symbolically. It's exactly the same format as for DC analysis.

$$\text{Node } A_0: \quad \frac{\bar{V}_a - \bar{V}}{Z_c} + \frac{\bar{V}_a}{R} + \frac{\bar{V}_a - \bar{V}_b}{Z_L} = 0 \quad (\text{eqn1})$$

$$\text{Node } B_0: \quad \frac{\bar{V}_b - \bar{V}_a}{Z_L} - \bar{I} = 0 \quad (\text{eqn2})$$


The basic AC circuit analysis is the same as for DC circuit analysis.

Is it different than \bar{I} ?

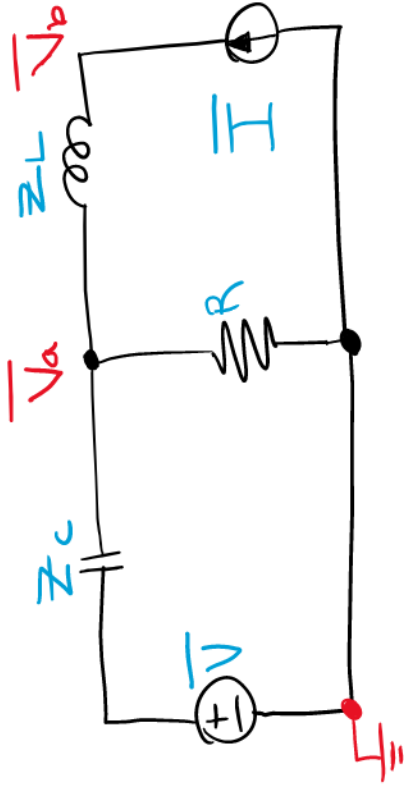

* What is $-\bar{I}$?

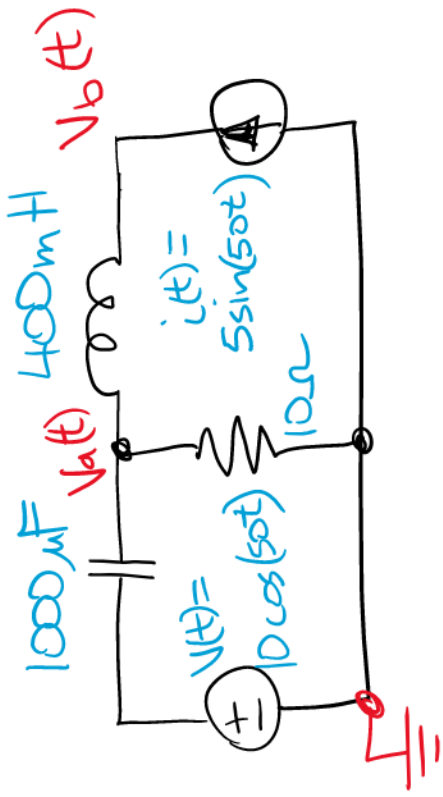Example: Find the node voltages $V_a(t)$ and $V_b(t)$.



$$\frac{\bar{V}_a - \bar{V}}{Z_c} + \frac{\bar{V}_a}{R} + \frac{\bar{V}_a - \bar{V}_b}{Z_L} = 0 \quad (\text{eqn 1})$$


$$\frac{\bar{V}_b - \bar{V}_a}{Z_L} - \bar{I} = 0 \quad (\text{eqn 2})$$

Let's develop the expressions for the phasors and impedances.


$$\bar{V} : V(t) = 10 \cos(50t) \quad \omega \text{ disappears}$$

$$V(t) = 10 \cos(50t + 0^\circ)$$

$$\bar{V} = 10 \angle 0^\circ = 10$$

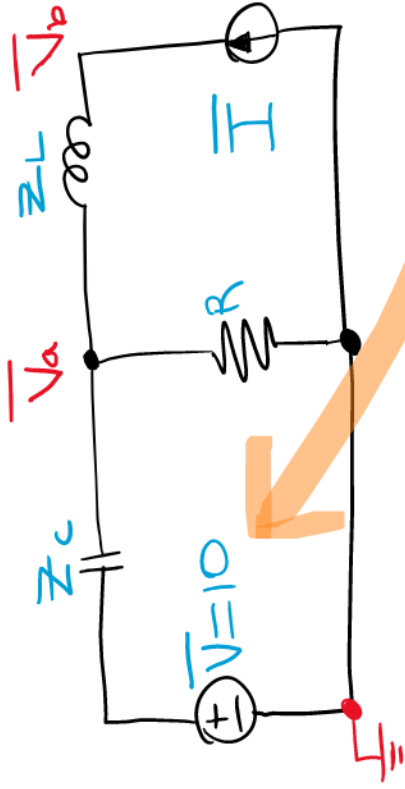

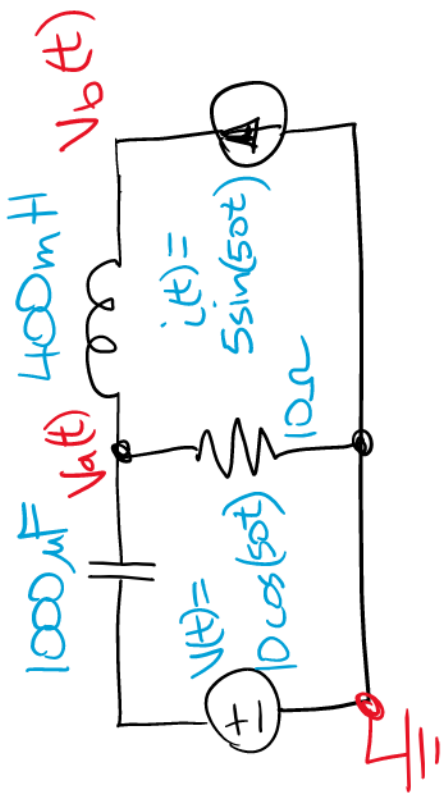Example: Find the node voltages $v_a(t)$ and $v_b(t)$.



$$\frac{\bar{V}_a - \bar{V}}{Z_c} + \frac{\bar{V}_a}{R} + \frac{\bar{V}_a - \bar{V}_b}{Z_L} = 0 \quad (\text{eqn 1})$$

$$\frac{\bar{V}_b - \bar{V}_a}{Z_L} - \bar{I} = 0 \quad (\text{eqn 2})$$


Let's develop the expressions for the phasors and impedances.

must convert to cosine form


$$\bar{I} : i(t) = 5 \sin(50t) \rightarrow 5 \cos(50t - 90^\circ)$$

$$i(t) = 5 \cos(50t - 90^\circ)$$

$$\bar{I} = 5 \angle -90^\circ$$

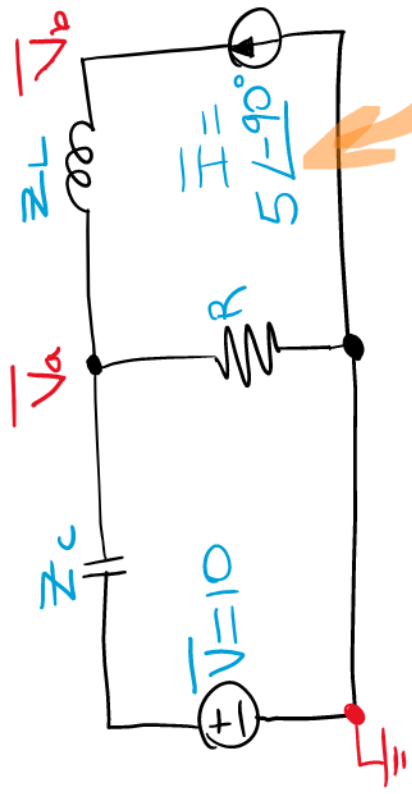

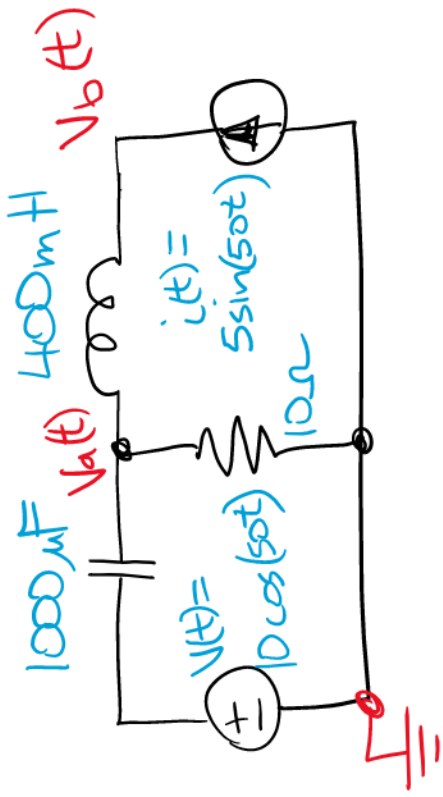Example: Find the node voltages $v_a(t)$ and $v_b(t)$.




$$\frac{\bar{V}_a - \bar{V}}{Z_c} + \frac{\bar{V}_a}{R} + \frac{\bar{V}_a - \bar{V}_b}{Z_L} = 0 \quad (\text{eqn 1})$$



$$\frac{\bar{V}_b - \bar{V}_a}{Z_L} - \bar{I} = 0 \quad (\text{eqn 2})$$

Let's develop the expressions for the phasors and impedances.

$$R : R = 10 \Omega$$

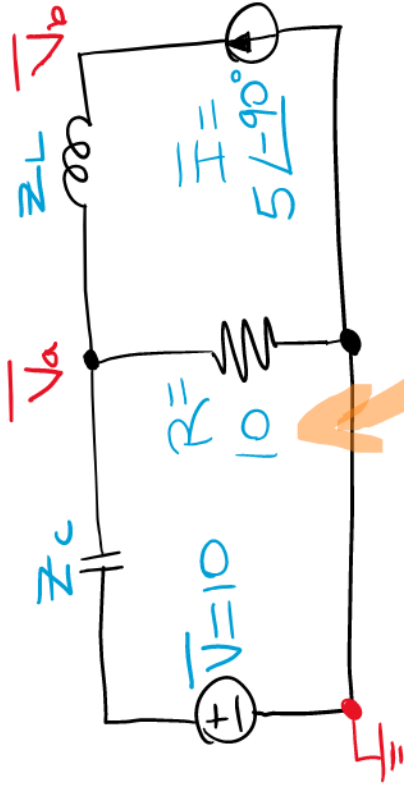

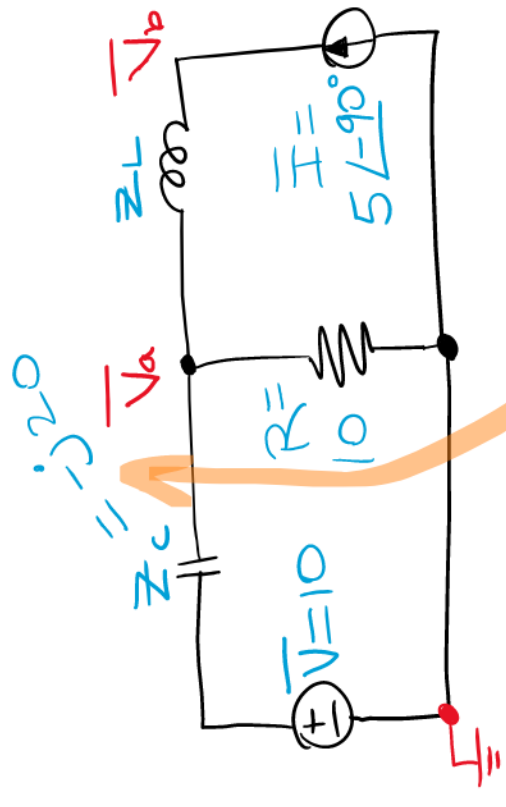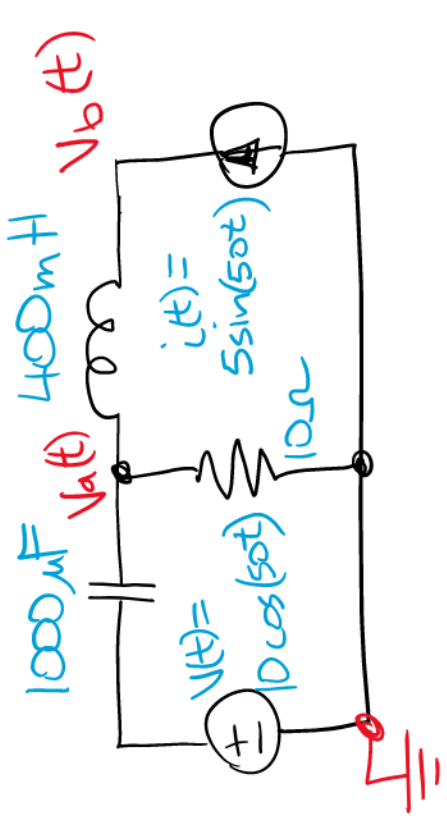Example: Find the node voltages $V_a(t)$ and $V_b(t)$.



$$\frac{\overline{V_a} - \overline{V}}{Z_c} + \frac{\overline{V_a}}{R} + \frac{\overline{V_a} - \overline{V_b}}{Z_L} = 0 \quad (\text{eqn 1})$$

$$\frac{\overline{V_b} - \overline{V_a}}{Z_L} - \overline{I} = 0 \quad (\text{eqn 2})$$

Let's develop the expressions for the phasors and impedances.

$$Z_c = \frac{1}{j\omega C}$$

$$C = 1000 \mu F$$



$$\omega = 50 \frac{\text{radian}}{\text{second}}$$

from $\cos(50t)$ and $\sin(50t)$

$$Z_c = \frac{1}{j \times 50 \times 1000 \times 10^{-6}} = -j20 \Omega$$

Recall:
 $\frac{1}{j} = -j$

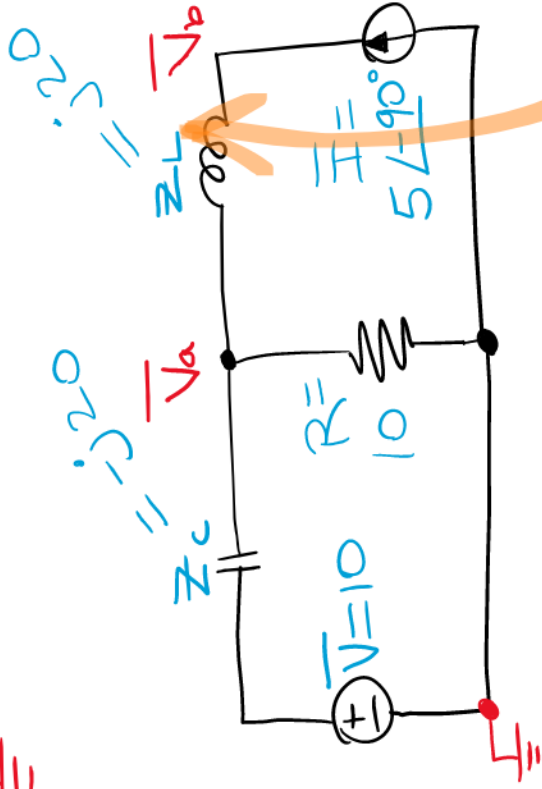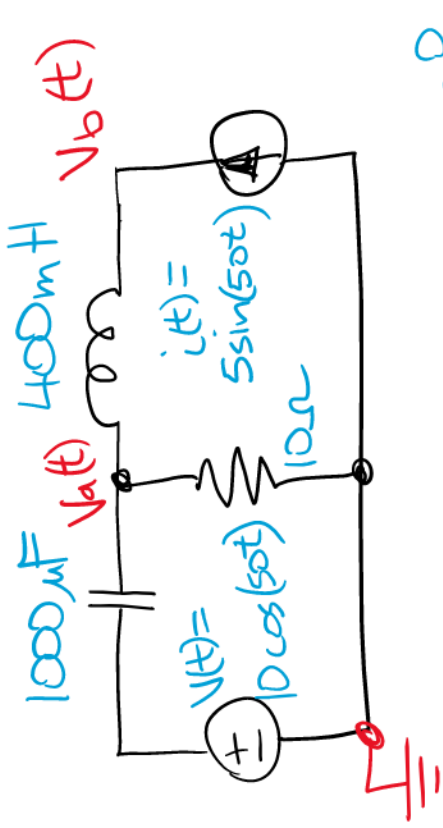Example: Find the node voltages $V_a(t)$ and $V_b(t)$.



$$\frac{\bar{V}_a - \bar{V}}{Z_c} + \frac{\bar{V}_a}{R} + \frac{\bar{V}_a - \bar{V}_b}{Z_L} = 0 \quad (\text{eqn 1})$$

$$\frac{\bar{V}_b - \bar{V}_a}{Z_L} - \bar{I} = 0 \quad (\text{eqn 2})$$

Let's develop the expressions for the phasors and impedances.



$$Z_L = j\omega L$$

$$\omega = 50 \frac{\text{radian}}{\text{second}}$$

$$L = 400 \text{ mH}$$

$$Z_L = j \times 50 \times 400 \times 10^{-3} = j20 \Omega$$

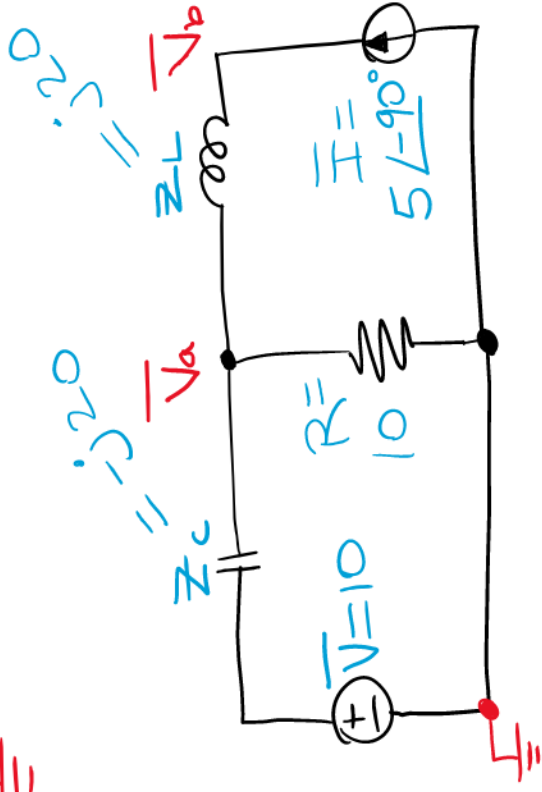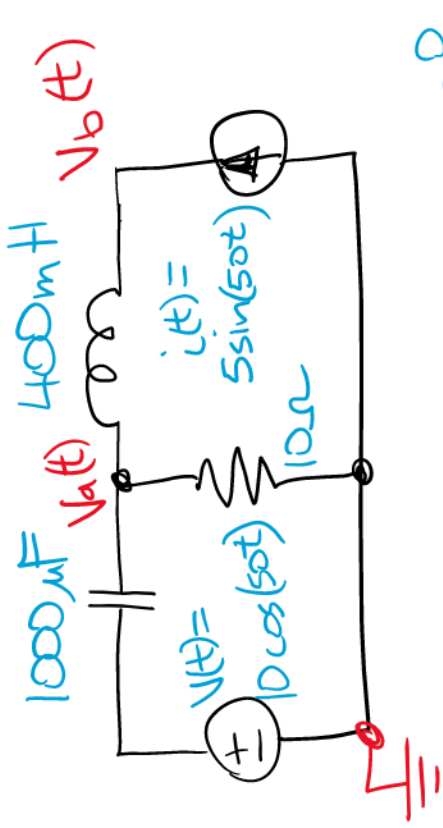Example: Find the node voltages $V_a(t)$ and $V_b(t)$.



$$\frac{\bar{V}_a - \bar{V}}{Z_c} + \frac{\bar{V}_a}{R} + \frac{\bar{V}_a - \bar{V}_b}{Z_L} = 0 \quad (\text{eqn 1})$$

$$\frac{\bar{V}_b - \bar{V}_a}{Z_L} - \bar{I} = 0 \quad (\text{eqn 2})$$



Plug in values into eqn 1

$$\frac{\bar{V}_a - 10}{-j20} + \frac{\bar{V}_a}{10} + \frac{\bar{V}_a - \bar{V}_b}{j20} = 0$$

$$(\times j20) \quad -(\bar{V}_a - 10) + j2\bar{V}_a + \bar{V}_a - \bar{V}_b = 0$$

Simplify $j2\bar{V}_a - \bar{V}_b = -10 \quad (\text{eqn 3})$

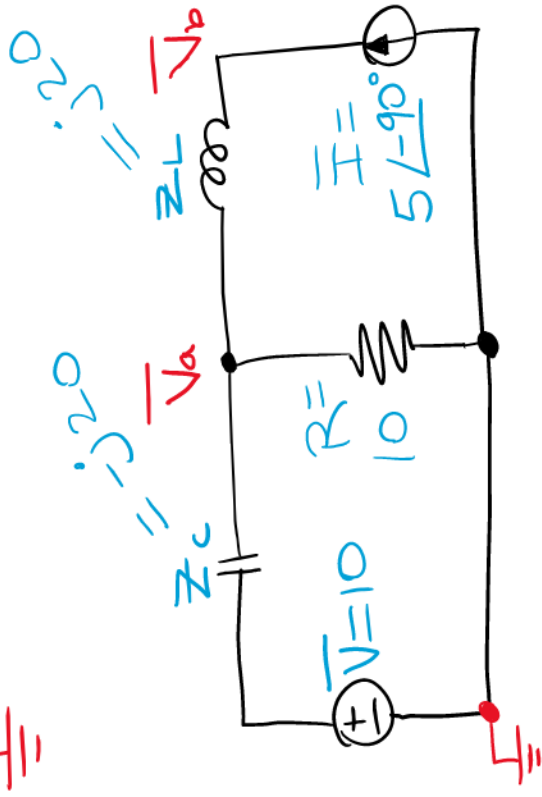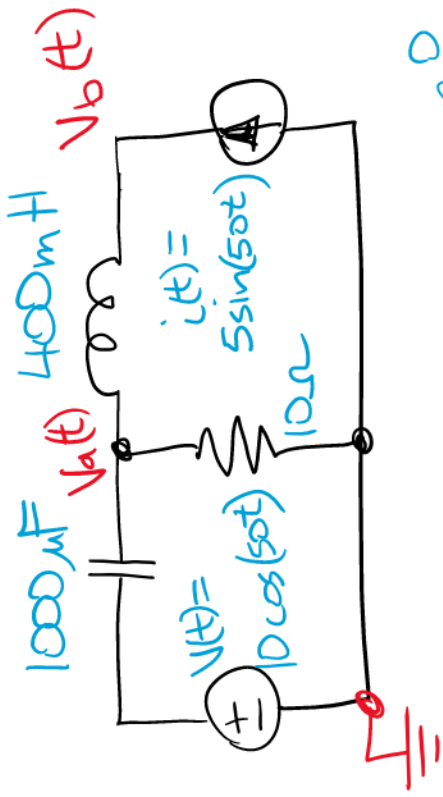Example: Find the node voltages $V_a(t)$ and $V_b(t)$.




$$\frac{\overline{V_a} - \overline{V}}{Z_c} + \frac{\overline{V_a}}{R} + \frac{\overline{V_a} - \overline{V_b}}{Z_L} = 0 \quad (\text{eqn 1})$$

$$j2\overline{V_a} - \overline{V_b} = -10 \quad (\text{eqn 3})$$

Plug in values into eqn 2
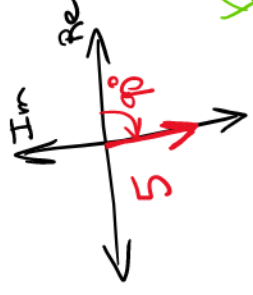
$$\frac{\overline{V_b} - \overline{V_a}}{j20} - 5 \angle -90^\circ = 0$$



mixed
rectangular
and polar
form

$$5 \angle -90^\circ = 0 - j5 = -j5$$



$$\text{Then } \frac{\overline{V_b} - \overline{V_a}}{j20} - (-j5) = 0$$

$$(xj20) \quad \overline{V_b} - \overline{V_a} - 100 = 0$$

$$\overline{V_b} - \overline{V_a} = 100 \quad (\text{eqn 4})$$

$$\frac{\overline{V_b} - \overline{V_a}}{Z_L} - \overline{I} = 0 \quad (\text{eqn 2})$$

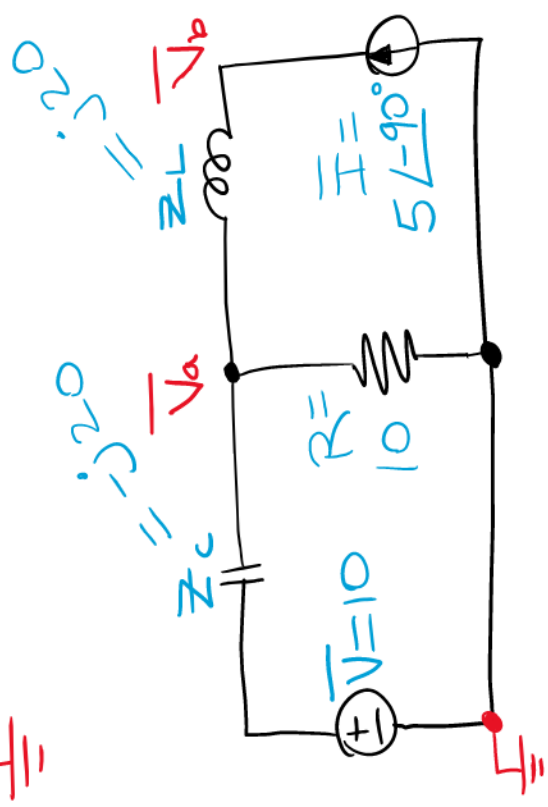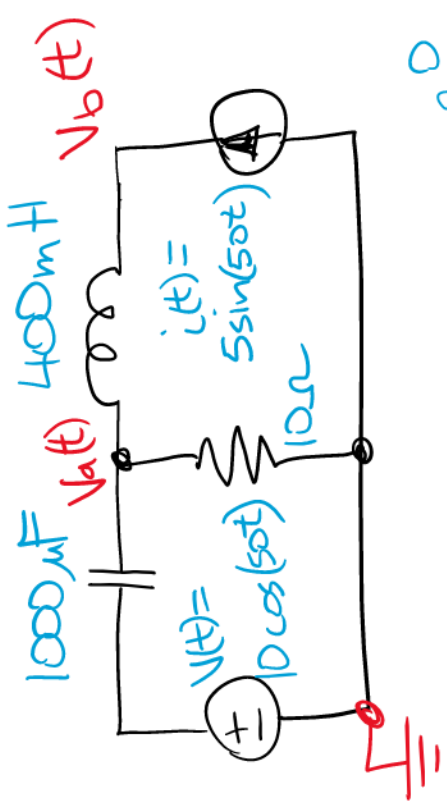Example: Find the node voltages $V_a(t)$ and $V_b(t)$.



$$j2\bar{V}_a - \bar{V}_b = -10 \quad (\text{eqn 3}) \quad \bar{V}_b - \bar{V}_a = 100 \quad (\text{eqn 4})$$

Add eqn 3 and eqn 4

$$\begin{aligned} j2\bar{V}_a - \bar{V}_b &= -10 \\ + \quad \bar{V}_b - \bar{V}_a &= 100 \\ \hline -\bar{V}_a + j2\bar{V}_a + 0 &= 90 \end{aligned}$$

need to convert
to standard form:
 $\bar{X} = \text{Re}[\bar{X}] + j\text{Im}[\bar{X}]$



$$\bar{V}_a = \frac{90}{-1+j2}$$

$$\begin{aligned} \text{(factor)} \quad \bar{V}_a(-1+j2) &= 90 \Rightarrow \bar{V}_a = \frac{90}{-1+j2} \\ &= \frac{-90-j180}{1+4} = \frac{-90-j180}{5} \end{aligned}$$

$$\text{(multiply by complex conjugate)} \quad \bar{V}_a = \frac{90}{-1+j2} \times \frac{-1-j2}{-1-j2} = \frac{-90-j180}{1+4}$$

$$\bar{V}_a = -18 - j36$$

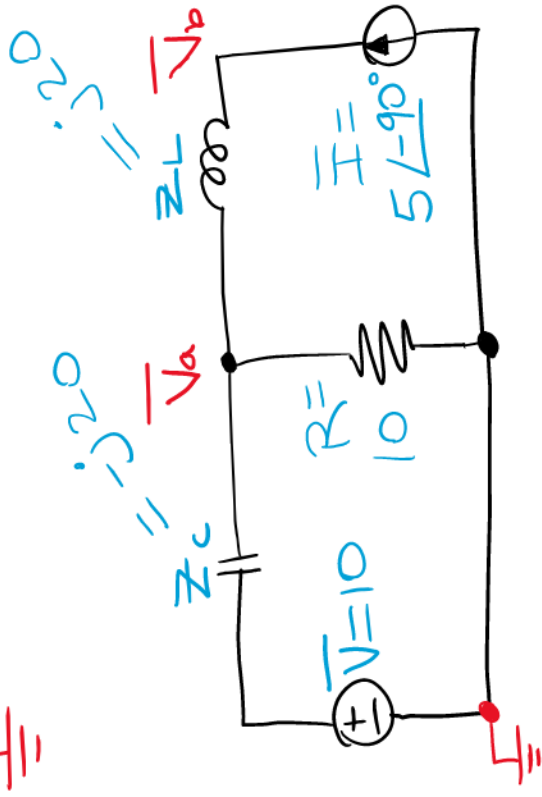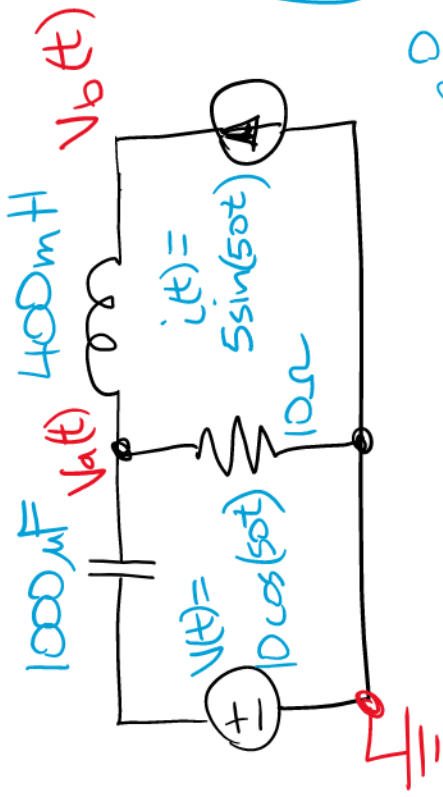Example: Find the node voltages $V_a(t)$ and $V_b(t)$.



$$j2\overline{V_a} - \overline{V_b} = -10 \quad (\text{eqn 3}) \quad \overline{V_b} - \overline{V_a} = 100 \quad (\text{eqn 4})$$



$$\overline{V_a} = -18 - j36$$

$$\overline{V_b} - (-18 - j36) = 100$$

(Sub $\overline{V_a}$ into eqn 4)

$$\overline{V_b} = 82 - j36$$

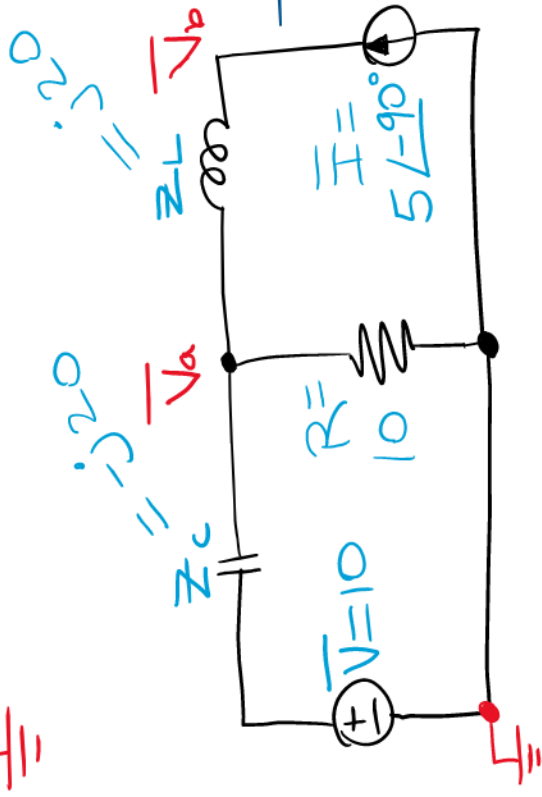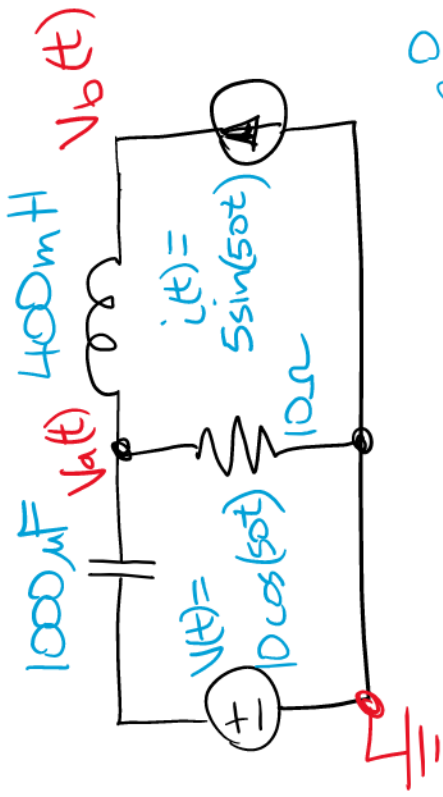
Example: Find the node voltages $V_a(t)$ and $V_b(t)$.



Now, convert from polar form to time domain

$$\bar{V}_a = -18 - j36$$

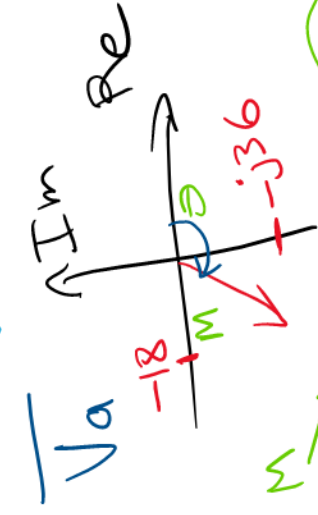To find the time domain ($V_a(t), V_b(t)$) representation, we must convert the rectangular representation to polar representation.




$$\bar{V}_a = \sqrt{18^2 + 36^2} \angle -180^\circ + \tan^{-1}\left(\frac{36}{18}\right)$$

$$\bar{V}_a = 40.25 \angle -116.6^\circ$$

$$V_a(t) = 40.25 \cos(50t - 116.6^\circ)$$

$$\bar{V}_b = 82 - j36$$

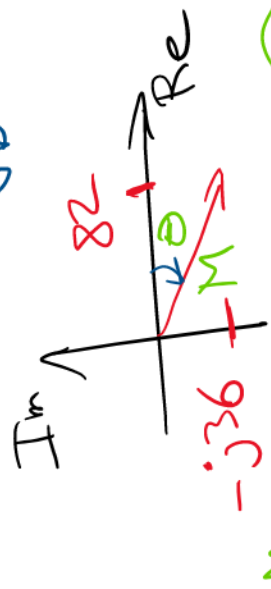

$$\bar{V}_b = \sqrt{36^2 + 82^2} \angle \tan^{-1}\left(\frac{-36}{82}\right)$$

$$\bar{V}_b = 89.55 \angle -23.7^\circ$$


$$V_b(t) = 89.55 \cos(50t - 23.7^\circ)$$

A couple ways to solve for $V_a(t)$

$$\bar{V}_a = \frac{90}{-1+j2}$$

$$\bar{V}_a = \frac{90}{-1+j2} \times \frac{-1-j2}{-1-j2} = \frac{-90-j180}{1+4}$$
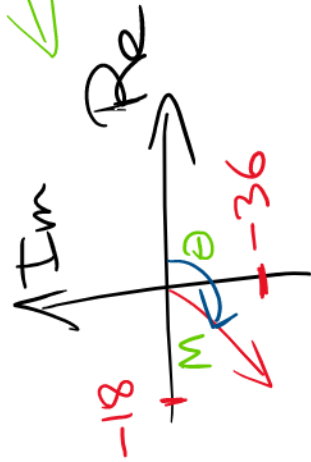
$$\bar{V}_a = \frac{-90-j180}{5} = -18-j36$$




$$\bar{V}_a = \frac{-18-j36}{5} = \frac{\sqrt{(-18)^2 + (-36)^2} \angle -180 + \tan^{-1}(\frac{36}{18})}{5}$$

$$\bar{V}_a = 40.25 \angle -116.6^\circ$$

$$V_a(t) = 40.25 \cos(50t - 116.6^\circ)$$

$$\bar{V}_a = \frac{90}{-1+j2}$$

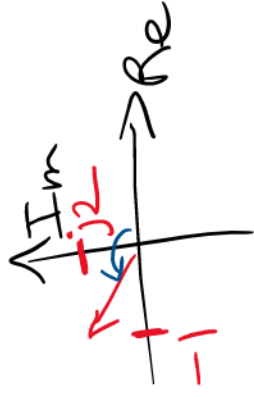

$$-1+j2 \Rightarrow \sqrt{(-1)^2 + (2)^2} \angle 180^\circ - \tan^{-1}(\frac{2}{1})$$

$$= \sqrt{5} \angle 116.6^\circ$$

Then

$$\bar{V}_a = \frac{90}{-1+j2} = \frac{90}{\sqrt{5} \angle 116.6^\circ}$$

$$\bar{V}_a = 40.25 \angle -116.6^\circ$$

$$V_a(t) = 40.25 \cos(50t - 116.6^\circ)$$

same

What is the difference between \bar{I} and $-\bar{I}$ or \bar{V} and $-\bar{V}$? Don't AC waveforms go positive and negative anyway?

$$\text{Let } \bar{V} = 10 \angle 0^\circ$$

$$\text{then } v(t) = 10 \cos(\omega t)$$

$$\text{This implies } -\bar{V} = -10 \angle 0^\circ$$

$$\text{then } -v(t) = -10 \cos(\omega t)$$

we can also say:

$$-v(t) = -10 \cos(\omega t) = 10 \cos(\omega t + 180^\circ) = 10 \cos(\omega t - 180^\circ)$$

$$-\bar{V} = -10 \angle 0^\circ = 10 \angle -180^\circ$$

